

# Understanding H1's O3 B Electronics Compensation Systematic Error

J. Kissel for the Calibration Group

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{\text{UIM}}$
8. Converting sys error in  $A_{\text{UIM}}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

1. Review of the Circuit
2. Fit Results for each channel
3. Converting fit results in to systematic error in C
4. Converting sys error in C to sys error in R

# But -- your time is valuable

This is 126 page slide show. Here are the answers, in case you don't have time to be educated as to how I came to each conclusion, with the confusing details and the lessons learned that got me to it. I hope at least some folks read it.

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

- **Executive summary:** non-Jeff's everywhere whom guessed the answer ahead of time are vindicated in that the UIM electronics error -- either from differences in compensation between states, or poor compensation in general – doesn't substantially contribute to the response function systematic error. (See slide 70 for quantitative answer)
- We may safely proceed with O3B chunk 1 uncertainty budget development without including this systematic error.
  - Note that this would have \*not\* been "covered" by the GPR even if it were non-negligible.

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

- **Executive summary:** While I can predict the systematic error from the configuration switch, it also doesn't substantially contribute to the response function systematic error (see slide 124 for quantitative answer).
- We can probably proceed with O3B chunk 2 uncertainty development without including this systematic error.
- We need to remeasure and recompensate the OMC Whitening Chassis.
- We need to find out what happened on / around 2020-03-23 instead.
- We need to use different measurements we have to make the best guess for the systematic error...

PART I:  
The ETMX UIM Driver,  
from Nov 27 to Dec 03 2019

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

- 1. Why do you care about the UIM?**
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{\text{UIM}}$
8. Converting sys error in  $A_{\text{UIM}}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020


# I.1 Why do you care about the UIM?

- The UIM always gets pushed to “low priority” because “we should be rolling off its authority fast enough that it doesn’t matter in the detection band.”
- That means: we ignore it, assuming anything we do above 10 Hz to the UIM doesn’t matter, and don’t stress about the consequences when we change something until it’s too late.
- We’ve already identified one systematic error in the UIM that has bit us ‘cause we ignored it: the nasty bending response of the UIM Blade + Non-magnetic Blade Dampers.
- This amplifies the contribution of the UIM to the response function at 150 Hz, making **\*all\*** UIM systematic error important, right in the bucket. (This is true only for H1, which doesn’t roll off their UIM fast enough. L1 should be safe.)
- **But also: this is the era of the 1%. Even when we fix the UIM contribution by rolling it off faster, this study emphasizes that we must question everything and *\*confirm\** *\*quantitatively\** that something is “negligible.”**
- **This didactic presentation is good practice, and by presenting in great detail, I aim to train the next generation, lest the art of understanding analog electronics analysis dies.**

# I.1 Why do you care about the UIM?
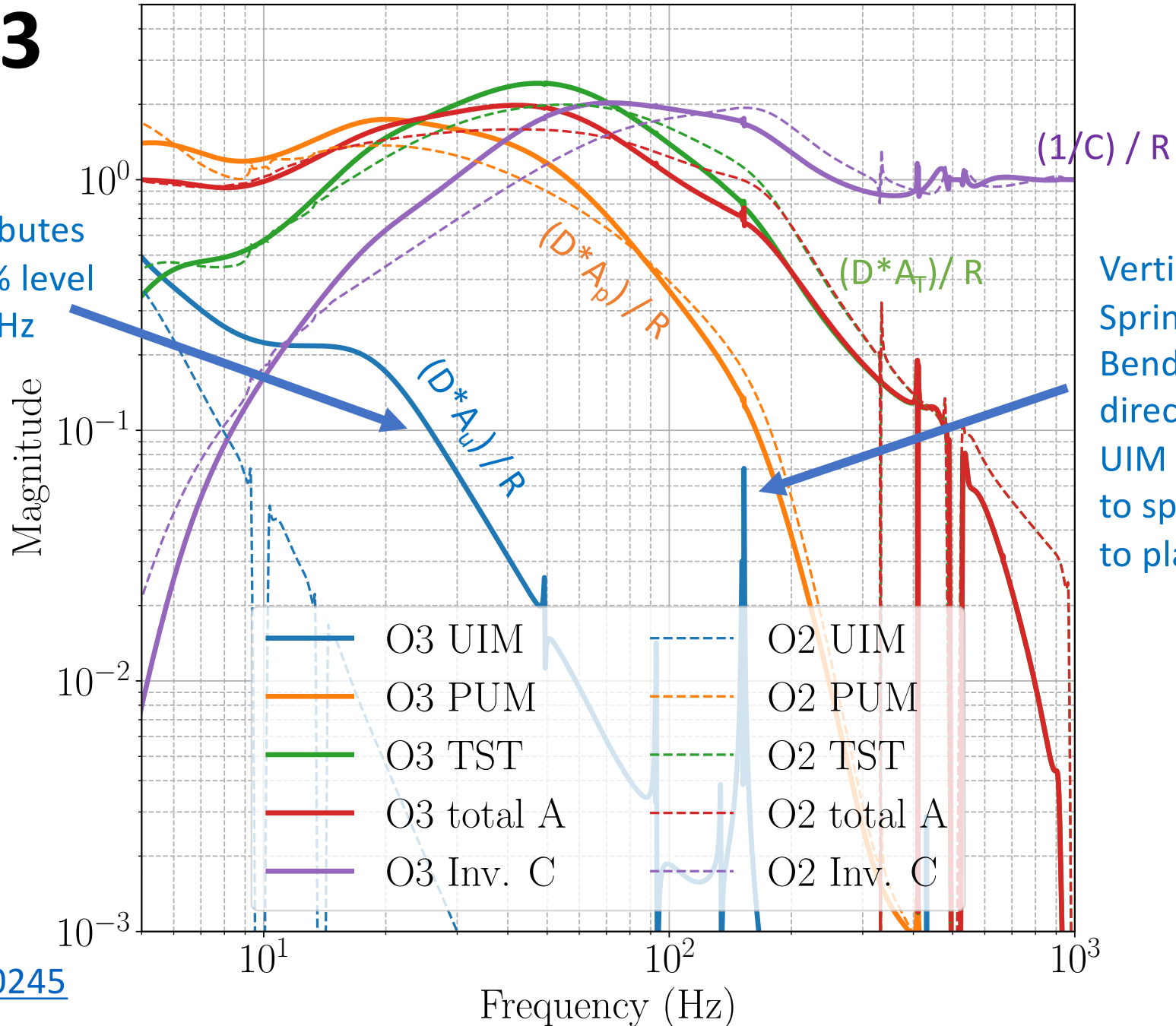
## H1 O3

UIM Contributes at the ~10% level out to ~25 Hz



Vertical Blade Spring Twisting / Bending in L direction causes UIM contribution to spike back in to play at 150 Hz

Figure 4  
from [P1900245](#)

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
- 2. Review where we were before we started**
3. Review of the Circuit
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{\text{UIM}}$
8. Converting sys error in  $A_{\text{UIM}}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020




# I.2 Review of where we were before starting

UIM Driver State Machine  
Modified as per T1400233  
T1100507-v8

STATE 1: All Lowpasses OFF

	simLP1 [10.5 : 1]	simLP2 [10.5 : 1]	simLP3 [10.5 : 1]	
FM1	FM2	FM3	FM4	FM5
antiAcq [300 : 85]	antiLP1 [1 : 10.5]	antiLP2 [1 : 10.5]	antiLP3 [1 : 10.5]	
FM6	FM7	FM8	FM9	FM10

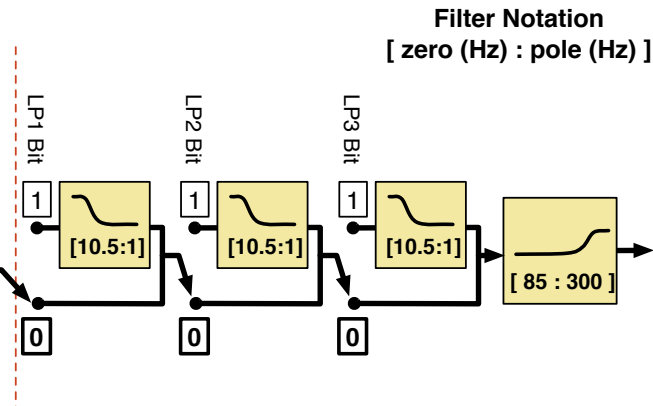

- During O1 and O2, we were using all ETMY stages for the DARM actuators, the UIM included.
- We updated the low-pass compensation filters on ETMY based on fit to measurements [\[LHO:21283\]](#), but we only used the “DTT measurements with the coil driver monitor circuits” technique, which are insensitive to the 85:300 zero:pole pair which results from the output impedance network [\[LHO:21142\]](#), and we ran out of time (remember GW150914?), so we didn’t update the antiAcq filter.
- We ran in ETMY, UIM, State 1 for all of O1 and O2, so the updates didn’t actually matter (Sorry Darkhan!).
- In Jan 2019, 4 months before O3, we made the switch to using all ETMX stages for the DARM actuator.
- The UIM electronics were fully measured in analog on Feb 03 2019 (yes, a Sunday!), by Rich Abbott and Jeff Kissel. Rich was unconvinced that we needed the differential driver full setup as described in [D1900027](#), so we did some sort of single-ended, direct via clip-leads measurement [\[LHO:46927\]](#) (this becomes important later).
- Lilli tried to fit the State 1 data, but they didn’t make any sense to us at the time [\[LHO:47195\]](#).
- We did take the DTT data on Feb 07 2019 to update the low pass compensation, but never got to processing it.
- Because of confusion about the results in the State 1 measurements, and because the UIM was low priority, we just chose not to update anything: [\[LHO:47167\]](#). (Remember ER14 and how there was systematic error everywhere [\[LHO:47378\]](#)?)
- Flash-forward to Nov 27 2019, we got suspicious of DAC quantization noise [\[LHO:53376\]](#), and switched the ETMX UIM driver to State 2 [\[LHO:53528\]](#), forgetting the terrible state of the compensation, and assuming “the UIM doesn’t matter.”
- Only 6 days later on Dec 03 2019 (and thus in between regular calibration sweeps), we reverted back to State 1 [\[LHO:53652\]](#).
- **The switch happened between two regular actuator sweeps (taken on 2019-11-11 and 2019-12-04), so there for we must model what the systematic error with the measurements we have (namely, the Feb 03 2019 data) for this 6 day period, in which -- of course -- there lies [GW191129](#).**

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
- 3. Review of the Circuit**
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{\text{UIM}}$
8. Converting sys error in  $A_{\text{UIM}}$  to sys error in R and Conclusions


## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# I.3 Review of the Circuit: Forest through the Trees

To understand the 2019-02-03 data, we need to understand the circuit and the measurement.


Let's start with the circuit: [D070481](#), specifically, the [UIMCircuit v5.pdf](#)

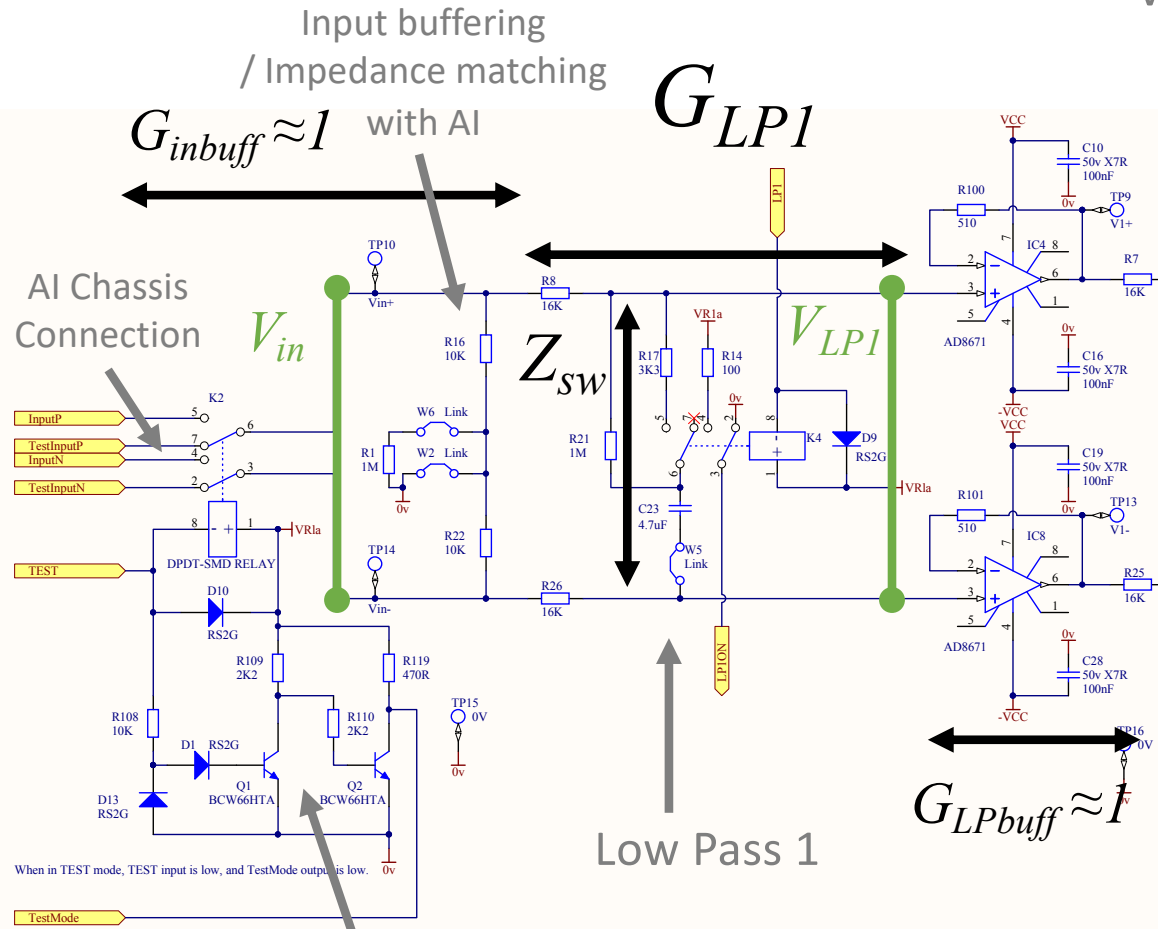It looks intimidating, so I'll start with the parts, and break it down to the parts that are important to our story.



Voltage Monitor Circuit

Pickoff

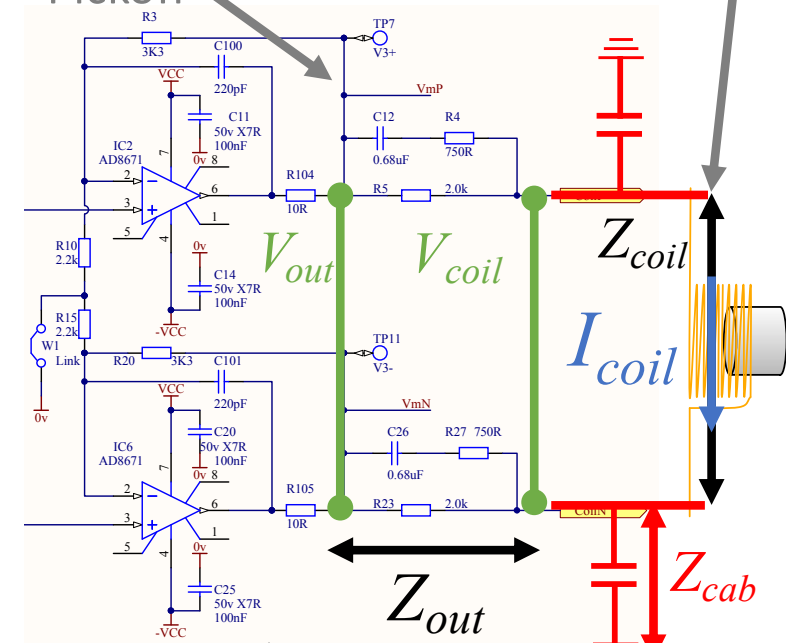

The BOSEM Coil Connected across P and N legs


Identical Low Passes 2 and 3 not shown

Output Current Driver

Output Impedance Network

# I.3 Review of the Circuit: simplified, Differential

Here's the circuit Simplified.

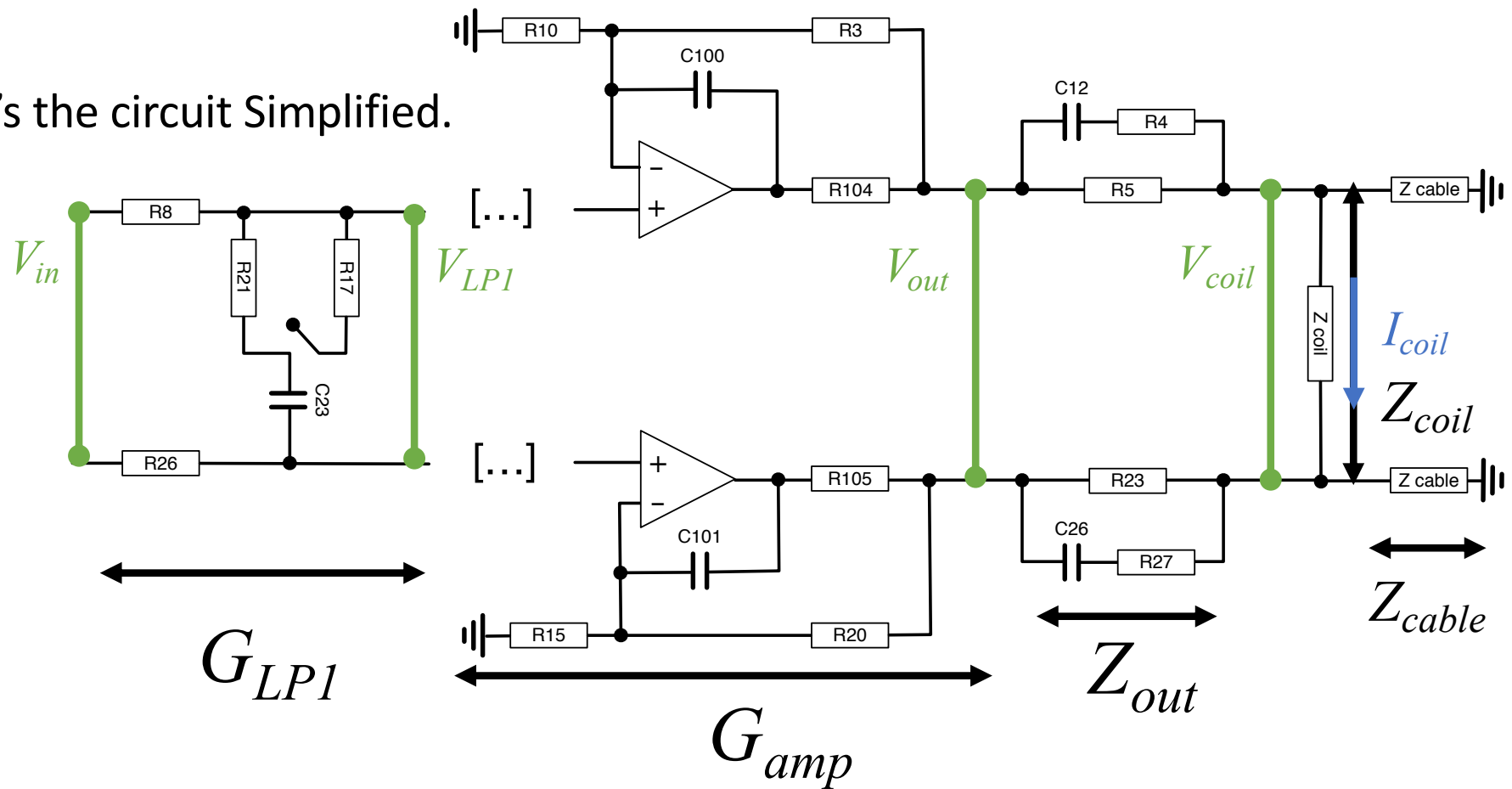

- All parts of the circuit that have gain, but no frequency dependence, we just ignore. We'll scale the gain of all models to the measurement in the end. We're looking for poles and zeros
- The low pass, the output impedance network, and the coil will define the "important" poles and zeros (below 1 kHz). (I wonder if the output current amplifier is important later)
- In the end, the "transfer function" we want the *transconductance* of the driver / coil system:  $I_{coil} / V_{in}$

# I.3 Review of the Circuit: Trust the Basics


Here's a friendly reminder of the tools in the circuit analysis toolbox:

Converting to Impedance:

$$Z_R = R$$


$$Z_C = 1/i\omega C$$


$(\omega = 2\pi f)$



$$Z_L = i\omega L$$


Series Impedance:


$$Z_{tot}^S = Z_1 + Z_2 + \dots$$

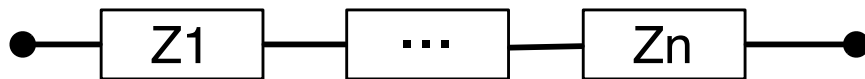

Parallel Impedance:

$$\frac{1}{Z_{tot}^P} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$$

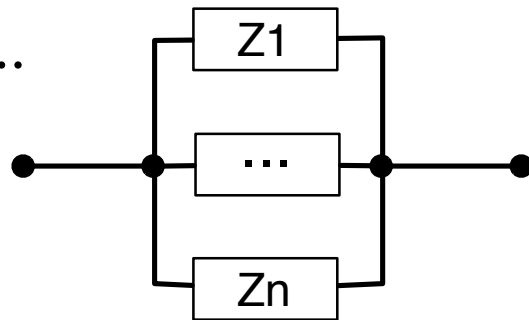
$$Z_{tot}^{P(2)} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$



Ohm's Law:


$$V = I Z$$

Voltage Divider:

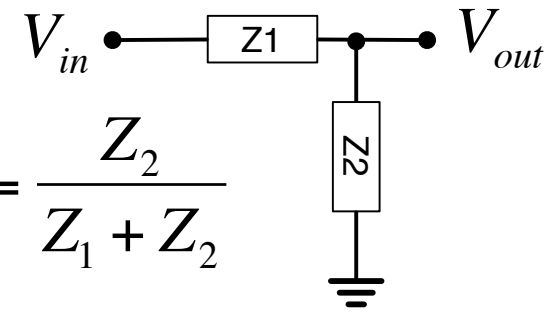


$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

Non-inverting Op-Amp

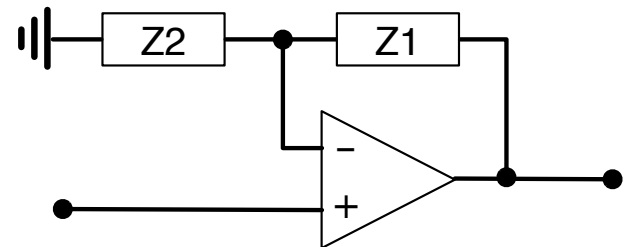


$$\frac{V_{out}}{V_{in}} = 1 + \left(\frac{Z_1}{Z_2}\right)$$

Inverting Op-Amp

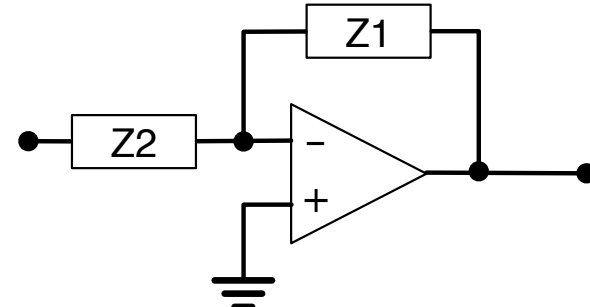

$$\frac{V_{out}}{V_{in}} = -\left(\frac{Z_1}{Z_2}\right)$$
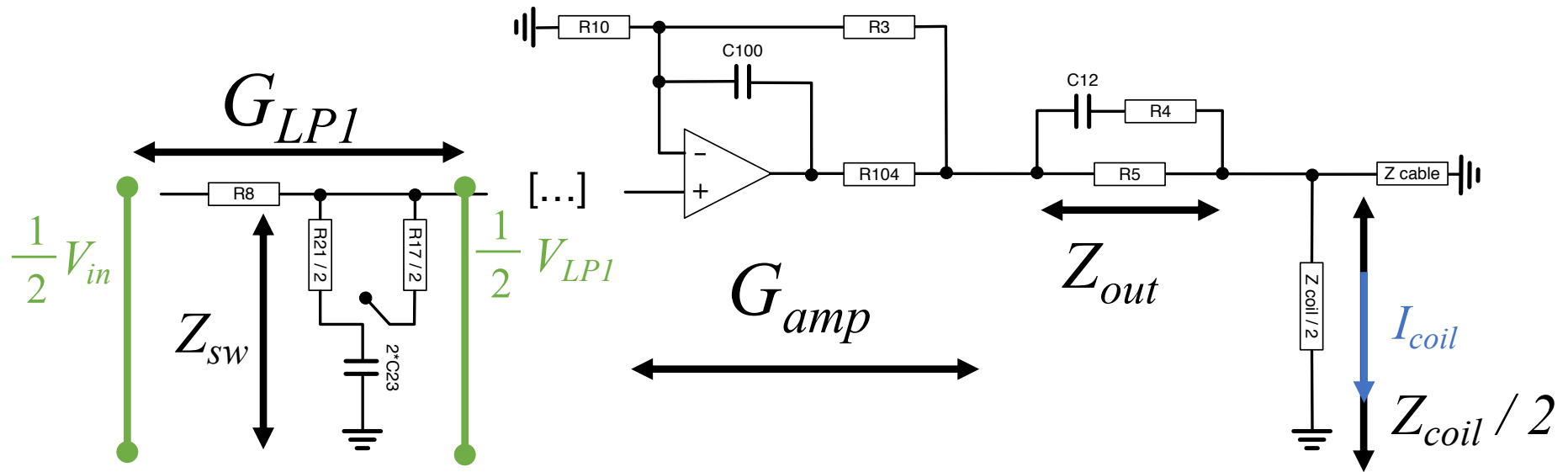
# I.3 Review of the Circuit: Simplified, Single-Ended



- **One trick for differential circuit analysis:** consider only one leg, and divide everything that “crosses between legs” by two -- voltage, impedance, etc, -- and reference everything to ground (0V). The transfer functions are the same, and the analysis is equivalent.

$$Z_{sw}^{Open}(\omega) = \frac{1}{2} \left( R_{21} + \frac{1}{i\omega C_{23}} \right)$$

$$Z_{sw}^{Closed}(\omega) = \frac{1}{2} \left( \left[ \frac{R_{17}R_{21}}{R_{17} + R_{21}} \right] + \frac{1}{i\omega C_{23}} \right)$$

$$\frac{(1/2) V_{LP1}}{(1/2) V_{in}} = \frac{V_{LP1}}{V_{in}} = G_{LP1} = \frac{Z_{sw}}{R_8 + Z_{sw}}$$

With the switch closed, that means,

$$G_{LP1} \Big|_{closed} = \frac{\frac{1}{2} \left( \left[ \frac{R_{17}R_{21}}{R_{17} + R_{21}} \right] + \frac{1}{i\omega C_{23}} \right)}{R_8 + \frac{1}{2} \left( \left[ \frac{R_{17}R_{21}}{R_{17} + R_{21}} \right] + \frac{1}{i\omega C_{23}} \right)}$$

which is enough to plot the transfer function, but we can re-arrange to show the analytic computation of the poles and zeros of this TF...

# I.3 Review of the Circuit: The Low Pass

$$G_{LP1}|_{closed} = \frac{\left(1 + i\omega \left[\frac{R_{17}R_{21}}{R_{17} + R_{21}}\right] C_{23}\right)}{\left(1 + i\omega \left(R_8 + \frac{1}{2} \left[\frac{R_{17}R_{21}}{R_{17} + R_{21}}\right]\right) (2C_{23})\right)}$$

That means

$$f_z^{LP1}|_{closed} = 1 / \left(2\pi \left[\frac{R_{17}R_{21}}{R_{17} + R_{21}}\right] C_{23}\right) = 10.2953 \text{ Hz} \quad \frac{1}{2} V_{in}$$

$$f_p^{LP1}|_{closed} = 1 / \left(2\pi \left[R_8 + \frac{1}{2} \frac{R_{17}R_{21}}{R_{17} + R_{21}}\right] (2C_{23})\right) = 0.9596 \text{ Hz}$$


Consistent with the expected low pass z:p = (10.5 : 1.0) Hz.

With the switch open, Rpara reduces to R17, leaving,

$$G_{LP1}|_{open} = \frac{1 + i\omega R_{21} C_{23}}{1 + i\omega \left(R_8 + \frac{1}{2} R_{21}\right) (2C_{23})}$$

$$f_z^{LP1}|_{open} = 1 / (2\pi R_{21} C_{23}) = 0.0339 \text{ Hz}$$



$$f_p^{LP1}|_{closed} = 1 / \left(2\pi \left[R_8 + \frac{1}{2} R_{21}\right] (2C_{23})\right) = 0.0328 \text{ Hz}$$

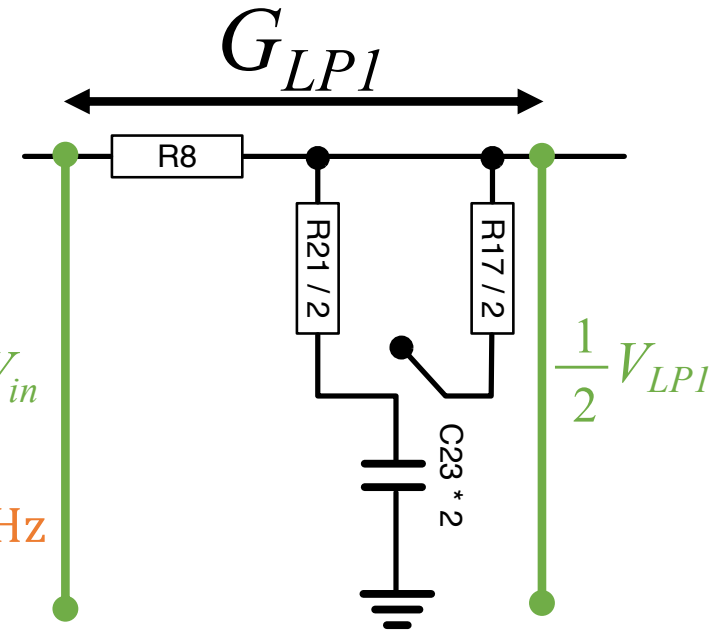

R8 = 16e3	# Ohms
R17 = 3.3e3	# Ohms
R21 = 1e6	# Ohms
C23 = 4.7e-6	# Farads

# I.3 Review of the Circuit: The Low Pass

Low Pass Response,  $V_{LP1} / V_{in}$

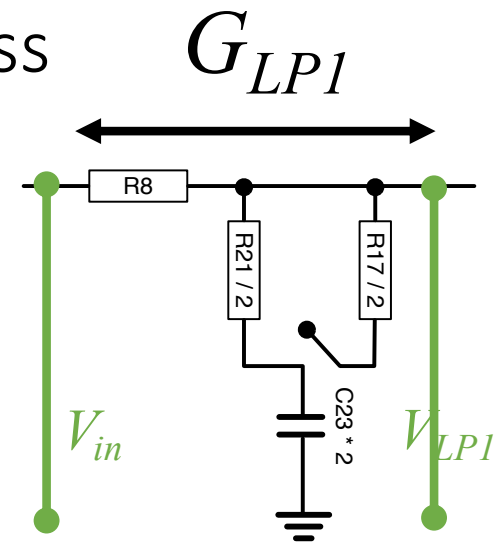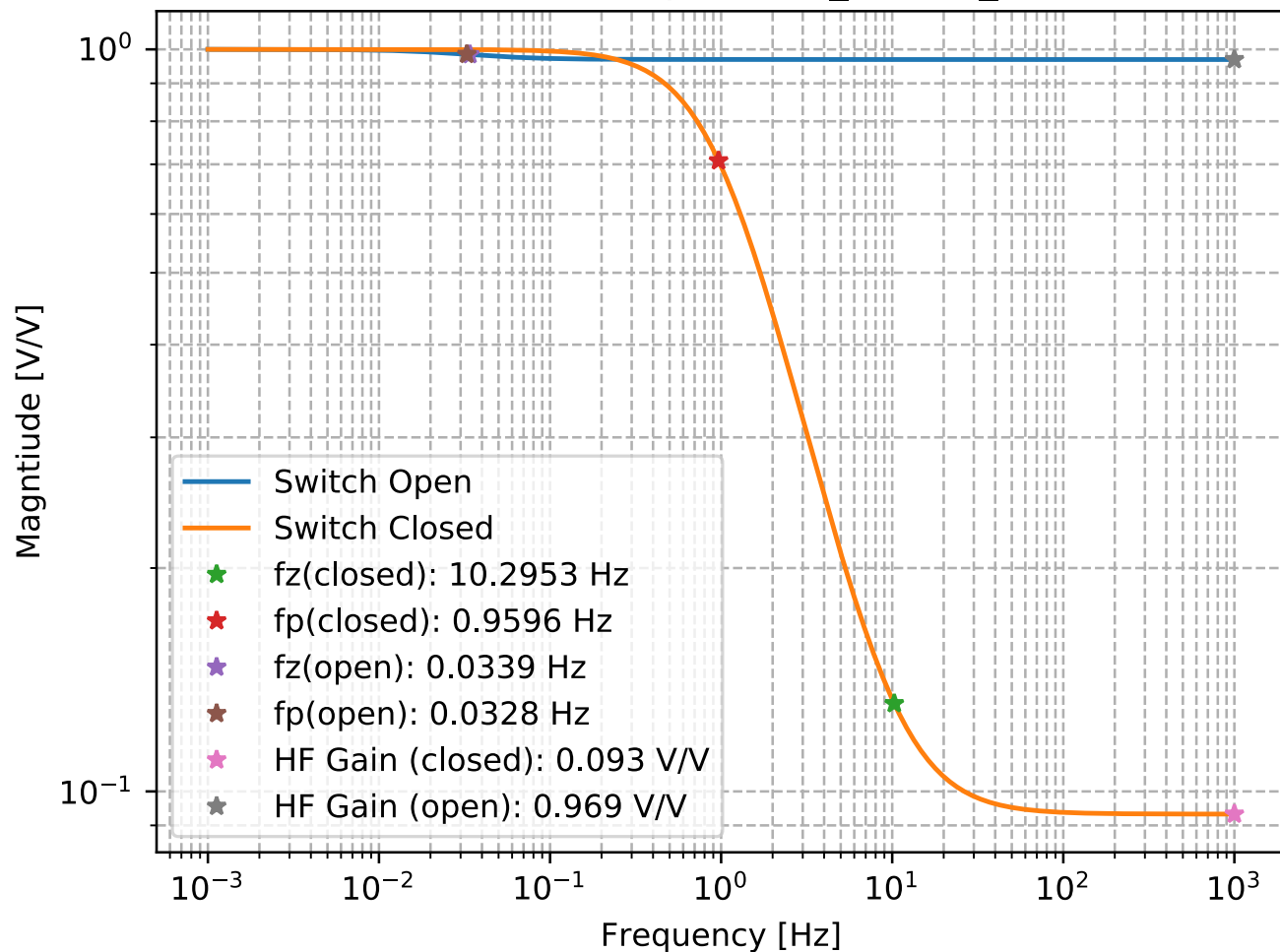

Another analysis trick:  
 the suppression of the low pass (i.e. the asymptotic gain at high frequency) is the ratio of  $f_p / f_z$   
 Also, with the switch open, the pole and zero nearly cancel.





- When the switch is open, each LP stage – above 0.1 Hz – has gain of 0.969 V/V  $\approx$  1 V/V.
- Where we're concerned – above 1 Hz – we can treat this as “just” a part of the overall gain to be measured later, and uninteresting in terms of the frequency response
- **Thus: For State 1 (with no low passes on, all switches open), we can ignore the response of all three low passes.**



# I.3 Review of the Circuit: The Output

On to the response of the amplifier gain and impedance network.

These are important for State 1.

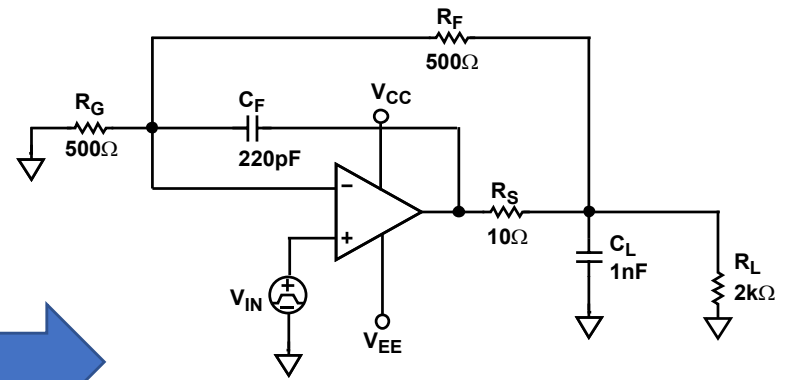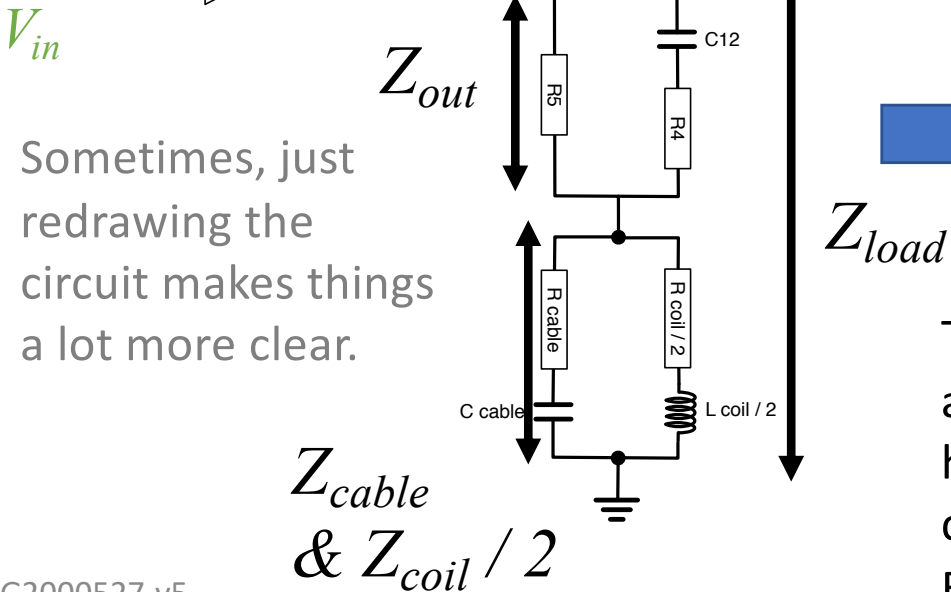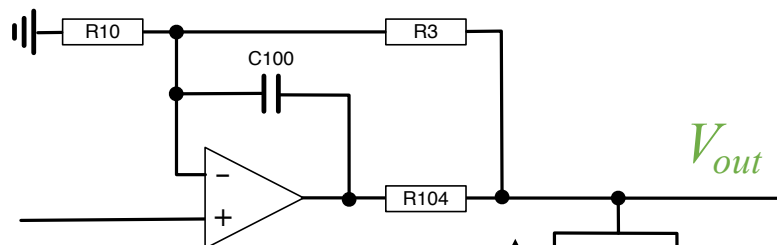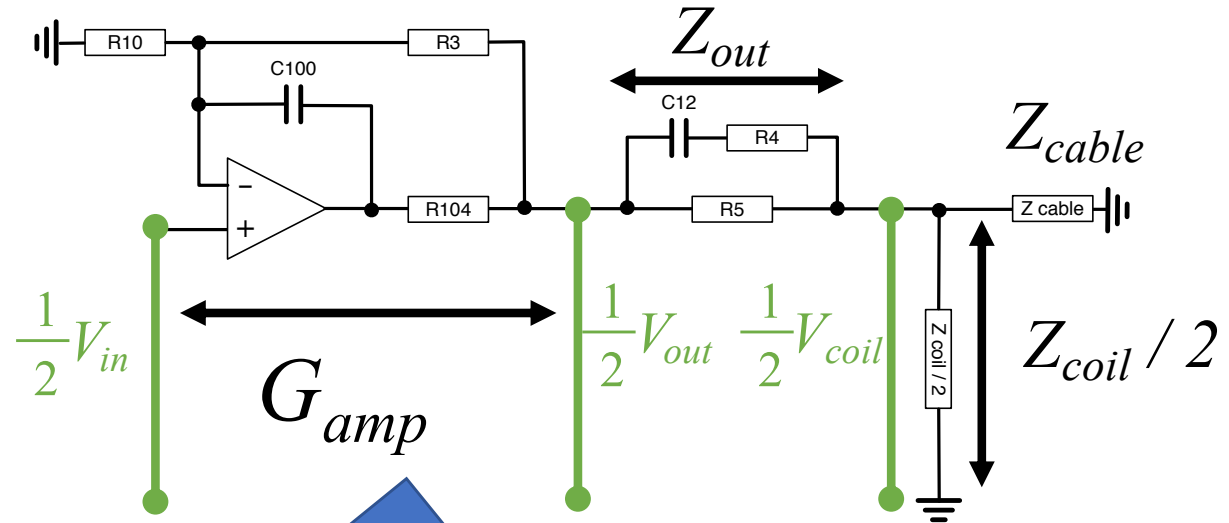

From the AD8671 Data Sheet!

This complicated network can be treated as “just” a non-inverting amplifier, with capacitive load, that has been “in-loop compensated.” More in-loop compensation [here](#).


But, with a “duct tape and bubble gum” story ...
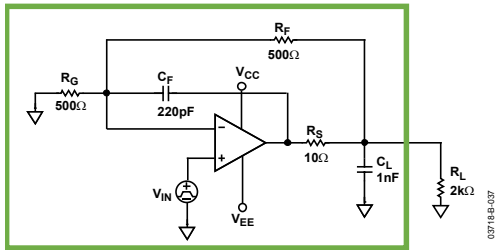
# I.3 Review of the Circuit:




- $R_S = R_{104} = 10$  # Ohm
- $R_F = R_3 = 3.3e3$  # Ohm
- $R_G = R_{10} = 2.2e3$  # Ohm
- $C_F = C_{100} = 0.22e-9$  # Farad
- $C_L = C_{cable} = 1.0e-9$  # Farad
- $R_4 = 750.0$  # Ohm
- " $R_L$ " =  $R_5 = 2.0e3$  # Ohm
- $C_{12} = 0.68e-6$  # Farad

- Use the [AD8671](#), it's a nice, low noise op amp.
- "OK, I'll use the data-sheet-recommended configuration, because the cable run will be pretty long – probably 3 nF of parasitic capacitance. Same component values should be fine."
- Right, but be conscious of the current noise, so make sure  $R_L$  stays big (the BOSEM,  $Z_{coil}$ , should be connected after it), and DAC noise from upstream.
- "OK, cool, a big series resistor \*in the driver circuit\*, prior to the cable load with  $R_5 = 4k$  and increase  $R_F/R_G$  from 1 to 0.33."
- Mmm... but that reduces the actuator range. Can you give me more gain?
- "Sure –let's put in an RC bypass around  $R_L$  to amplify the range at 100 Hz."
- That reduces the protection against current noise, but should still be OK. And also... sorry... we still need [more range](#).
- "OK, dropping  $R_5$  to 2k, and bumping  $R_F/R_G$  up to 0.5."
- **But wait... the circuit isn't really ever capacitively loaded any more... so the this design doesn't make sense with this silly  $R_S$  that makes the circuit confusing to analyze!**



RC bypass  $Im\left\{\frac{1}{i\omega C_{12}}\right\} \ll \frac{R_4 R_5}{(R_4 + R_5)}$   
 by 1 kHz and above,  
 so AD8671, whose  
UGF is ~2-4 MHz with  
 a gain of 2.5, is quite  
 stable.

MOAR gain

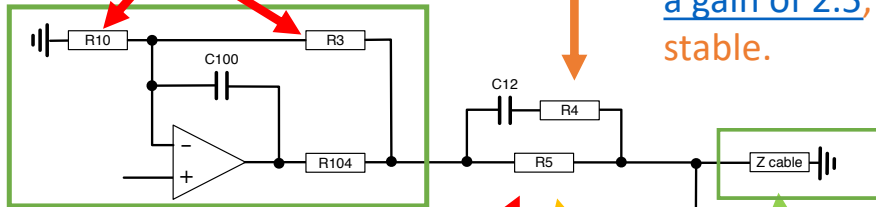

Original non-inverting opamp circuit, in-loop compensated with R104

MOAR gain

Big series resistor

Original cable load that motivated the in-loop compensation design

# I.3 Review of the Circuit: Op-Amp = Just a Gain

So can we just ignore  $R_5 = R104 = 10$  Ohms?



$R3 = 3.3e3$  # Ohm  
 $R10 = 2.2e3$  # Ohm  
 $R104 = 10$  # Ohm  
 $C100 = 220e-12$  # Farad

$$\frac{V_{out}}{V'_{out}} = \frac{R_3}{R_3 + R_{104}} = 0.997$$

YES. R10 is just a tiny voltage drop between  $V_{out}$  and  $V_{out}'$ .

Now, "just" a non-inverting amplifier.

What's the pole frequency?

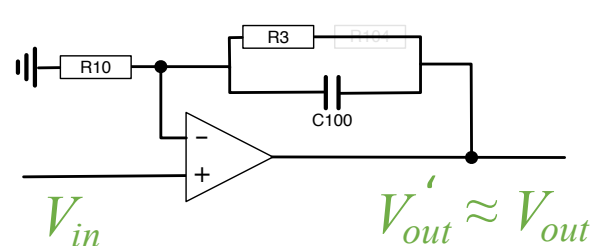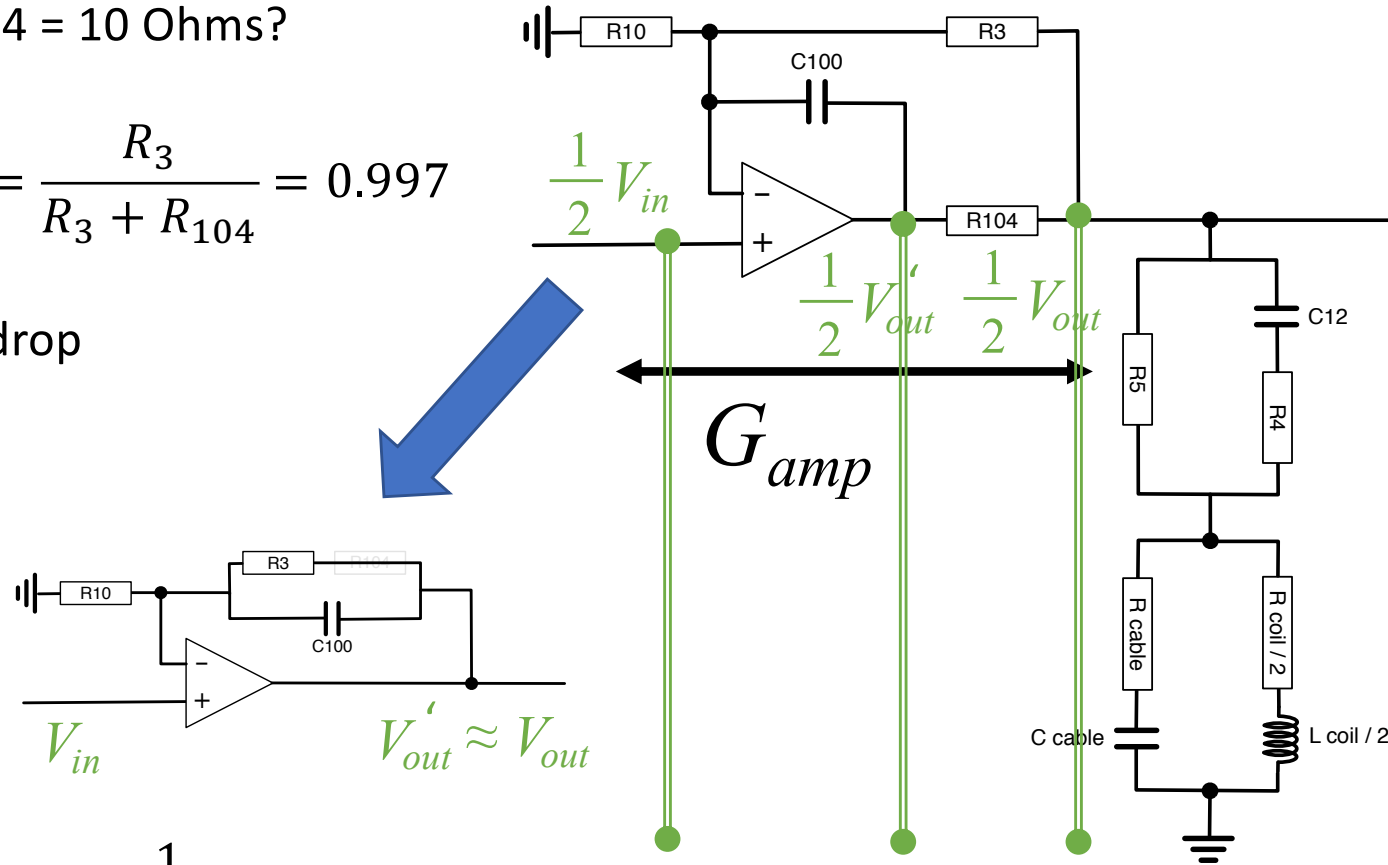

$$Z_{RC} \approx \frac{R_3(1/i\omega C_{100})}{R_3 + 1/i\omega C_{100}} = R_3 \frac{1}{(1 + i\omega R_3 C_{100})}$$

$$G_{amp} \approx \frac{V_{out}}{V_{in}} = 1 + \left(\frac{Z_{RC}}{R_{10}}\right) = 1 + \frac{R_3}{R_{10}} \left(\frac{1}{1 + i\omega R_3 C_{100}}\right)$$

$$G_{amp} \Big|_{DC} = 1 + \frac{R_3}{R_{10}} = 2.5$$

$$f_p^{RC} = 1/(2\pi R_3 C_{100}) = 219.2 \text{ kHz}$$

219 kHz is sufficiently high frequency that we can ignore this pole too.

So, YES, ignore **R104** and **C100**.

$G_{amp}$  for us is just 2.5.

This won't be a part of the State 1 response either

# I.3 Review of the Circuit: Output Zs: Rs, Ls, and Cs

Let's look at the load impedance.

We'll find out here's from where **\*all\*** the response from State 1 comes.

$$Z_{out} = \frac{R_5(R_4 + 1/i\omega C_{12})}{R_5 + (R_4 + 1/i\omega C_{12})} = R_5 \left( \frac{1 + i\omega R_4 C_{12}}{1 + i\omega(R_4 + R_5)C_{12}} \right)$$

$$f_z^{out} = 1/(2\pi R_4 C_{12}) = 312.069 \text{ Hz}$$

$$f_p^{out} = 1/(2\pi(R_4 + R_5)C_{12}) = 85.110 \text{ Hz}$$

$$Z_{coil} = \frac{1}{2}(R_{coil} + i\omega L_{coil}) = \frac{R_{coil}}{2}(1 + i\omega(L_{coil}/R_{coil}))$$

$$f_z^{coil} = 1/(2\pi L_{coil}/R_{coil}) = 571.085 \text{ Hz}$$


$$Z_{RLC} = Z_{coil} \parallel Z_{cable}$$

$$= \frac{1}{2}R_{coil} \frac{(1 + i\omega[L_{coil}/R_{coil}])(1 + i\omega R_{cable}C_{cable})}{(1 + i\omega(2R_{cable} + R_{coil})C_{cable} - (1/2)\omega^2 L_{coil}C_{cable})}$$





$$f_z^{coil} = 1/(2\pi L_{coil}/R_{coil}) = 571.085 \text{ Hz}$$

$$f_z^{cable} = 1/(2\pi R_{cable}C_{cable}) = 2.27 \text{ MHz}$$

$$f_p^{coil||cable} = 1/(2\pi) \sqrt{\frac{1}{(1/2)L_{coil}C_{cable}} - \left(\frac{2R_{cable} + R_{coil}}{(1/2)L_{coil}}\right)^2} = 65.063 \text{ kHz}$$

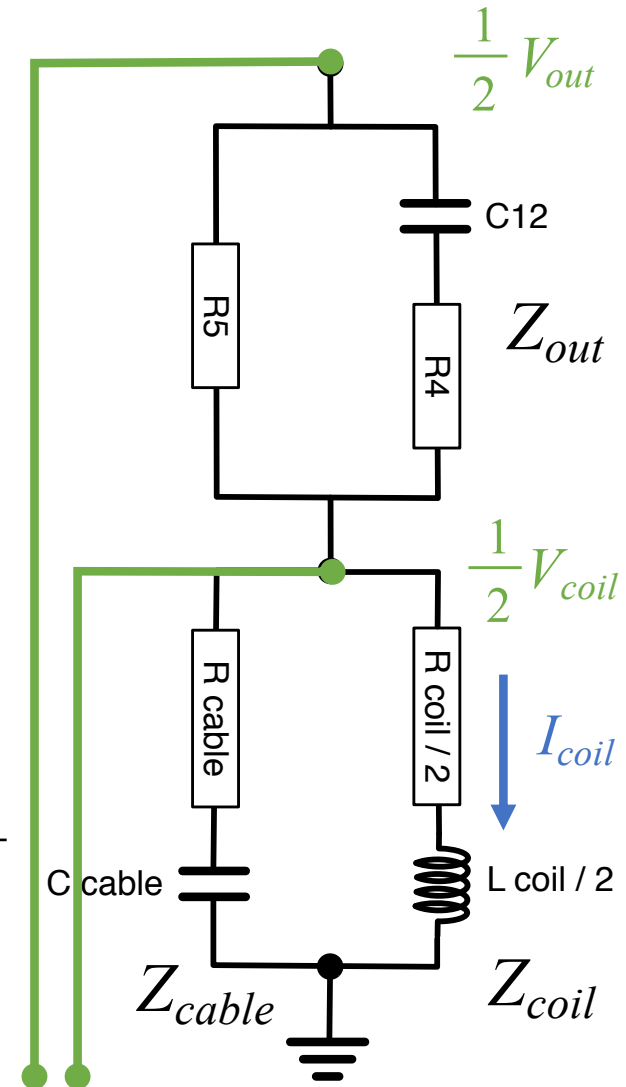

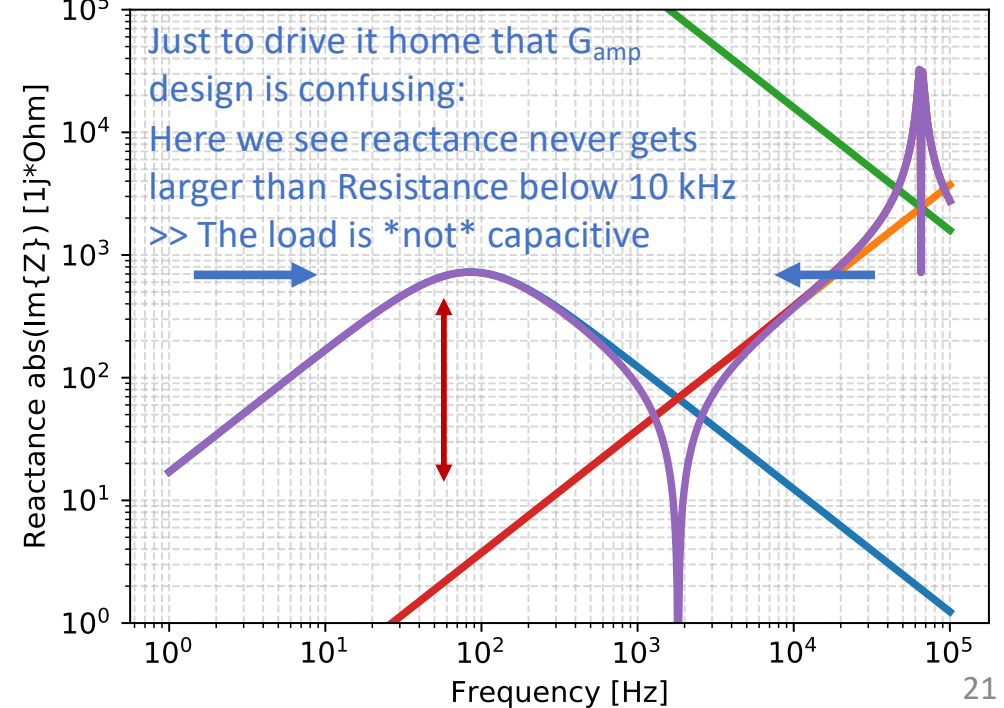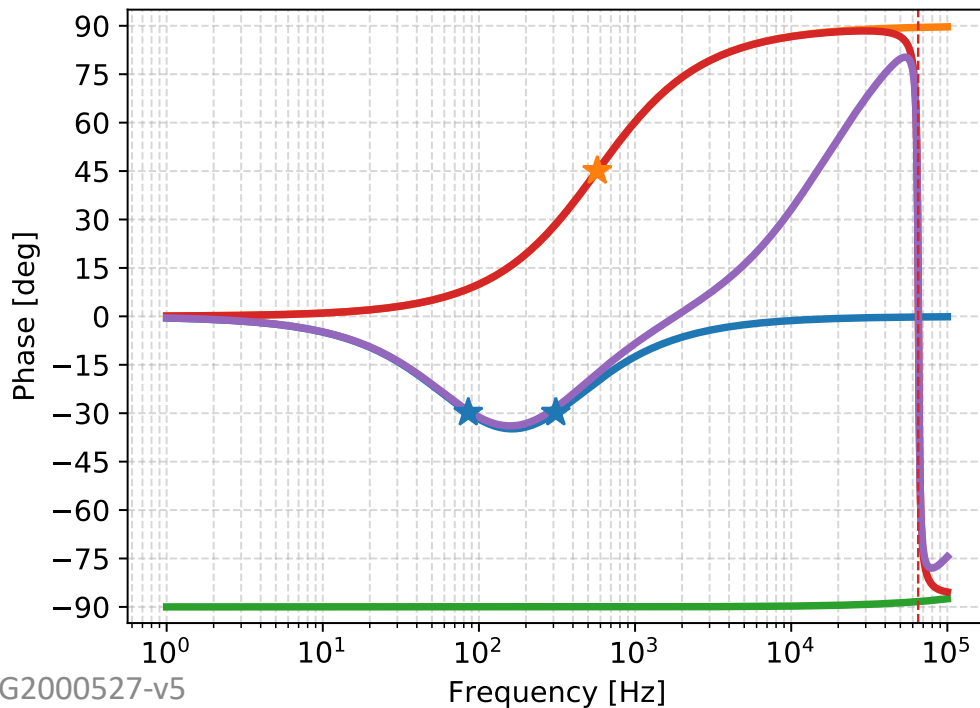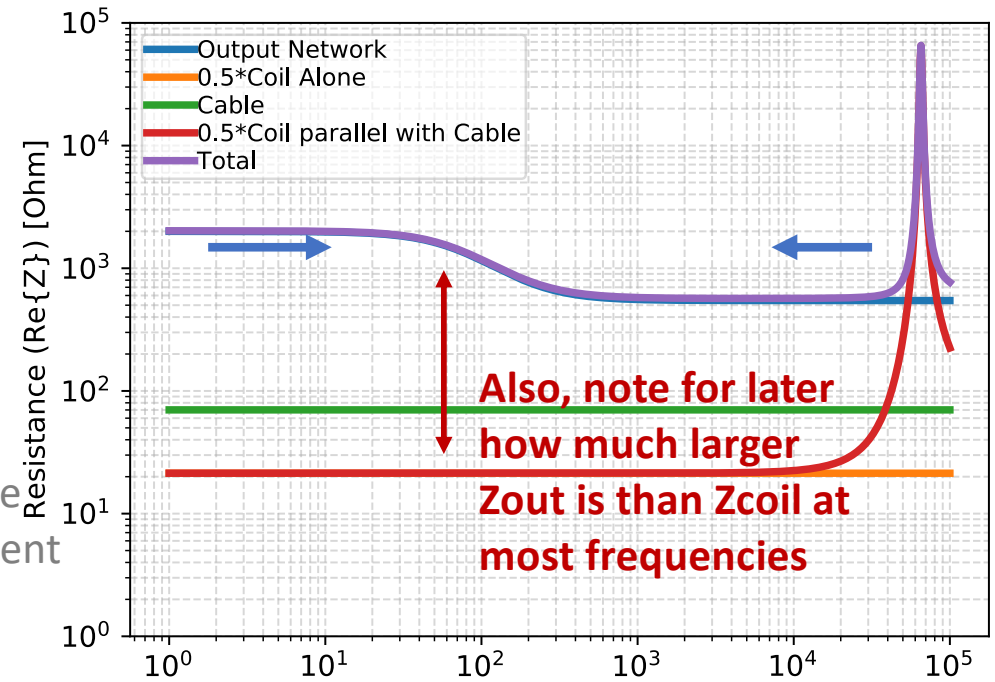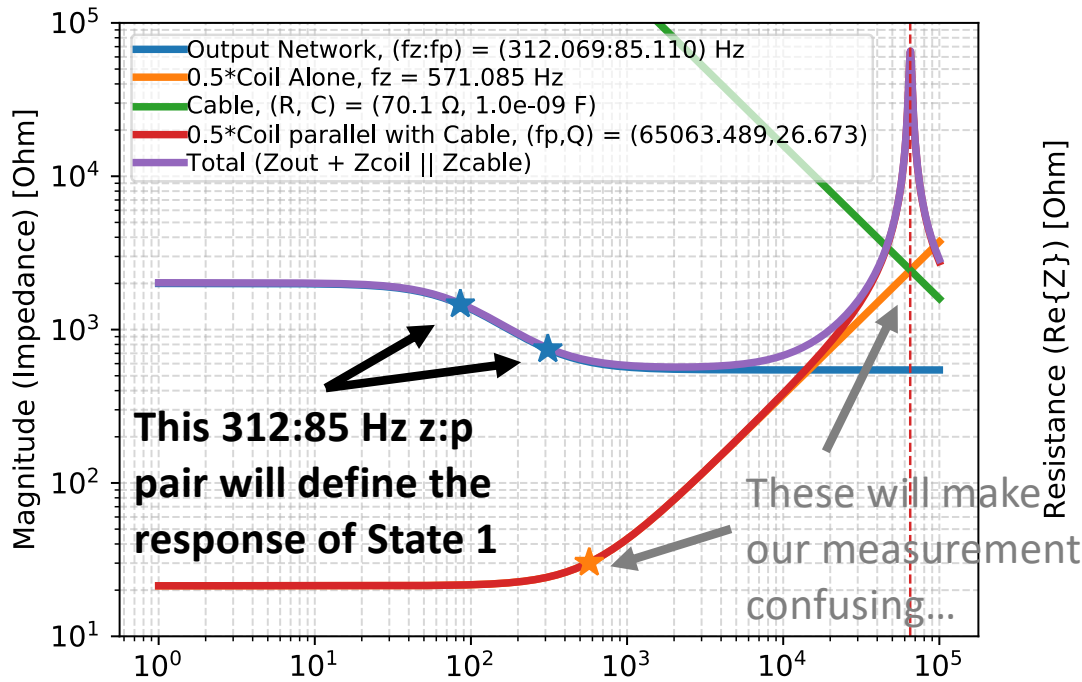
# I.3 Review of the Circuit: $Z_{total}$ : poles and zeros


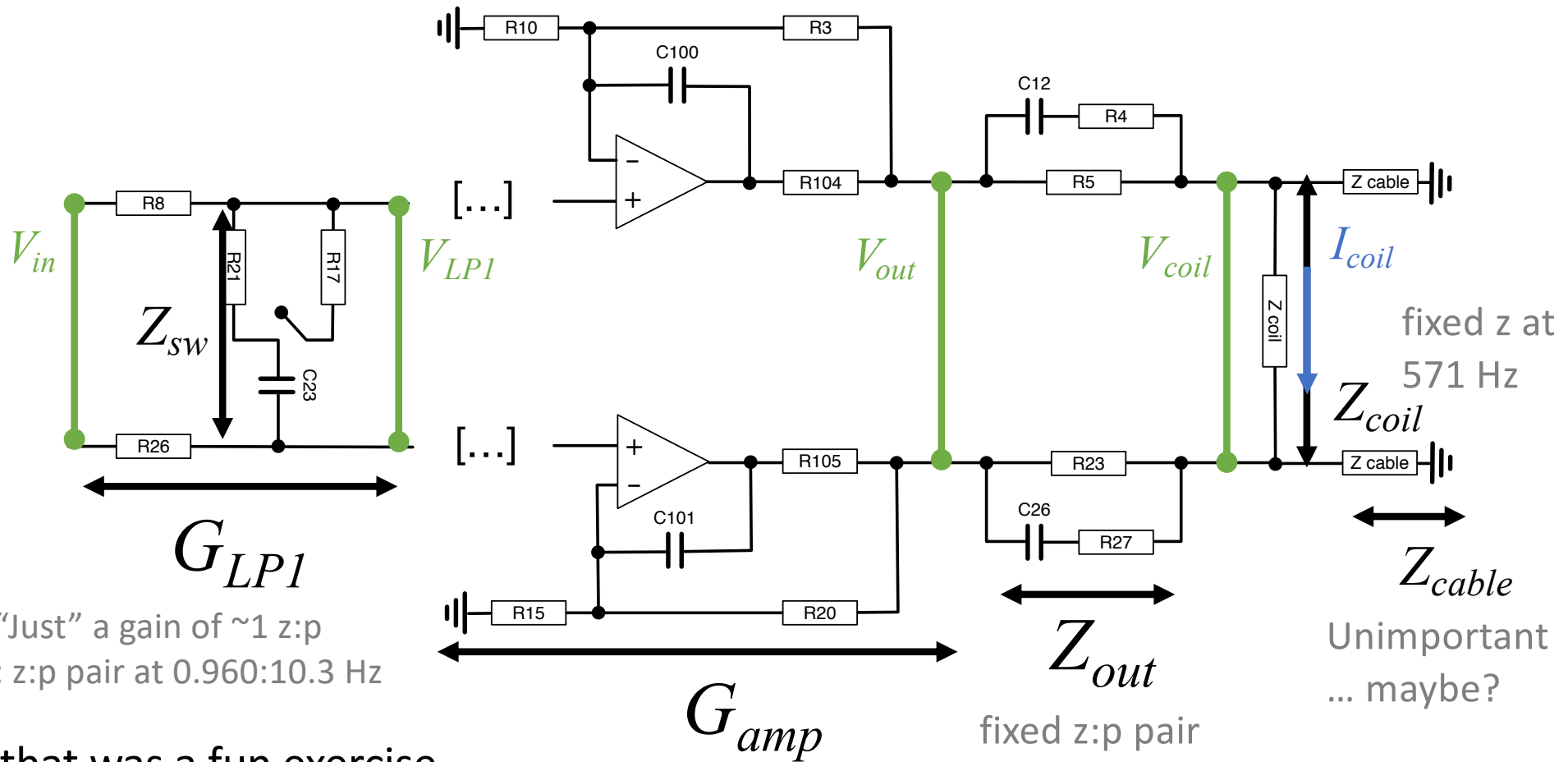
# I.3 Review of the Circuit: OK, Let's Review

OK, now that we know what kind of response to expect from everything, we can head back to the differential picture and summarize.



Open: "Just" a gain of  $\sim 1$  z:p  
 Closed: z:p pair at 0.960:10.3 Hz

Well, that was a fun exercise.  
 But what do we really want?

**The response of the current created across the coil,  $I_{coil}$  to  $V_{in}$ .**  
**So let's talk about how to measure it.**

"Just" a gain of 2.5.

fixed z:p pair  
 at 312:85 Hz

Unimportant  
 ... maybe?

# Outline


Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
- 4. The Measurement**
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{\text{UIM}}$
8. Converting sys error in  $A_{\text{UIM}}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# I.4 The Measurement: Coil Current/Vout

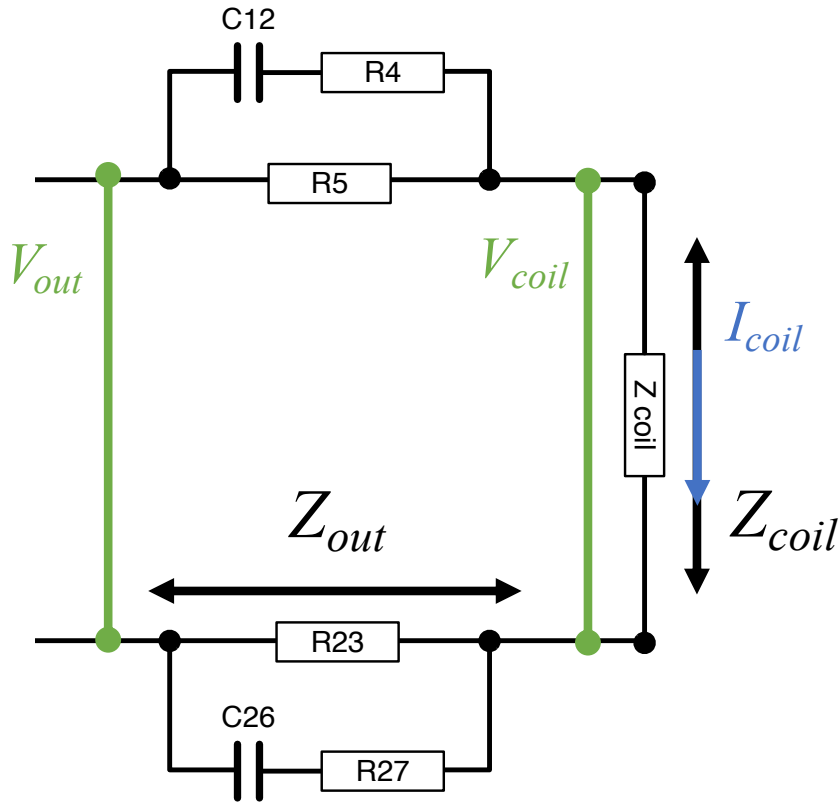

We calculated that whatever the values of  $R_{cable}$  and  $C_{cable}$  are, they're not going to matter until several 10s of kHz. So let's make it easy to think about.

In **State 1**, we already know,  $V_{out}/V_{in}$  is “just a gain” at  $\sim 2.5$ . So the current, held fixed by the  $G_{amp}$  opamps, will just obey Ohms Law as it heads out to the coil and back across the differential connection to the coil:

$$V_{out} = I_{coil} Z_{total} = I_{coil} (2Z_{out} + Z_{coil})$$

$$\frac{I_{coil}}{V_{out}} = \frac{1}{(2Z_{out} + Z_{coil})}$$

And, we know for State 1, that means,

$$\left. \frac{I_{coil}}{V_{in}} \right|_{State\ 1} \approx \frac{2.5}{(2Z_{out} + Z_{coil})}$$

So let's look at that response, with our basic analytic model.





# I.4 The Measurement: Coil Current / Vout

$$I_{coil} / V_{out} = 1 / (2Z_{out} + Z_{coil})$$

Ah – OK, since  
 $abs(2 Z_{out}) \gg abs(Z_{coil})$   
 (from slide 17)

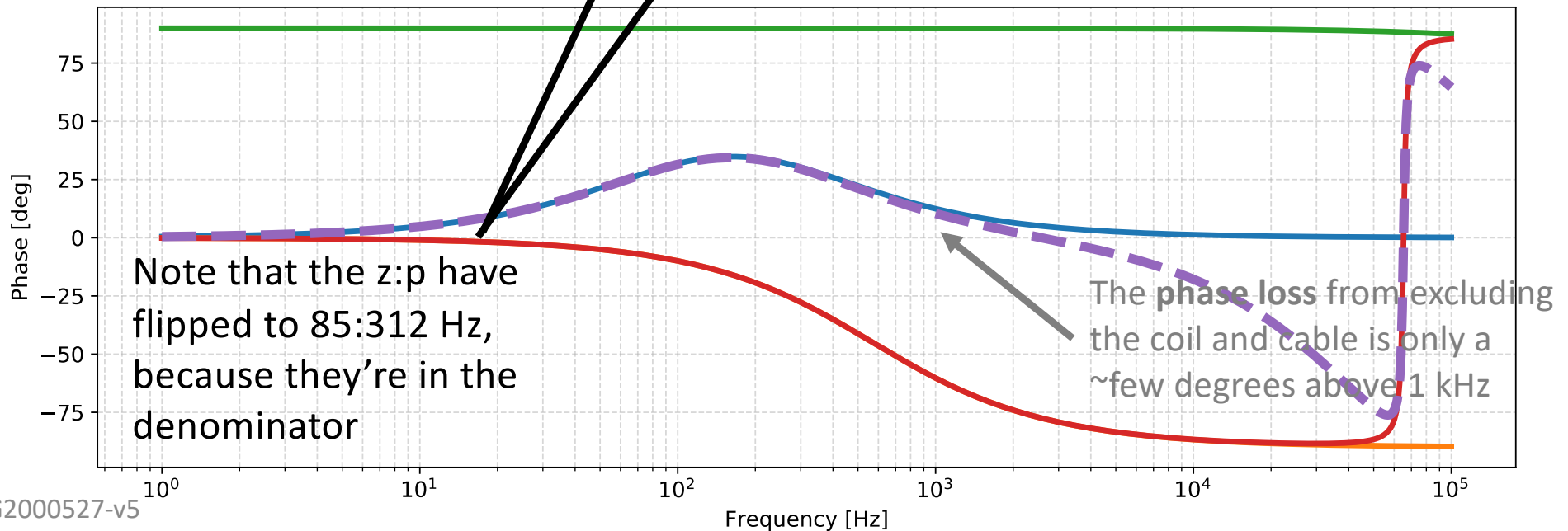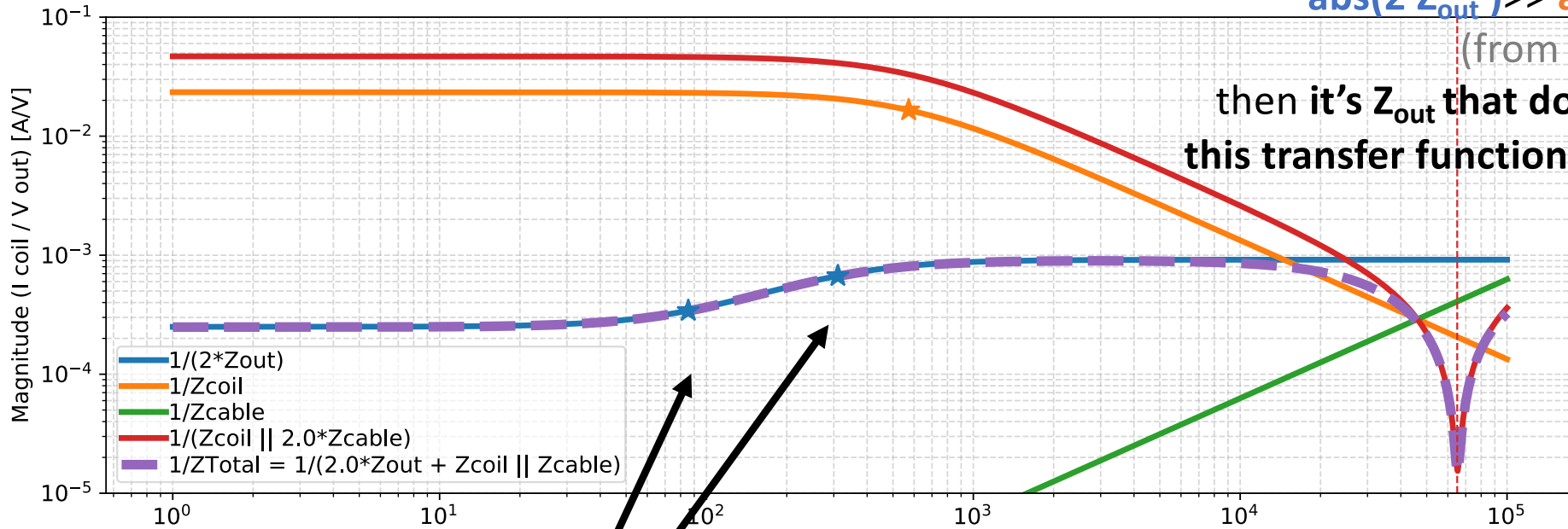
then it's  $Z_{out}$  that dominates  
 this transfer function out to a  
 few kHz


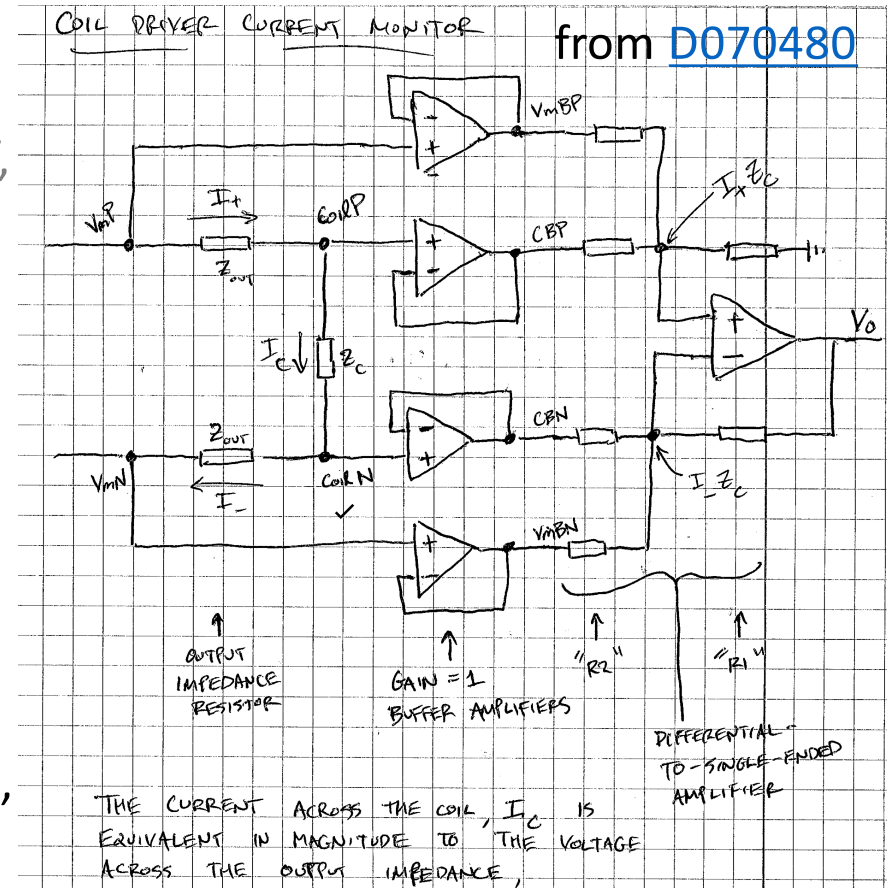
# I.4 The Measurement: Fast Current Monitor?

Why do we have to physically measure the transfer function in analog? Why not use the fast current monitor?

- The answer does include the output impedance network for this driver (contrary to popular belief, started by 2014 Jeff)
- BUT -- the fast current monitor board itself may contribute some frequency dependence, and there's an AA chassis between the analog IMON signal and where it's read in by the DAQ. **These responses will confuse fitting routines and/or your interpretation of the results.**
- It works well for \*ratios\* of measurements, namely to get poles and zeros from things that \*change\* between states (i.e. the low pass filters), but it does not help you characterize State 1.
- We typically operate in state 1, and at least the AA chassis has appreciable response in frequency bands of interest to us, so ...
- Analog measurement it is.




$$\frac{V_0}{I_C} = 2 Z_{out} \frac{R_1}{R_2}$$
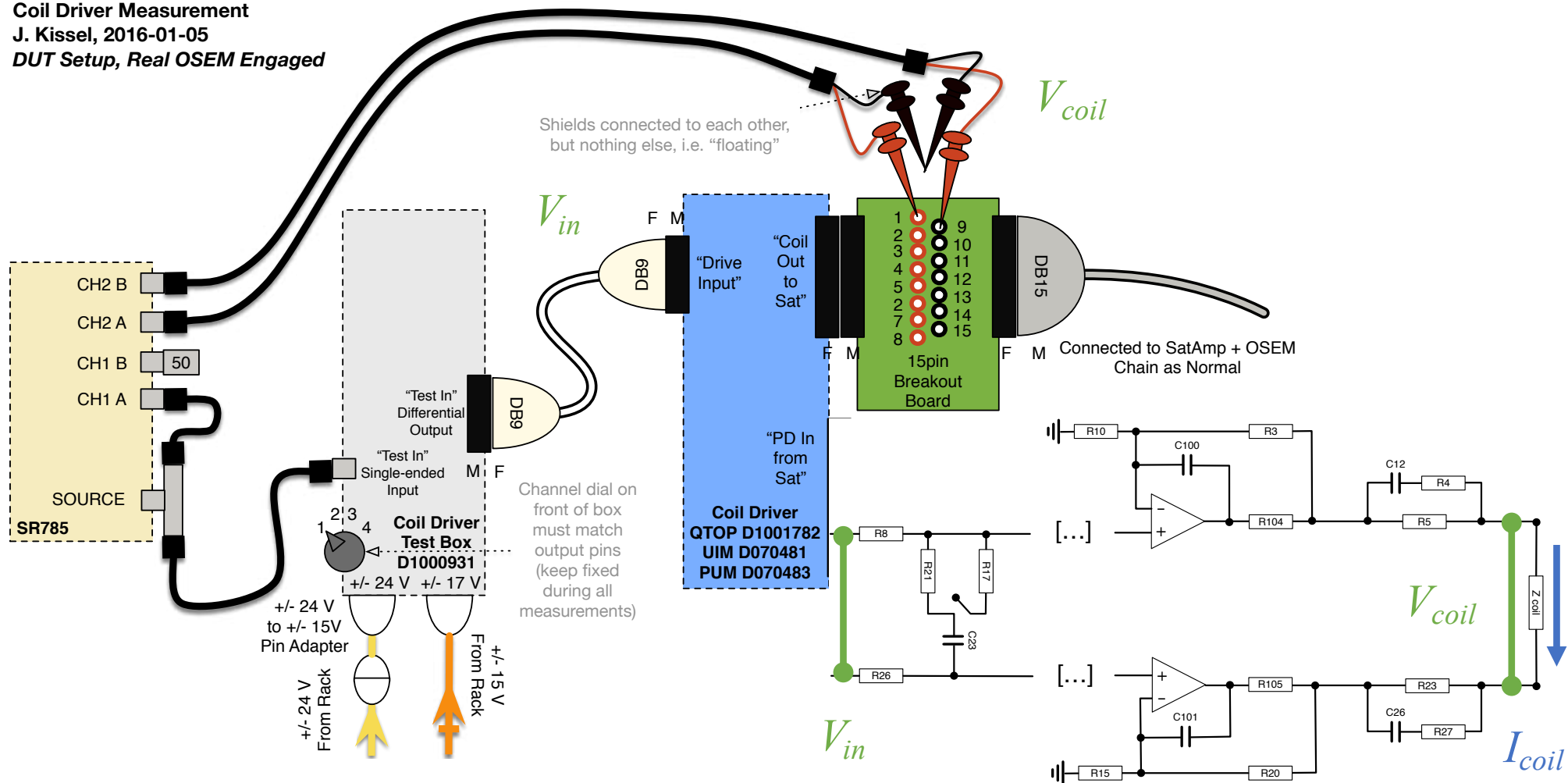
# I.4 The Measurement: should / Would / Could...

OK Great! Gung-ho Jeff will go out there, he'll take some clip leads, a differential driver, and breakout boards, to measure at the output of the driver – but leaving output connected to the OSEM as normal, “because you need the current to go across the output legs” – the op-amps need to be loaded with \*something,\* so might as well make it “as accurate as possible.”

**Coil Driver Measurement**  
 J. Kissel, 2016-01-05  
 DUT Setup, Real OSEM Engaged



# I.4 The Measurement: Facepalm!

But wait – if you’ve left the coil connect “as normal” then you’re not going to measure...

$$\left. \frac{I_{coil}}{V_{in}} \right|_1 \approx \frac{2.5}{(2Z_{out} + Z_{coil})}$$

But instead...


$$V_{coil} = I_{coil} Z_{coil}$$

$$\left. \frac{V_{coil}}{V_{in}} \right|_1 \approx \frac{2.5 Z_{coil}}{(2Z_{out} + Z_{coil})}$$

$$f_z^{coil} = 1/(2\pi L_{coil}/R_{coil}) = 571.085 \text{ Hz}$$

$$f_p^{out} = 1/(2\pi R_4 C_{12}) = 312.069 \text{ Hz}$$
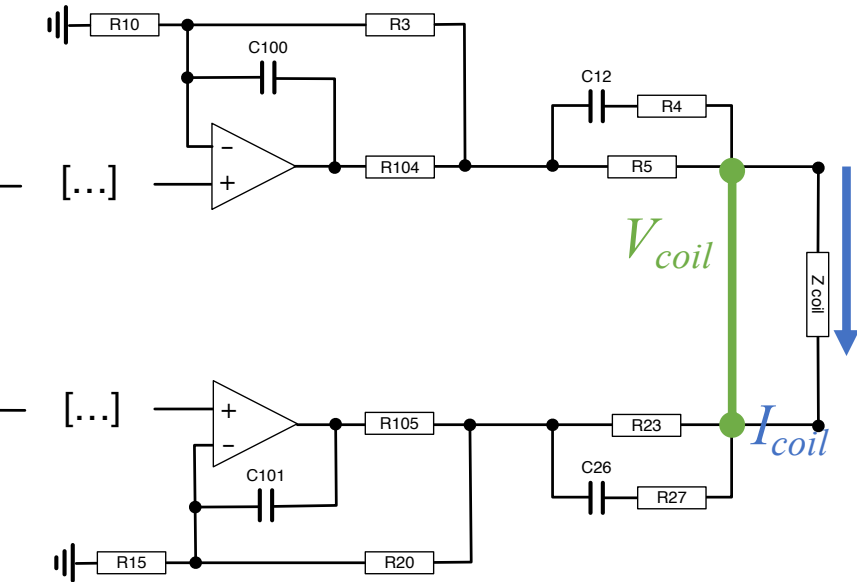
$$f_z^{out} = 1/(2\pi (R_4 + R_5) C_{12}) = 85.110 \text{ Hz}$$





flipped because Zout is in the denominator

Which means you’re going to be confused for months – YEARS – by your results, until you write this presentation!
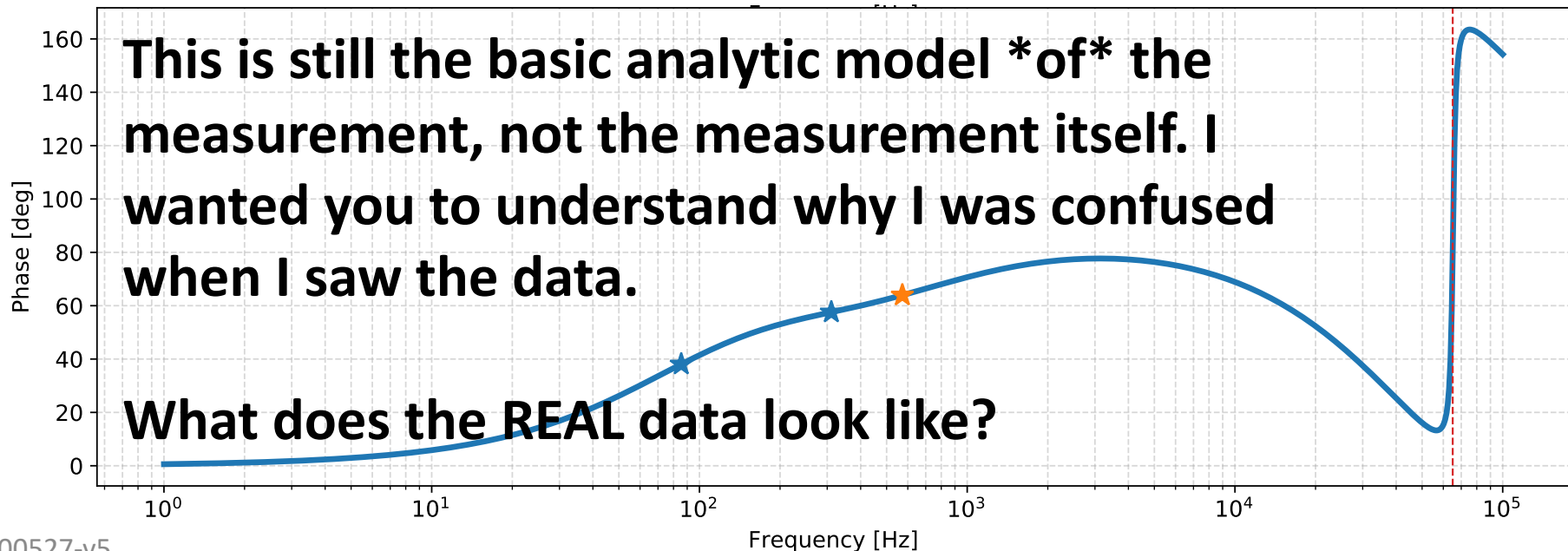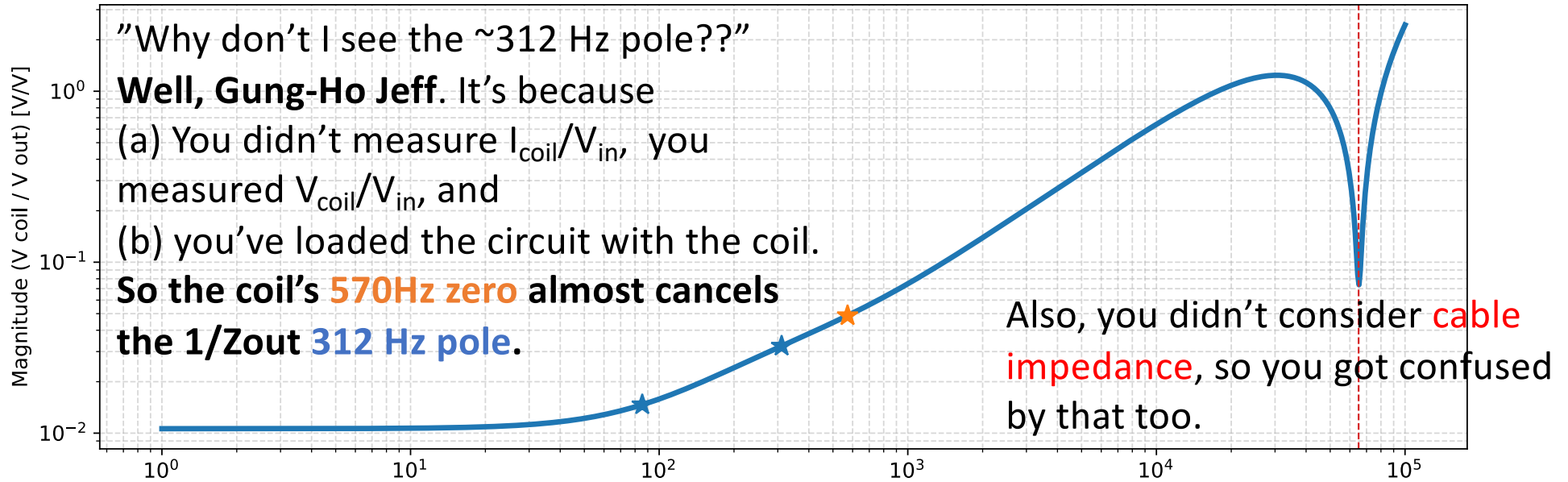
# I.4 The Measurement: “missing” pole, *really* solved.

$$V_{coil}/V_{in} \approx Z_{coil}/(2Z_{out} + Z_{coil})$$




# I.4 The Measurement: What we really did...





**But wait ... it gets worse.** To quote [\[LHO:46927\]](#):

“This time (unlike the 2016 attempt; with measurement as shown on the last slide, as in [\[LHO:24725\]](#)) we tried to cut corners by only driving the coil drivers with single-ended input directly from the SR785 -- so we can avoid having to characterize the details of the differential driver box that has been used previously. This failed, causing (what we believe to be saturations) of the coil driver electronics and wonky unphysical\*\*\* transfer functions.”

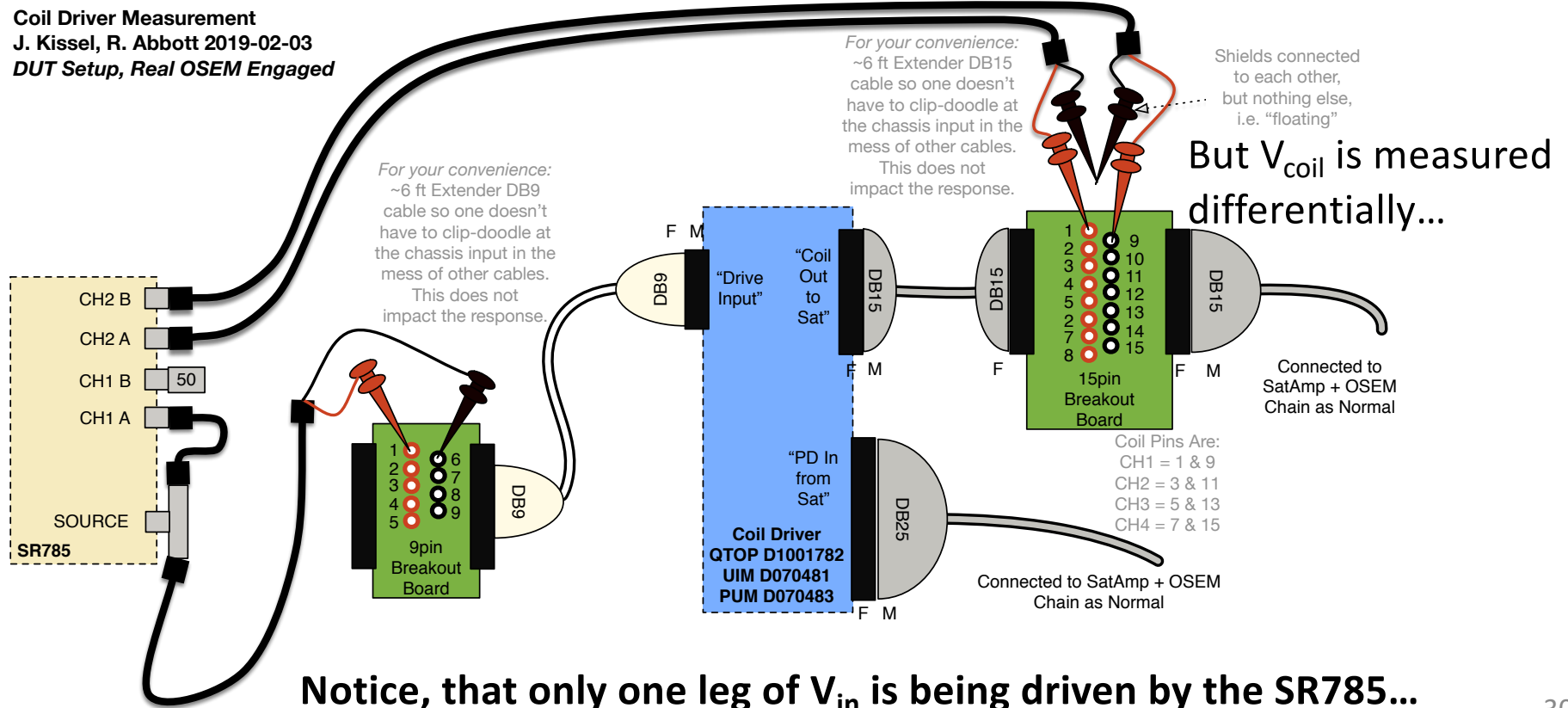The joys of that Sunday measurement you think will work to save you time...


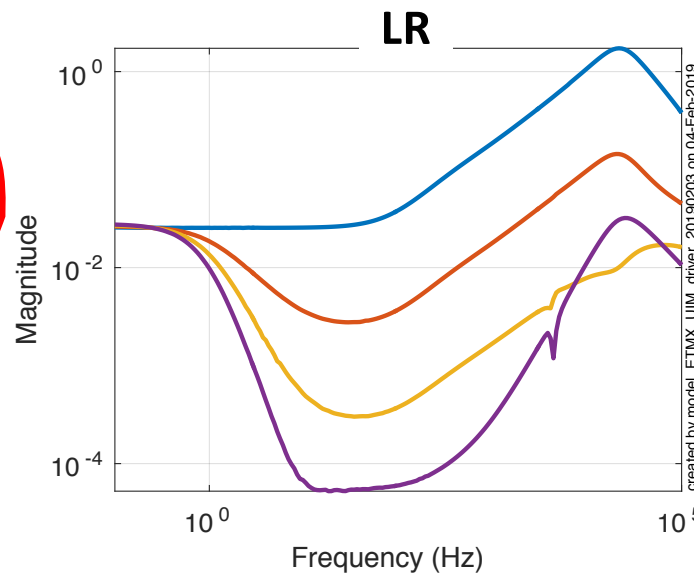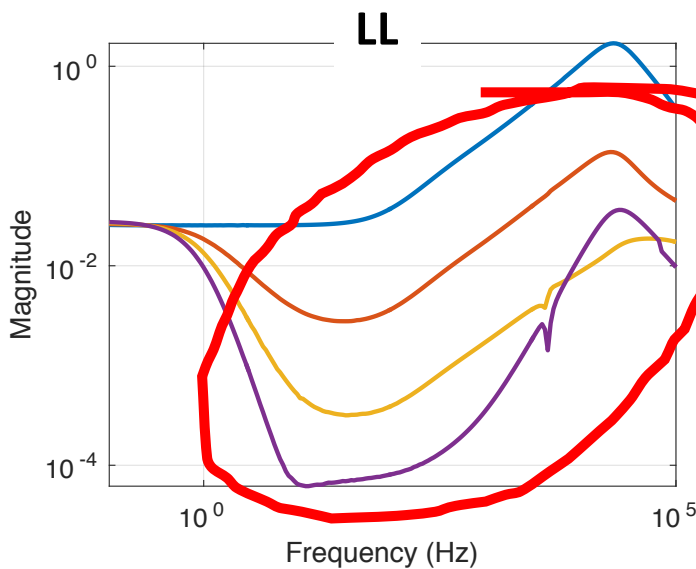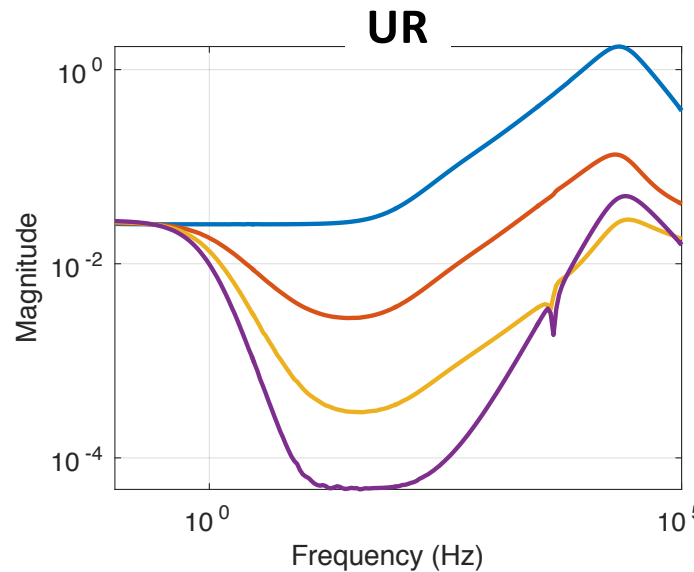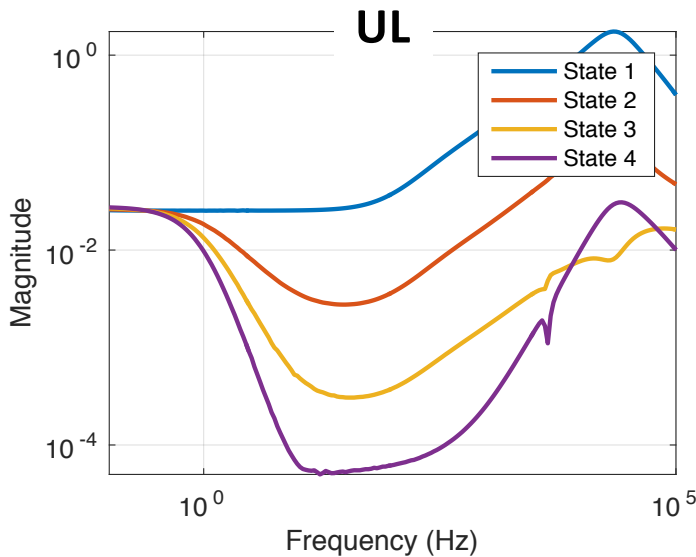
# I.4 The Measurement: \*\*\* wonky, unphysical TFs



Even plotted the results 2019-02-03 results the next day (see [\[LHO:46773\]](#)).  
Even apologizes for the lack of tick marks.

Sure, it looks like there's "there's no 300 Hz pole," but we now understand that.

Further, it looks like, for at least State 2, the  $z:p = 10.5:0.95$  Hz low pass shows up, good...


But look at how the **magnitude gets distorted** at (let's say 500 Hz) and above in States 3 and 4...

[^/trunk/Common/Electronics/H1/Data/SUSElectronics/ETMX/UIM/2019-02-03/2019-02-03\\_UIMdriver\\_measurementnotes.txt](#)

**But ... this is the data we have. Maybe we can salvage the data for States 1 and 2?** 31

# I.4 The Measurement: Finally, The Data.
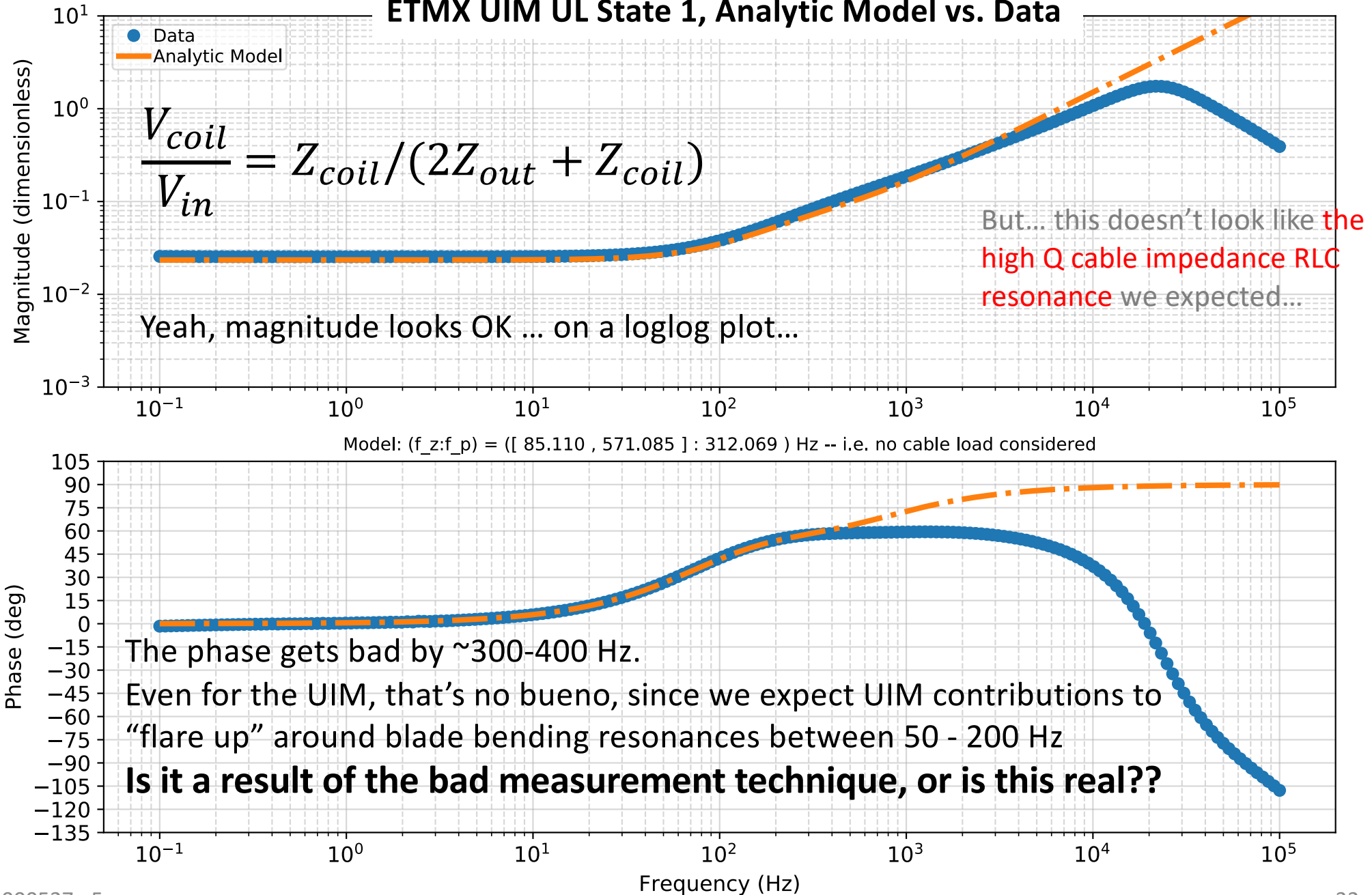
### ETMX UIM UL State 1, Analytic Model vs. Data





# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement
- 5. Other models of the circuit**
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{UIM}$
8. Converting sys error in  $A_{UIM}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# 1.5 Other Models of the Circuit

- **What if we use a more sophisticated model? Can we predict this deviation?** There are lots of more sophisticated modelling tools for circuits out there, LISO, Spice, Altium, etc.
- Chris Wipf put together a [LISO](https://svn.ligo.caltech.edu/svn/aligonoisebudget/trunk/Dev/SusElectronics/LISO/QUAD/UIM) model of the UIM circuit in the Noise Budget SVN,
  - <https://svn.ligo.caltech.edu/svn/aligonoisebudget/trunk/Dev/SusElectronics/LISO/QUAD/UIM>
  - Note that, unfortunately, the LISO models Chris ran didn't export poles and zeros, we so don't have them (we'll find later that re-running to get them won't be worth it)
- It will be instructive to show that model too, especially because
  - More models = more understanding
  - More poles and zeros will appear from the fit than we predict from the analytic model,
  - The LISO model doesn't make approximations for clarity, and
  - The parameters of the cable and coil load are (apparently) quite uncertain

**But, also, let's just fit the data.**

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement This parts a four-sub-part doooosey
5. Other models of the circuit
- 6. The Fit and Each Coil Result**
7. Converting fit results in to systematic error in  $A_{UIM}$
8. Converting sys error in  $A_{UIM}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# I.6.1 The Fit: IIR Rational is Awesome


- Most transfer function software is unruly: if you don't understand what your data is, or the quality of the data, you're going to have a tough time tailoring the tool to suit your needs, and/or understanding the results.
- A 2016 call to action, [G1601173](#), inspired Lee McCuller to develop [IIRrational](#)v2. I've found it to work excellently, with minimal input.
- The script to run the fit lives here:
- [^/trunk/Common/Electronics/H1/Scripts/fit\\_ETMX\\_UIM\\_driver\\_20190203\\_IIRrational\\_20200401.py](#)
- Here's my environment that I used to get it to work (determined using [^/trunk/Common/Misc/Scripts/versioncheck.py](#) the output of which is quoted here):

```
This is Python version:  
3.7.4 (default, Aug 13 2019, 15:17:50)  
[Clang 4.0.1 (tags/RELEASE_401/final)]
```

If you import the following packages, you will get the versions listed below:

```
matplotlib.__version__ = 3.1.1  
numpy.__version__ = 1.17.2  
scipy.__version__ = 1.3.1  
sklearn.__version__ = 0.21.3  
gwpy.__version__ = 1.0.1  
nds2.__version__ = 0.16.5  
IIRrational.__version__ = 2.0.11  
h5py.__version__ = 2.9.0  
emcee.__version__ = 3.0.2  
corner.__version__ = 2.0.1
```
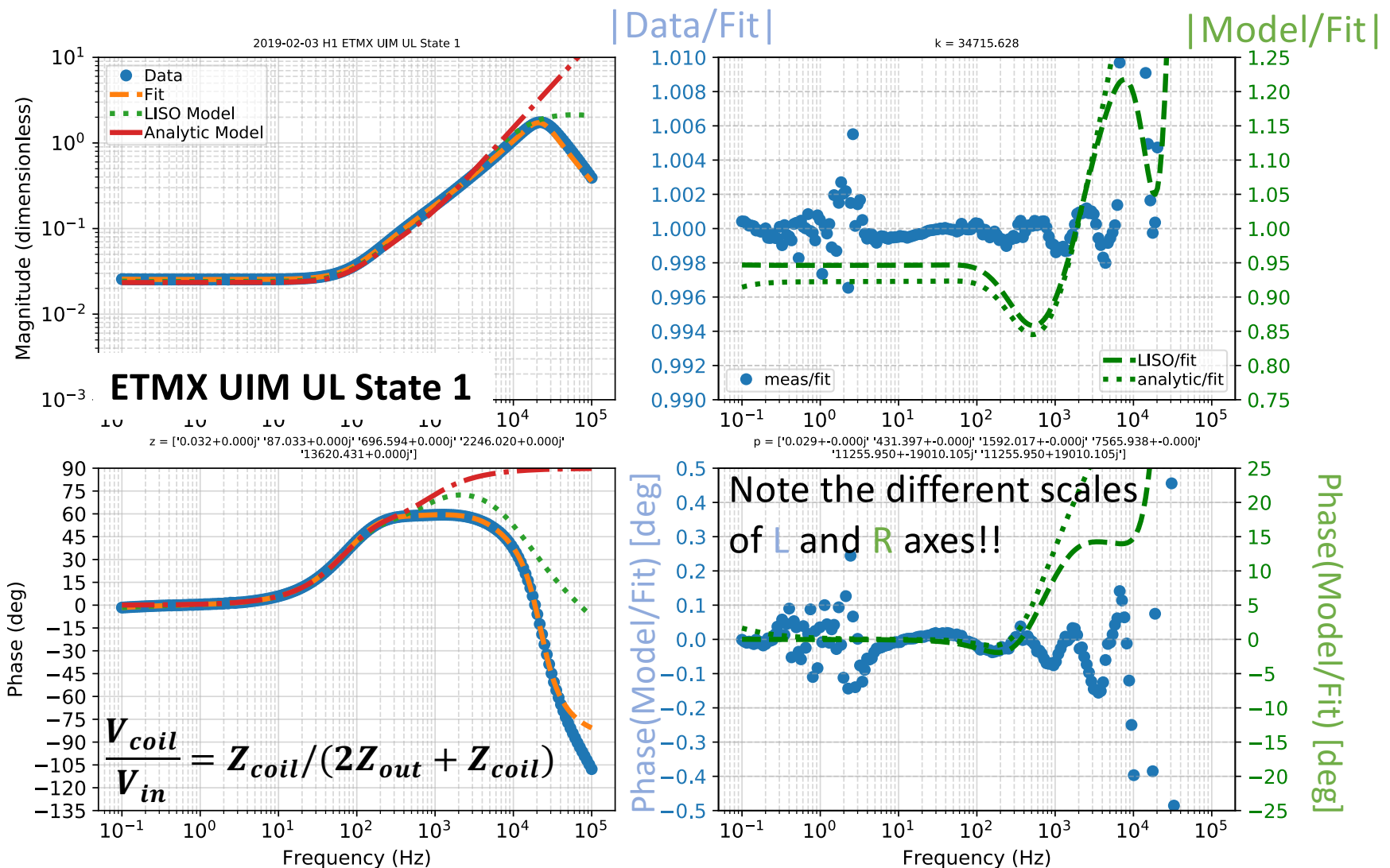
# I.6.1 The Fit Results Per Coil: Intro to Plot



- The **basic analytic model** is as bad as we know from slide 27 (residual shown in **dotted green**)
- The **LISO model** seems to miss the basic RC and Coil pole and zero frequencies, resulting in magnitude error of ~15% by 300 Hz, and also bad in phase (residual, in **dashed green**, is 10 deg by 1 kHz).
- The **IIR rational fit** is excellent, all the way out to 10 kHz. But ... let's look at all the poles and



# 1.6.1 Fit per Coil: State 1 Results Interpretation

Again, understand the fit results is an important part of the game:


- Do zeros and poles make sense?
- Are there more than you expect?
- Are results consistent across several coils?
- Can we ignore any?

Take UL for example:
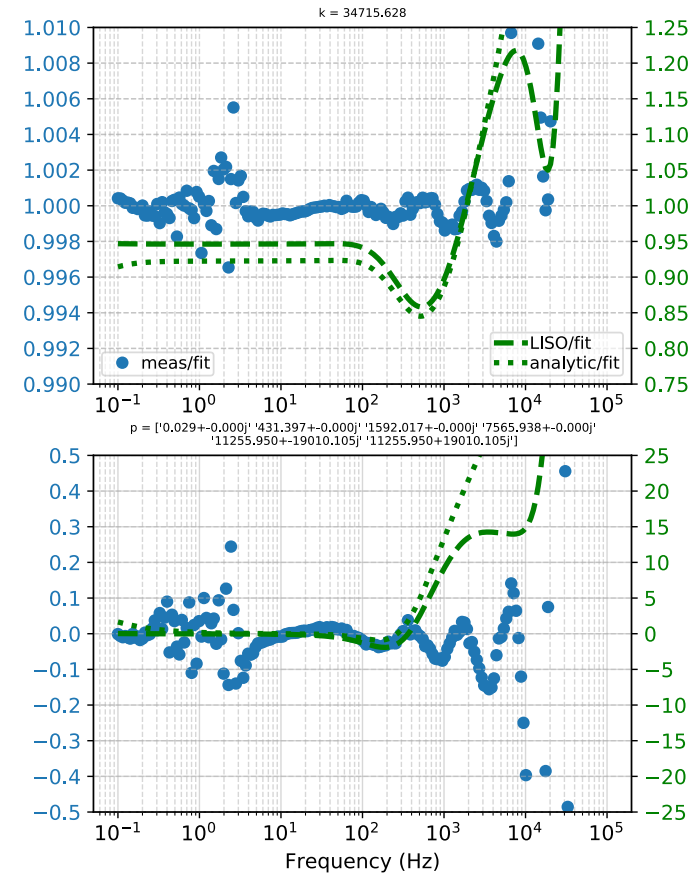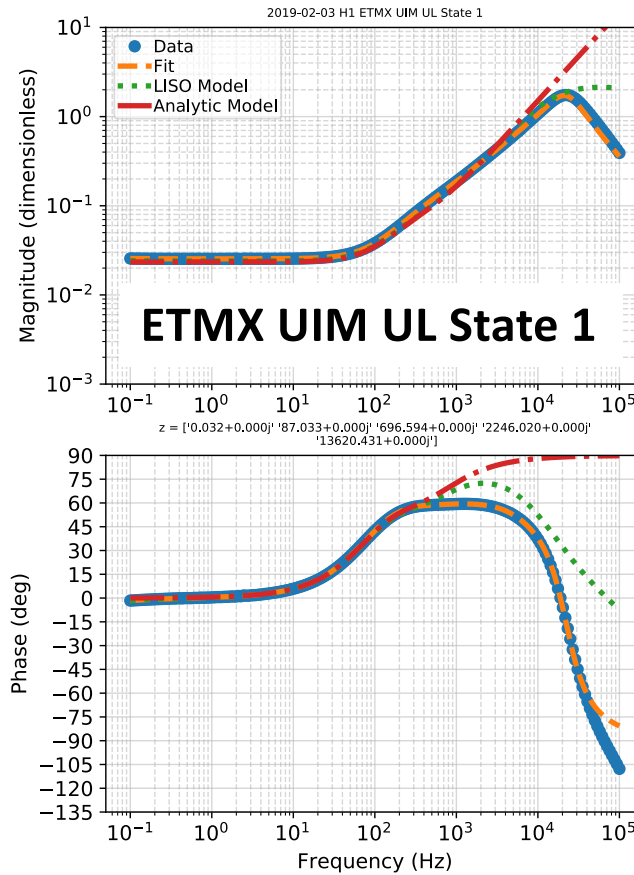
$$\frac{V_{coil}}{V_{in}} = Z_{coil} / (2Z_{out} + Z_{coil})$$



Circuit Feature Assignment	UL Fit Zeros	UL Fit Poles
Coil Impedance	696.5942 Hz	
RC Network	87.0329 Hz	431.3965 Hz
SW Closed LP	0.0325 Hz	0.0293 Hz
?????	2246.0201 Hz	1592.0174
Cable impedance?		pair(22092.54 Hz, 59.37 deg)

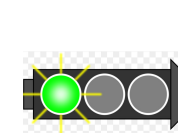

$f_z$  or  $f_p$ , or combo is right about where we expect. Or the  $f_z:f_p$  is close enough to “canceling” to ignore  $f_z$  or  $f_p$  is probably from feature X, but is pretty far off from expected, or maybe high frequency enough to not matter

WUT

# I.6.1 Fit per Coil: State 1 Results Summary

Circuit Feature Assignment	UL Fit Zeros	UL Fit Poles
Coil Impedance	696.5942 Hz	
RC Network	87.0329 Hz	431.3965 Hz
SW Closed LP	0.0325 Hz	0.0293 Hz
????	2246.0201 Hz	1592.0174
Cable impedance?		pair(22092.54 Hz, 59.37 deg)

$$f_z^{coil} = 1/(2\pi L_{coil}/R_{coil}) = 571.085 \text{ Hz}$$

$$f_p^{out} = 1/(2\pi R_4 C_{12}) = 312.069 \text{ Hz}$$

$$f_z^{out} = 1/(2\pi(R_4 + R_5)C_{12}) = 85.110 \text{ Hz}$$



Circuit Feature Assignment	LL Fit Zeros	LL Fit Poles
Coil Impedance	699.0254 Hz	
RC Network	86.5228 Hz	427.0135 Hz
SW Closed LP	No fit?	No fit?
????	2315.2727, 5247.6252 Hz	1623.5029, pair(5943.6595, 10.6624 deg)
Cable impedance?		pair(21390.090 Hz, 58.138 deg)

$$f_p^{coil||cable} = 65.063 \text{ kHz}$$

Circuit Feature Assignment	UR Fit Zeros	UR Fit Poles
Coil Impedance	671.7041 Hz	
RC Network	85.9533 Hz	422.2943 Hz
SW Closed LP	No fit?	No fit?
????	2337.1901 Hz	5132.4934 Hz
????	pair(12262.2781 Hz, 15.218 deg), pair(12822.8952 Hz, 21.5666)	pair(11037.6219 Hz, 61.3485 deg)
????	19443.5355	
Cable impedance?		pair(21731.503 Hz, 73.7415 deg)

Circuit Feature Assignment	LR Fit Zeros	LR Fit Poles
Coil Impedance	570.3 Hz	
RC Network	86.019 Hz	380.235 Hz
SW Closed LP	0.036 Hz	0.032 Hz
????	160.731 Hz	1104.104 Hz
Nearly canceling	pair(3998.485 Hz, 64.2946 deg)	pair(3991.249 Hz, 63.6625 deg)
????	pair(12280.307 Hz, 4.400 deg)	6807.508, 11411.143
Cable impedance?		pair(21818.686 Hz, 59.566 deg)

# I.6.1 Fit per Coil: State 1 Results LR

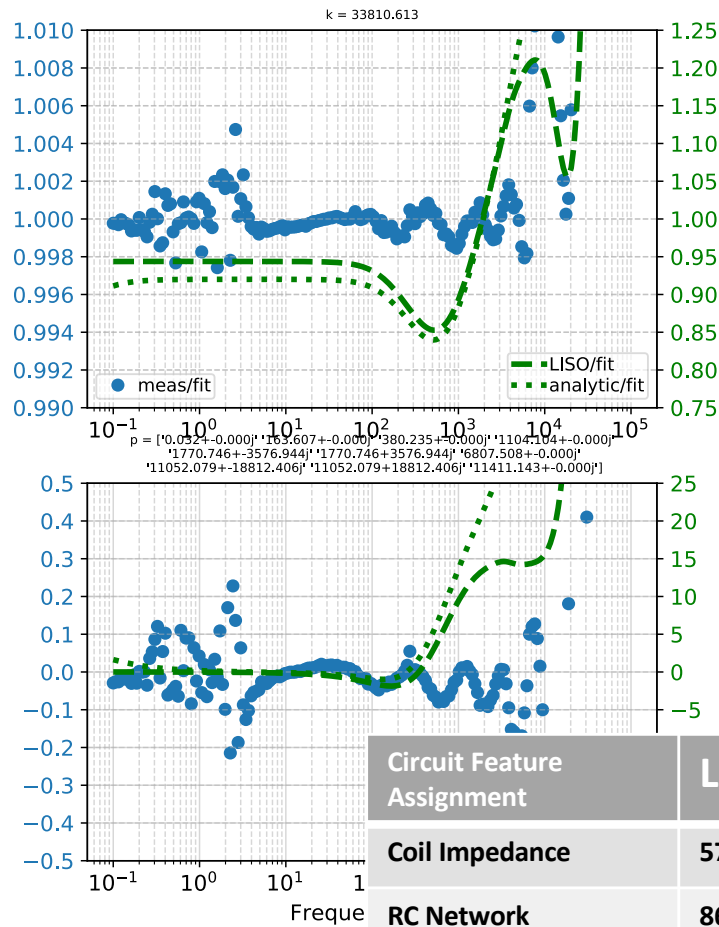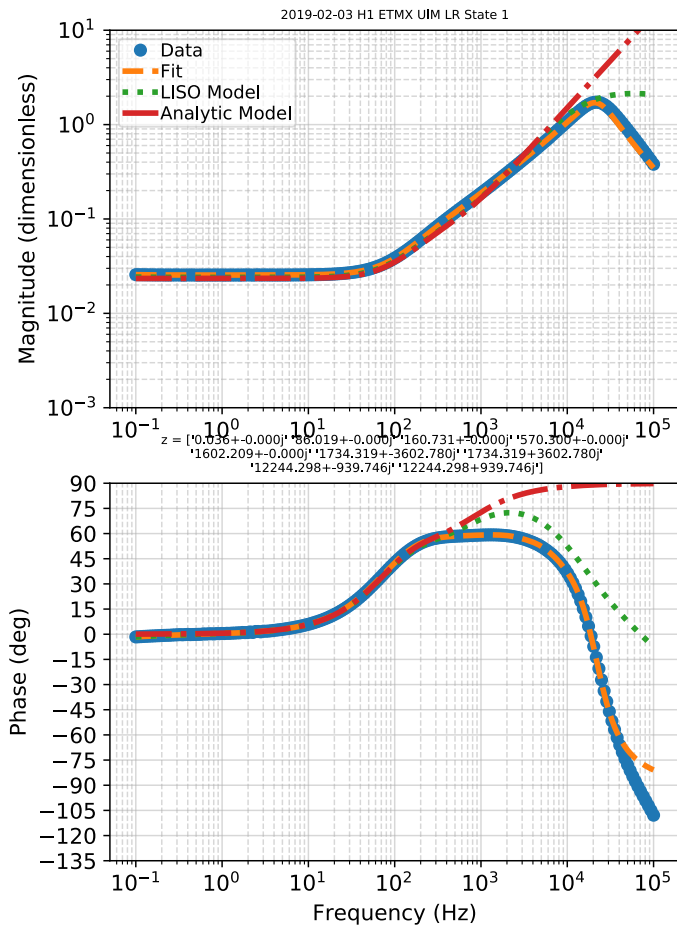

Just to show that the data, the fit, or the fit residuals for the LR “poster child” don’t look any different, but the fit has poles and zeros **right where we expect**, AND some ones that **we don’t expect at all**.

Circuit Feature Assignment	LR Fit Zeros	LR Fit Poles
Coil Impedance	570.3 Hz	
RC Network	86.019 Hz	380.235 Hz
SW Closed LP	0.036 Hz	0.032 Hz
???	160.731 Hz	1104.104 Hz
Nearly canceling	pair(3998.485 Hz, 64.2946 deg)	pair(3991.249Hz, 63.6625 deg)
???	pair(12280.307 Hz, 4.400 deg)	6807.508, 11411.143
Cable impedance?		pair(21818.686 Hz, 59.566 deg)



# I.6.1 The Fit per Coil: State 1 Results Discussion

- Why is LR the poster child, with  $f_z:f_p = (86, 570: 380)$  Hz, where the other three are consistently  $f_z:f_p = (86, 690: 430)$ ?
  - Let's assume that, for whatever reason, the three coils – though not as expected, are fit at real values. 430 vs. 380 Hz means  $R_4$ ,  $C_{12}$  values are in question, and 690 vs. 570 Hz means  $R_{coil}$  or  $L_{coil}$  are in question.
  - Let's assume we know the resistances well at  $(R_4, R_{coil}) = (750, 42.7)$  Ohm. That means  $(C_{12}, L_{coil})$  are actually  $\sim(0.49e-6 \text{ F}, 9.8 \text{ mH})$  instead of the drawing/cannon values of  $(0.68e-6 \text{ F}, 11.9 \text{ mH})$ .
  - Plausible...
- What are all of these mid- kHz poles and zeros? Can we get by with ignoring the fit results above 1 kHz?
  - Is this a manifestation of the bad measurement / saturation?
- Why is the cable impedance so low in frequency and so low in Q?
  - Is \*this\* a manifestation of the bad measurement / saturation?

# 1.6.1 The Fit per Coil: What's next?



You feel I'm in the weeds. I know. \*I\* feel I'm in the weeds. How can we come back up for air? Look at some more weeds.

2. We can blindly assume that the fit is perfect for all coils. If so, we'd use the value of the coil  $f_z$ , divide it out of the  $V_{\text{coil}} / V_{\text{in}}$  data, and look at the  $I_{\text{coil}} / V_{\text{in}}$  transfer function. Does it make sense? Should we bother (re)fitting \*that\* data?
3. Look at the ratio of State 2 to State 1. Is getting the low pass  $f_z:f_p$  pair from that as easy as we expect?
4. Look (and fit) at state 2 by itself. Does the data match the State 1 fit \* (State 2 / State 1) fit?


# I.6.2 Fit per Coil: state 1 $I_{\text{coil}} / V_{\text{out}}$ , taking out “knowns”

What does  $I_{\text{coil}}/V_{\text{out}}$  look like, if we assume good fit for coil  $f_z$  and the RC network's  $f_z:f_p$ ?


2019-02-03 H1 ETMX UIM LL State 1

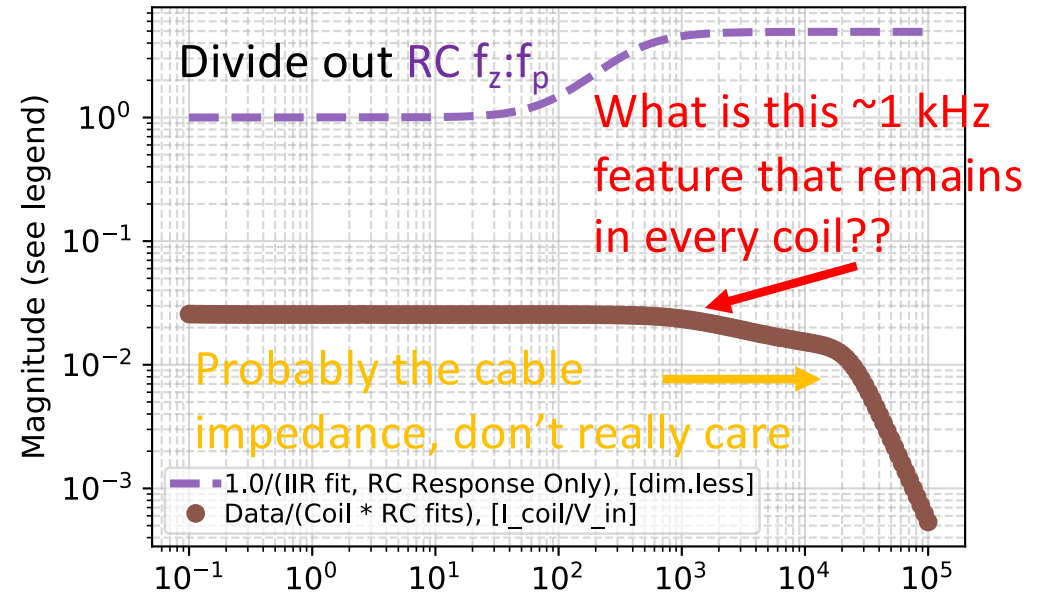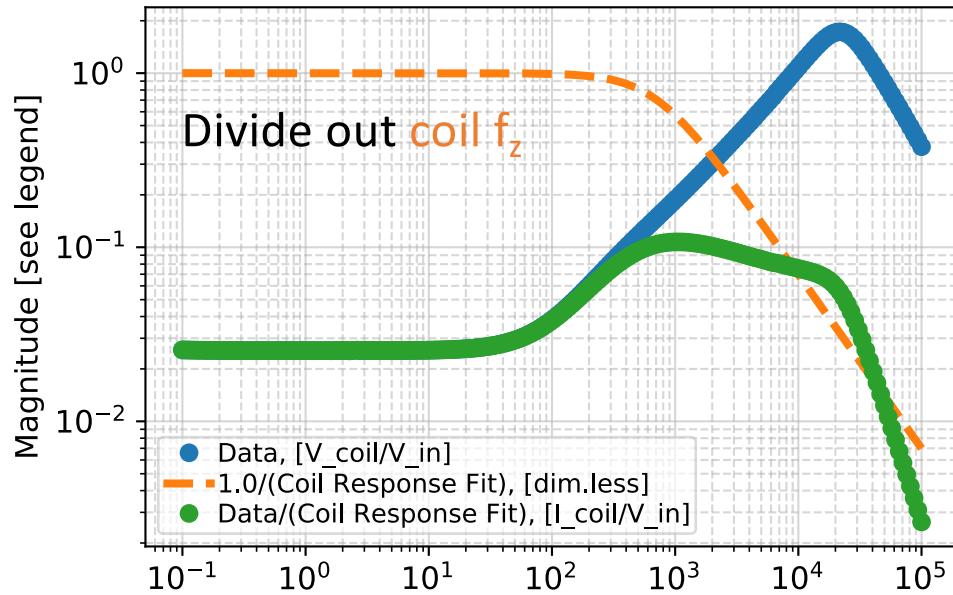

Coil Response  $f_z$  : 699.025 [Hz]

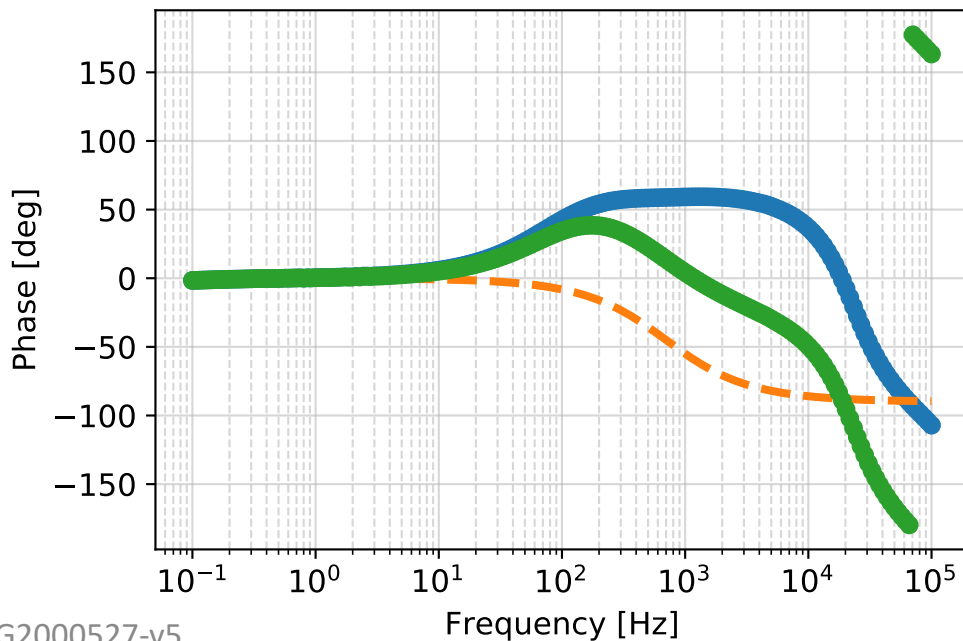


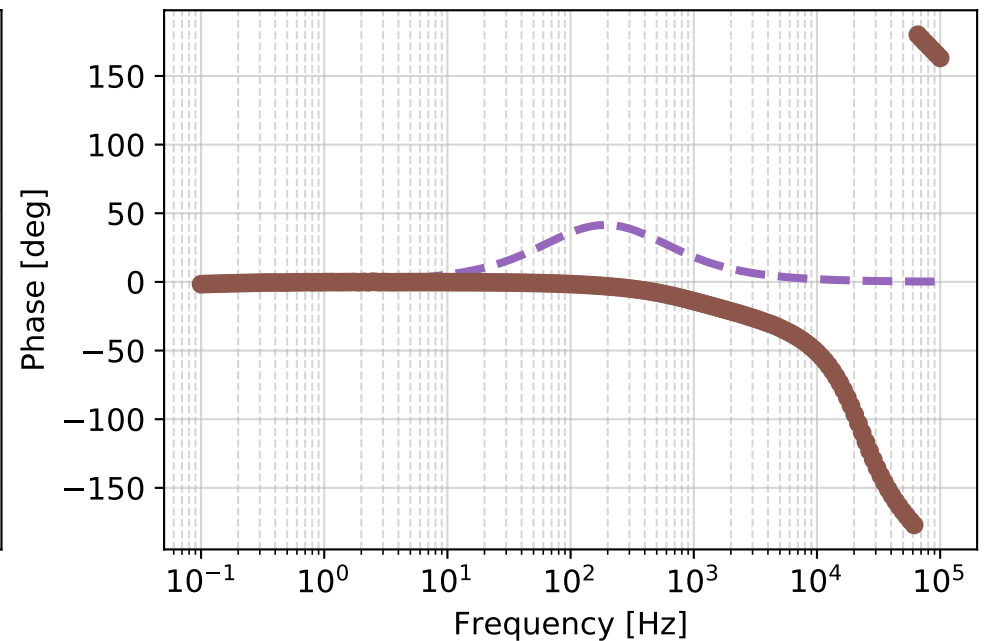
RC Response ( $f_z:f_p$ ) = (86.523:427.013) [Hz]




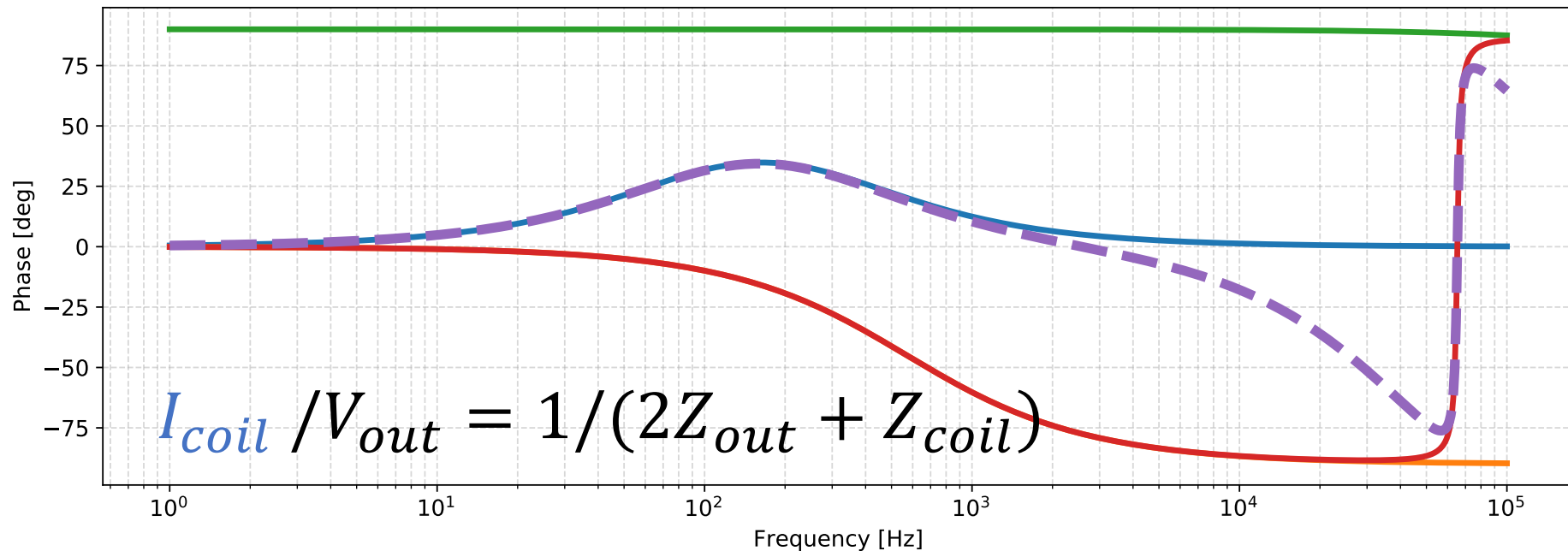
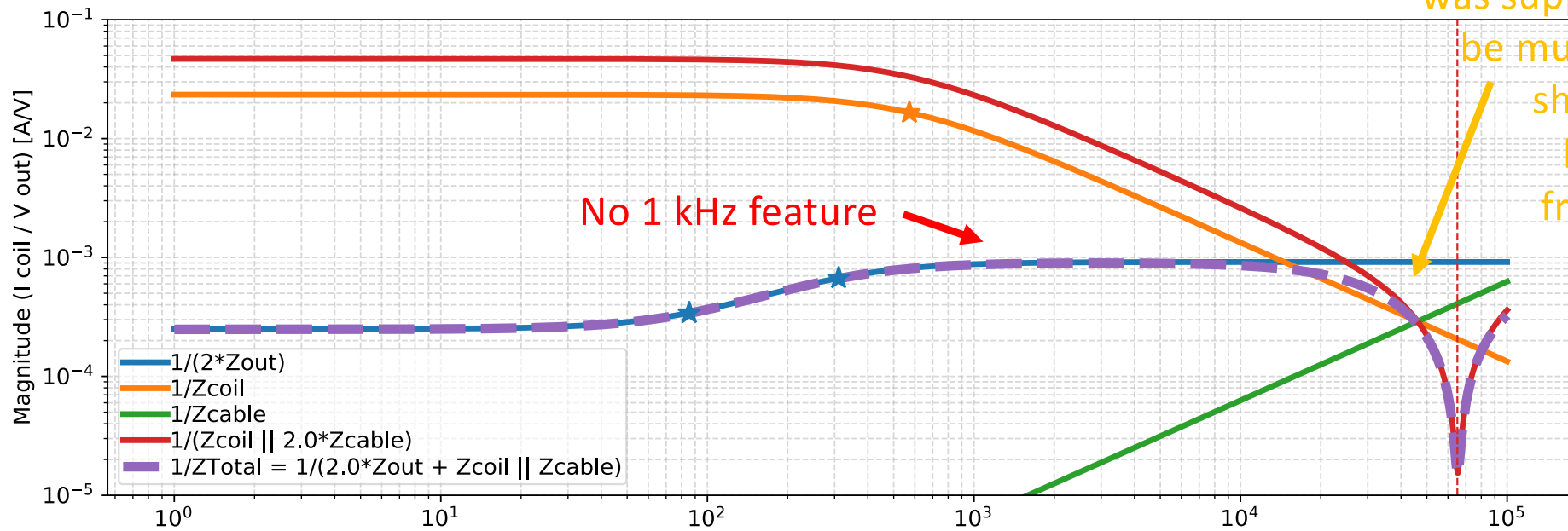
# 1.6.2 Fit per Coil: State 1 remember our expectations?

Green Solid on previous slide should look like Purple dashed here

Coil Impedance was supposed to be much more sharp, and higher in frequency



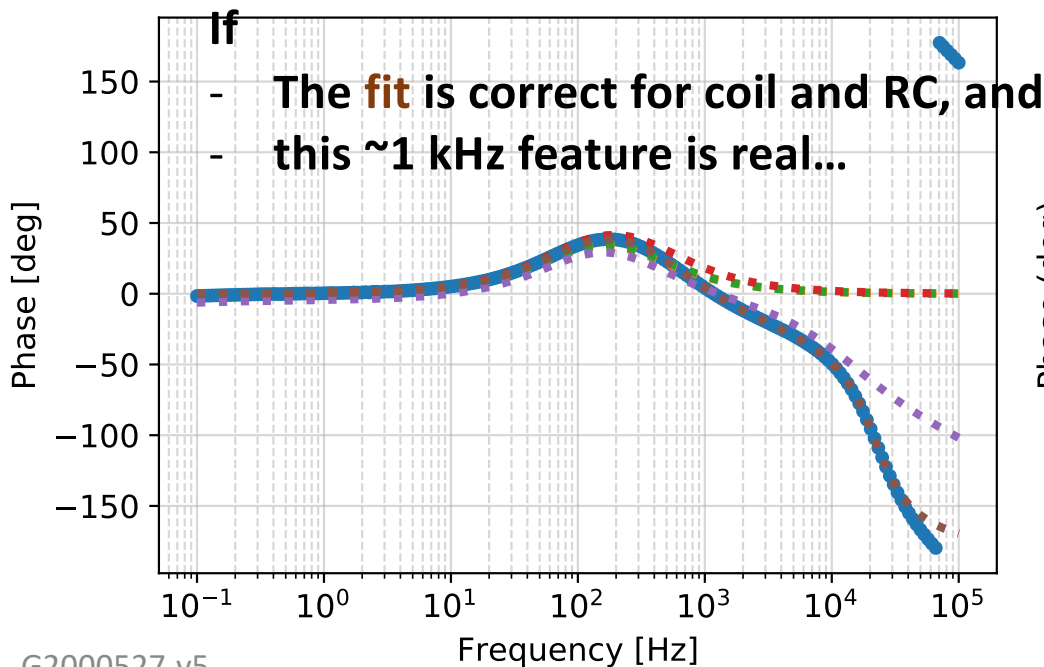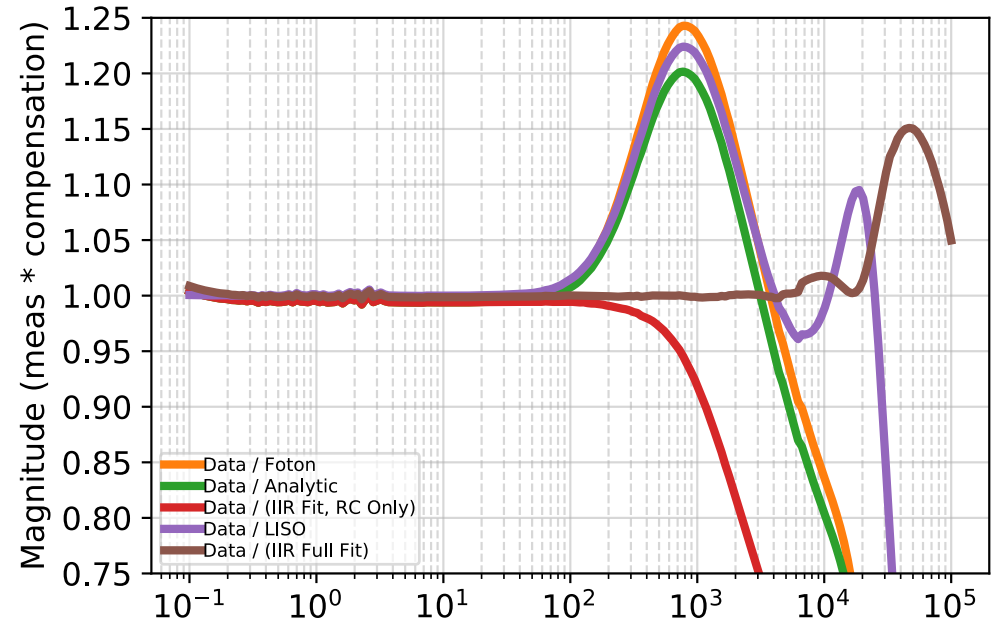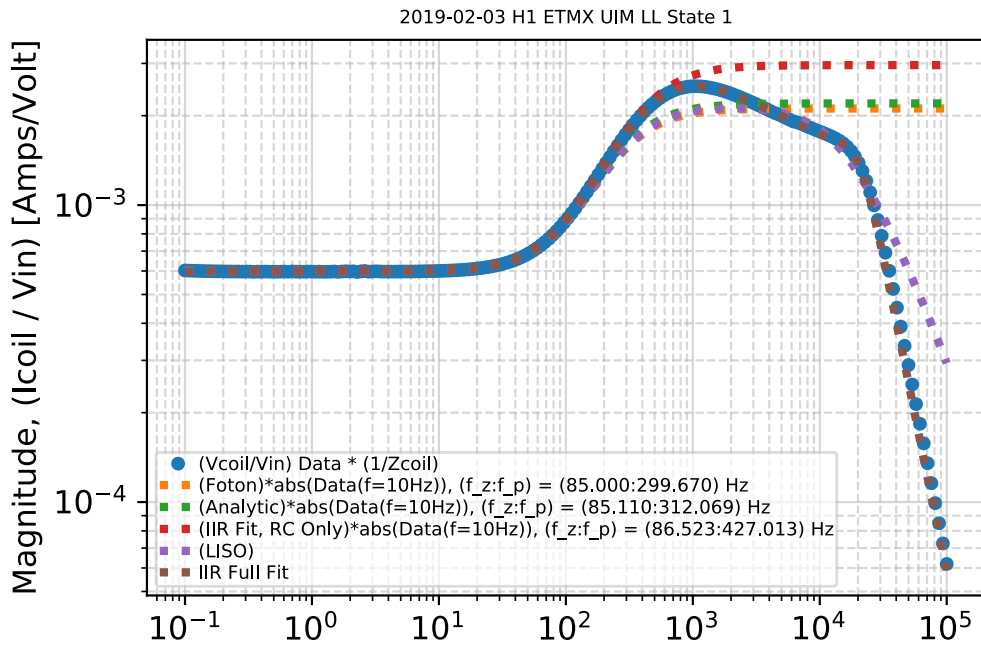
# 1.6.2 Fit per Coil: State 1 How bad would it be?



... then **foton** has the UIM TF

wrong by 10% / 5 deg at 300 Hz ...

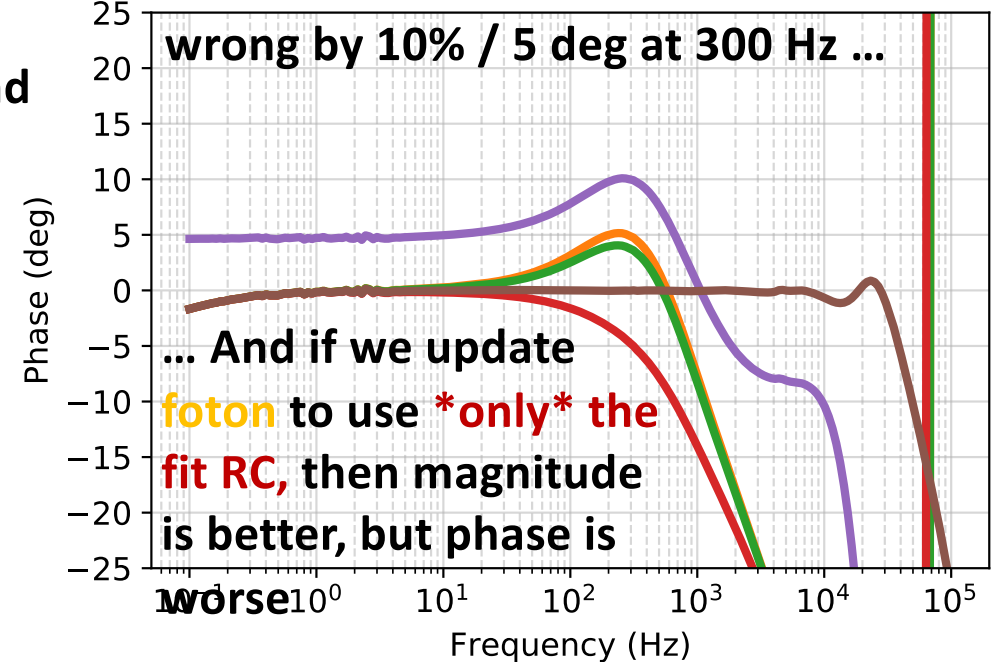

# 1.6.1 The Fit per Coil: What's next?

You feel I'm in the weeds. I know. \*I\* feel I'm in the weeds. How can we come back up for air? Look at some more weeds.

2. We can blindly assume that the fit is perfect for all coils. If so, we'd use the value of the coil  $f_z$ , divide it out of the  $V_{\text{coil}} / V_{\text{in}}$  data, and look at the  $I_{\text{coil}} / V_{\text{in}}$  transfer function. Does it make sense? Should we bother (re)fitting \*that\* data?


Conclude: There's really something weird with this data, manifesting at 1-2 kHz

3. Look at the ratio of State 2 to State 1. Is getting the low pass  $f_z:f_p$  pair from that as easy as we expect?
4. Look (and fit) at state 2 by itself. Does the data match the State 1 fit \* (State 2 / State 1) fit?

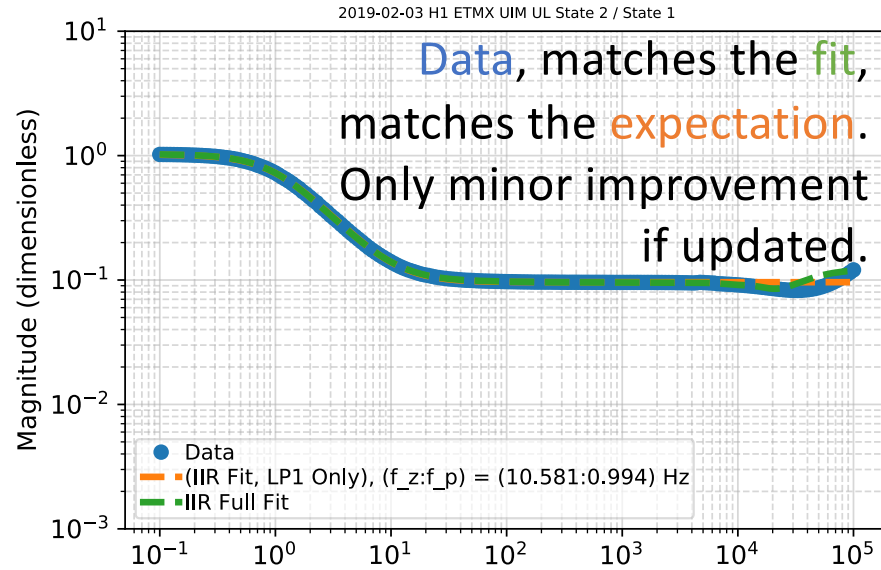
# 1.6.3 Fit per Coil: State 2/State 1: the LP1 zs and ps

OK. Need some air. Does the analog data we have make any sense? It does.



Look at the ratio between state 2 and state 1.



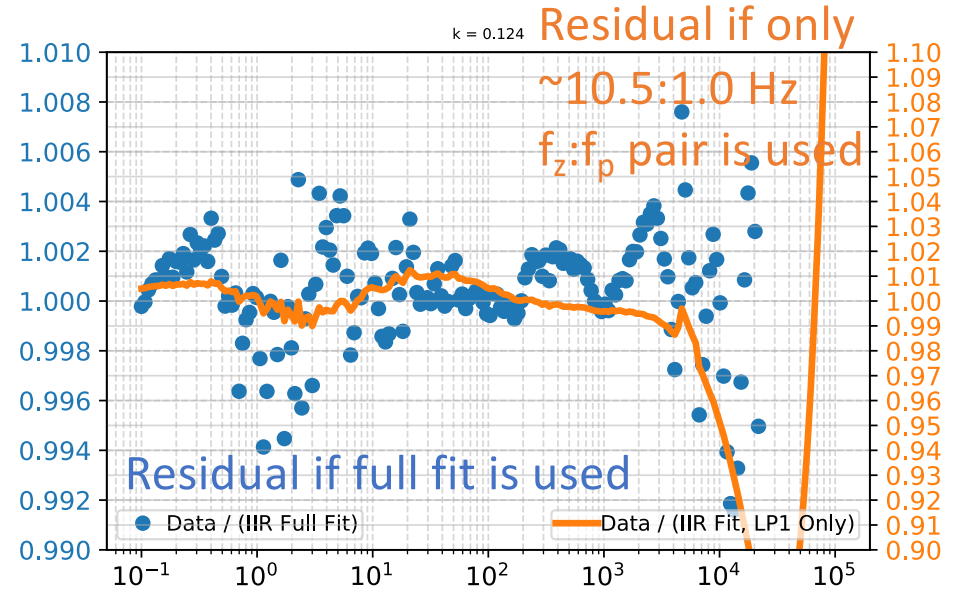$z = [2.900+0.000j \ 4.769+0.000j \ 10.581+0.000j \ 145.872+0.000j \ 1113.078+0.000j \ 4534.594+2872.478j \ 4534.594+2872.478j \ 5712.915+7530.408j \ 5712.915+7530.408j \ 12354.069+17080.675j \ 12354.069+17080.675j]$



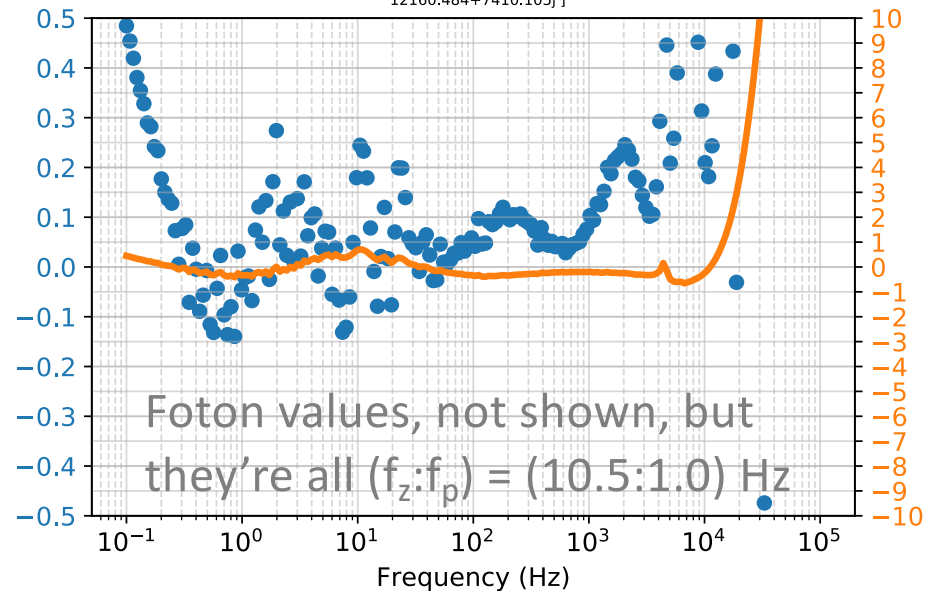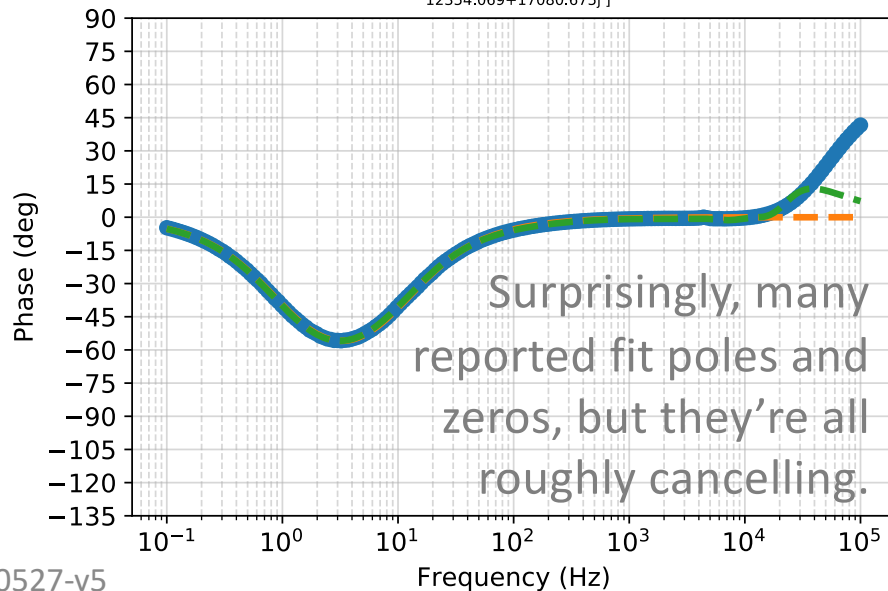$p = [0.994+0.000j \ 2.750+0.000j \ 5.059+0.000j \ 143.257+0.000j \ 1128.005+0.000j \ 6152.052+4502.674j \ 6152.052+4502.674j \ 10974.644+1875.236j \ 10974.644+1875.236j \ 12160.484+7410.105j \ 12160.484+7410.105j]$



# 1.6.3 Fit per Coil: State 2/State 1: Results Summary

UL	Fit Zeros	Fit Poles
Nearly cancelling	2.89952 Hz	2.75042 Hz
Nearly canceling	4.76888 Hz	5.05923 Hz
<b>SW Closed LP</b>	<b>10.5814 Hz</b>	<b>0.99443 Hz</b>
Nearly canceling	145.8720 Hz	143.2566 Hz
Nearly canceling	1113.0777 Hz	1128.0047 Hz
????	Pair(5367.8369 Hz, 32.3526 deg)	Pair(7623.7668 Hz, 36.2003 deg)
????	Pair(9452.2185 Hz, 52.8143 deg)	Pair(11133.7022 Hz, 9.6965 deg)
????	Pair(21080.1439 Hz, 54.1226 deg)	Pair(14240.3312 Hz, 31.3564 deg)

UR	Fit Zeros	Fit Poles
<b>SW Closed LP</b>	<b>10.3314 Hz</b>	<b>0.98556 Hz</b>
Nearly canceling	52.4826 Hz	51.6746 Hz
Nearly canceling	344.4865 Hz	341.47236 Hz
Nearly canceling	2137.9732 Hz	2163.3018 Hz
????	3211.9846 Hz	5833.4346 Hz
????	pair(4802.2480 Hz, 32.800 deg)	4409.4475 Hz, 5019.2094 Hz
????	pair(11329.7897 Hz, 52.0737 deg)	Pair(14962.1253 Hz, 39.2143 deg)
????	pair(24347.3447 Hz, 57.547 deg)	15509.4456 Hz, 17175.5778 Hz

LL	Fit Zeros	Fit Poles
<b>SW Closed LP</b>	<b>10.3830 Hz</b>	<b>0.9820 Hz</b>
Nearly canceling	61.3351 Hz	60.2293 Hz
Nearly canceling	282.9903 Hz	291.4153 Hz
Nearly canceling	Pair(643.6467 Hz, 11.4552 deg)	630.7973 Hz, 654.7394 Hz
????	Pair(5512.6344 Hz, 39.6531 deg)	Pair(6718.1860 Hz, 65.2573 deg)
????	Pair(7085.8327 Hz, 66.5343 deg)	10061.4559 Hz, 10891.6712 Hz
Nearly canceling	Pair(13638.8270 Hz, 63.1878 deg)	Pair(13419.9763 Hz, 26.1267 deg)
????	Pair(24657.6748 Hz, 61.7029 deg)	Pair(15566.9234 Hz, 55.0929 deg)





LR	Fit Zeros	Fit Poles
Nearly cancelling	0.05932 Hz	0.06045 Hz
<b>SW Closed LP</b>	<b>10.4728 Hz</b>	<b>0.98792 Hz</b>
Nearly canceling	93.0036 Hz	91.4280 Hz
Nearly canceling	1522.7636 Hz	1579.1637 Hz
????	Pair(4255.9612 Hz, 29.7771 deg) Pair(8332.2720 Hz, 54.3682 deg)	5443.8019 Hz, 8077.0312 Hz, Pair(11032.6047 Hz, 39.2195 deg)
Nearly canceling	Pair(13237.5898 Hz, 61.0969 deg)	Pair(13752.7035 Hz, 39.9270 deg)
????	Pair(25155.6858 Hz, 59.6633 deg)	Pair(13801.8767 Hz, 29.9008 deg)



# I.6.3 Fit per Coil: State 2 / State 1 Oddball -- UR

Only UR is of concern with the residual of “if we ignore everything but the fit fz:fp that closely matches the expected low pass frequencies” exceeding 1% in magnitude above 100 Hz...

UR	Zeros	Poles
SW Closed LP	10.3314 Hz	0.98556 Hz
Nearly canceling	52.4826 Hz	51.6746 Hz
Nearly canceling	344.4865 Hz	341.47236 Hz
Nearly canceling	2137.9732 Hz	2163.3018 Hz
????	3211.9846 Hz	5833.4346 Hz
????	pair(4802.2480 Hz, 32.800 deg)	4409.4475 Hz, 5019.2094 Hz
????	pair(11329.7897 Hz, 52.0737 deg)	Pair(14962.1253 Hz, 39.2143 deg)
????	pair(24347.3447 Hz, 57.547 deg)	15509.4456 Hz, 17175.5778 Hz

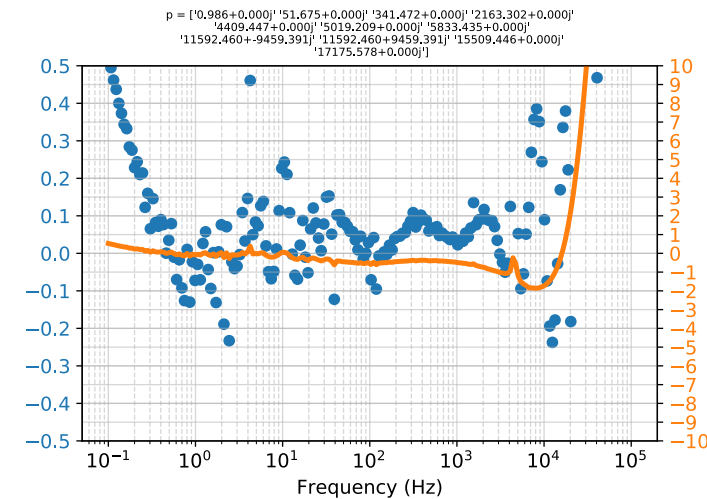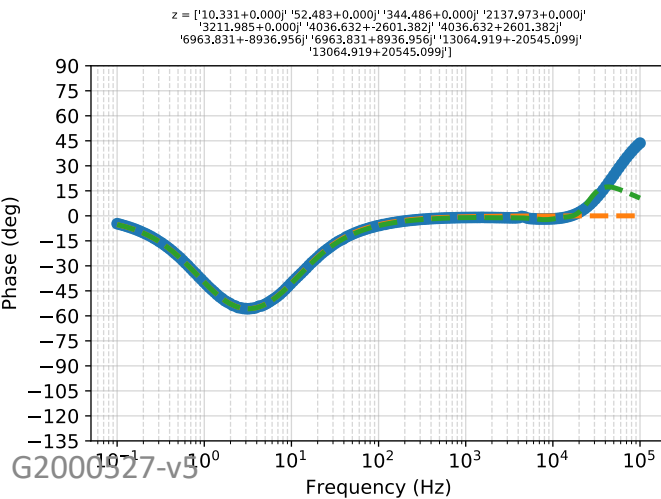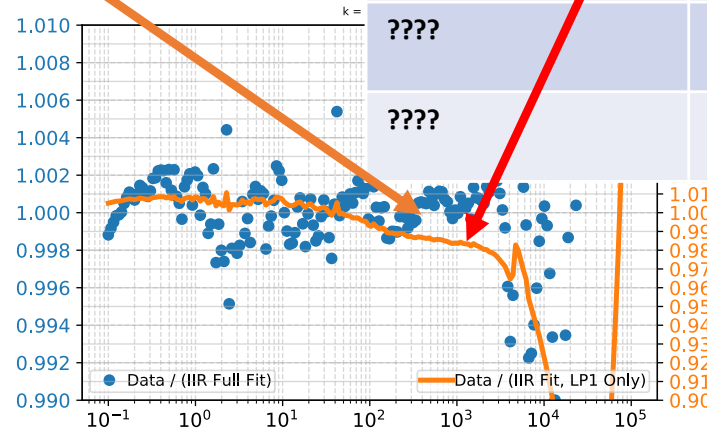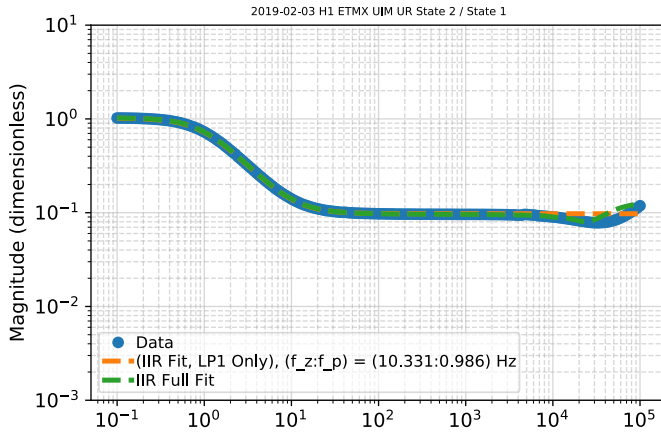

But ... as you'll see (and what is often said with details of these studies): we've got bigger fish to fry...

# 1.6.1 The Fit per Coil: What's next?

You feel I'm in the weeds. I know. \*I\* feel I'm in the weeds. How can we come back up for air? Look at some more weeds.

2. We can blindly assume that the fit is perfect for all coils. If so, we'd use the value of the coil  $f_z$ , divide it out of the  $V_{\text{coil}} / V_{\text{in}}$  data, and look at the  $I_{\text{coil}} / V_{\text{in}}$  transfer function. Does it make sense? Should we bother (re)fitting \*that\* data?








Conclusion: There's really something weird with this data, manifesting at 1-2 kHz

3. Look at the ratio of State 2 to State 1. Is getting the low pass  $f_z:f_p$  pair from that as easy as we expect?

Conclusion: Yes, we can safely extract the fit low pass  $f_z:f_p$  pair.

4. Look (and fit) at state 2 by itself. Does the data match the State 1 fit \* (State 2 / State 1) fit?

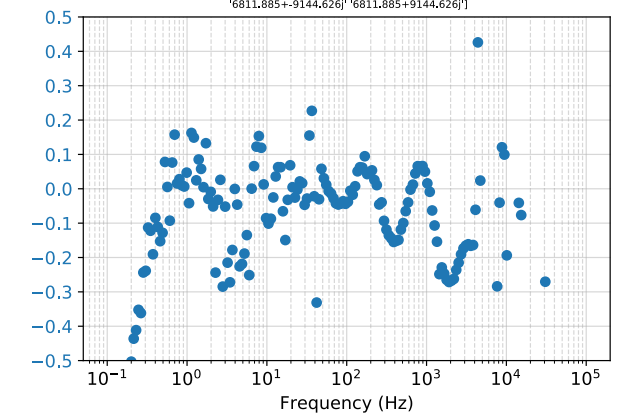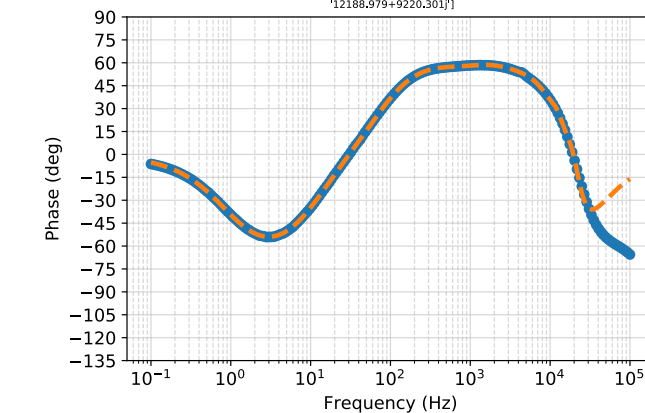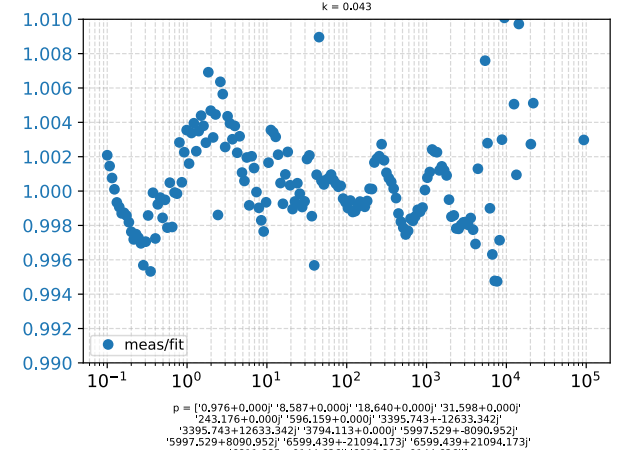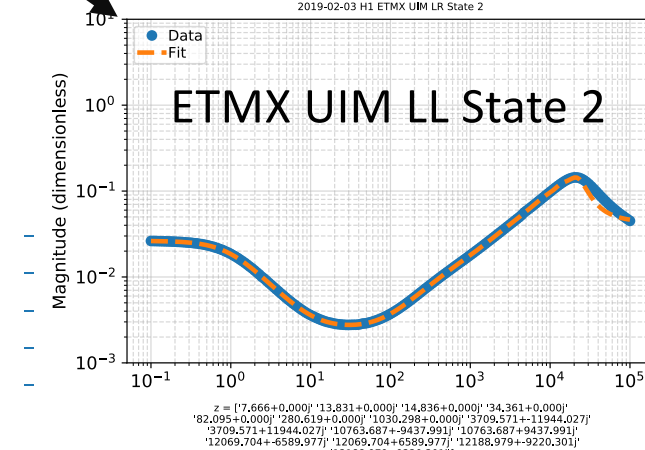
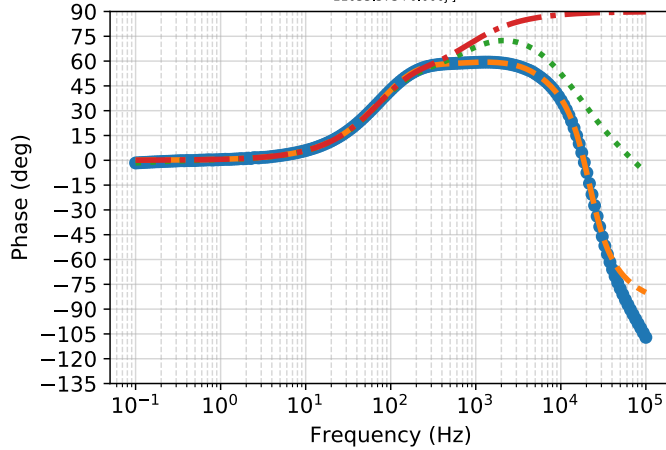
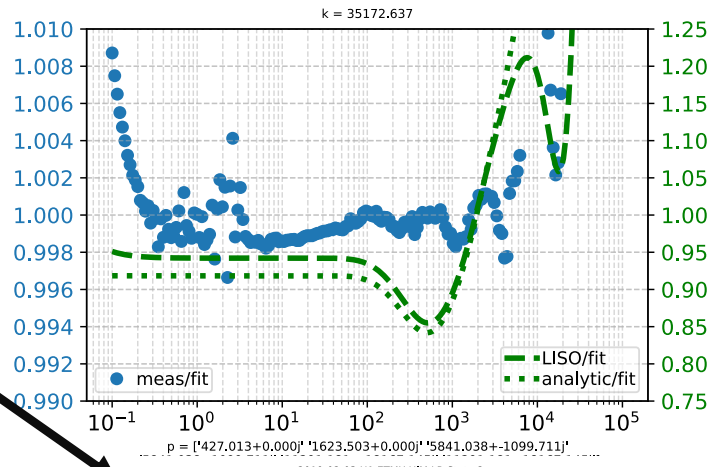
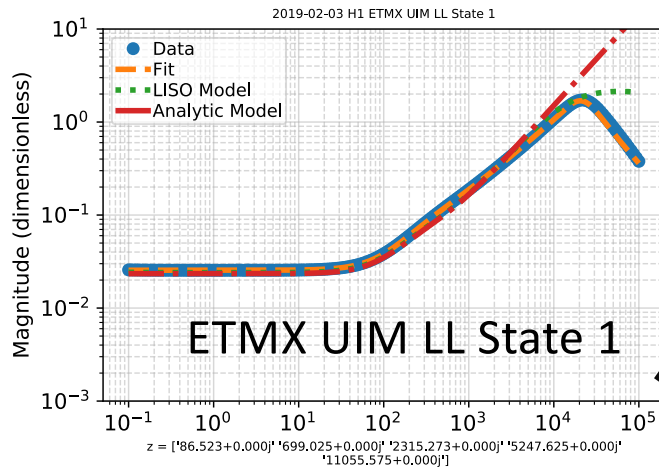
# I.6.4 Fit per Coil: State 2 vs State (1) and (2/1) Fits







Since the ratio behaved so much like expected, State 2 by itself is probably going to look like the product of the State 1 results and the State2/State1, and it does.

# I.6.4 Fit per Coil: State 2 $I_{\text{coil}} / V_{\text{in}}$ Residuals

2019-02-03 H1 ETMX UIM LL State 2

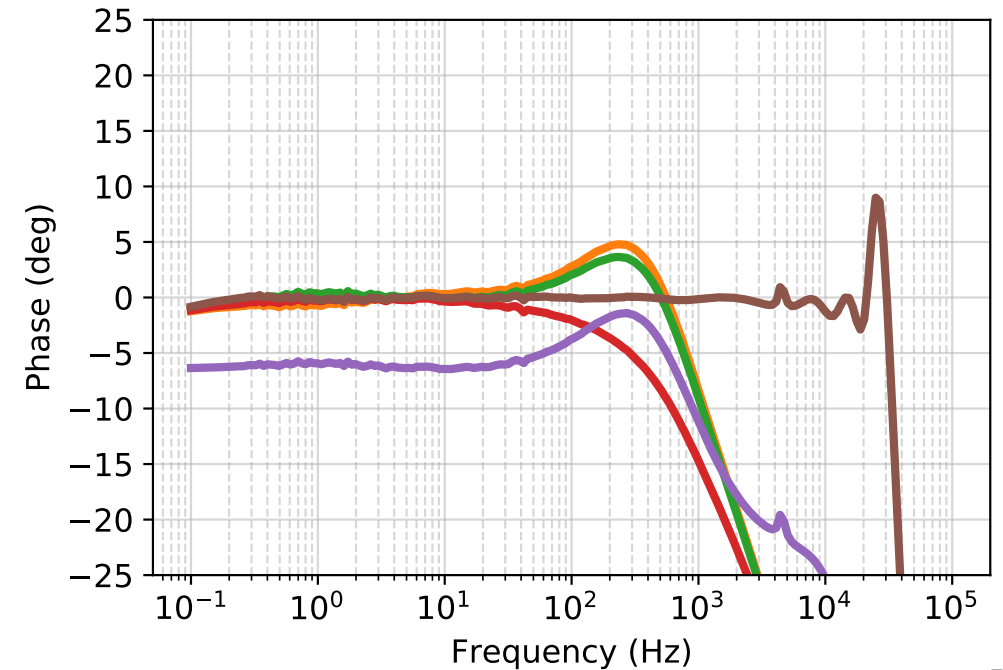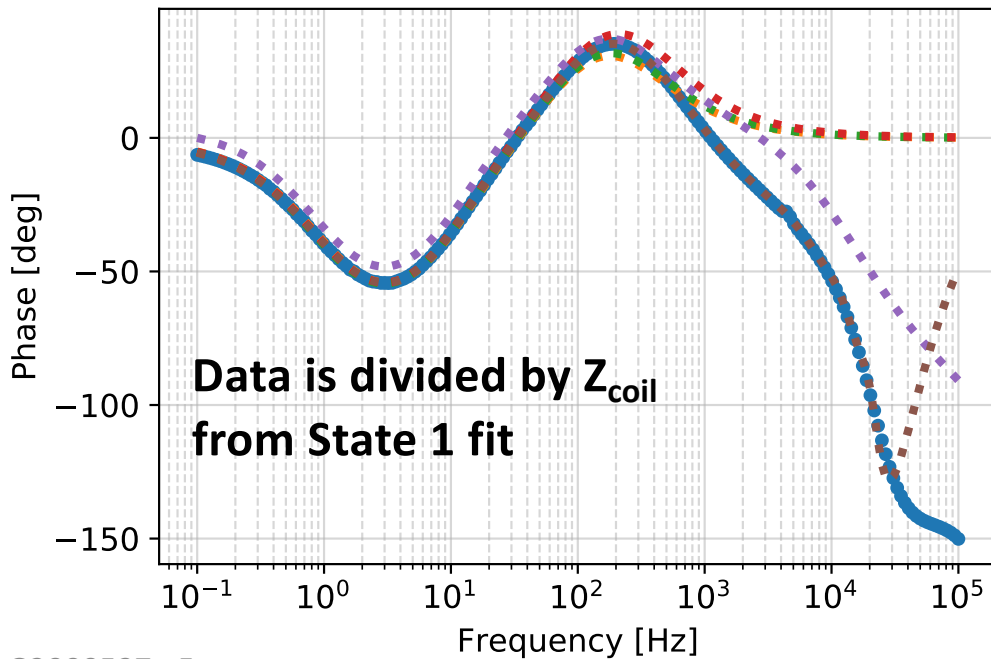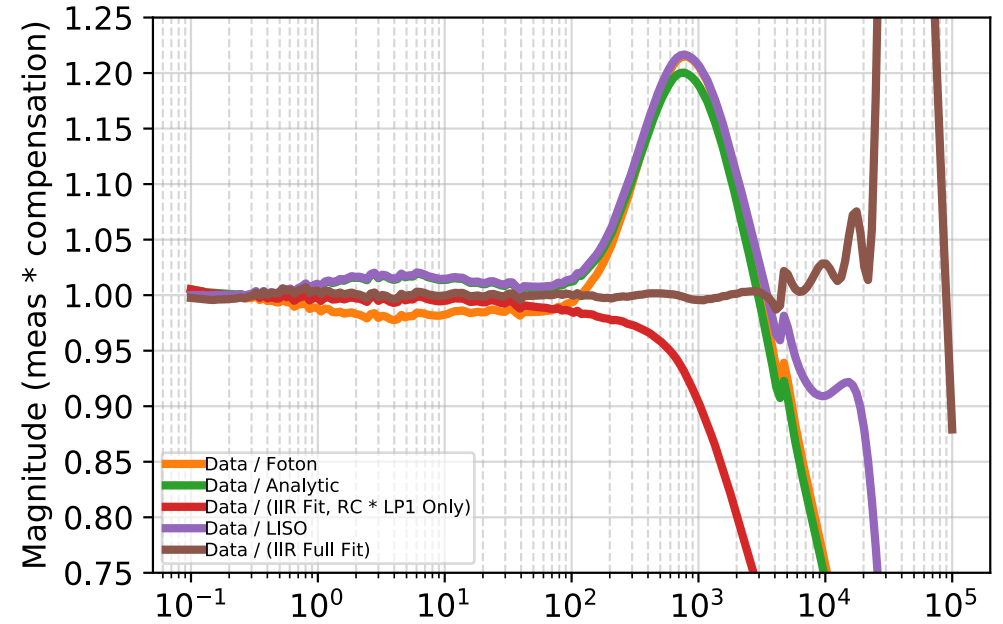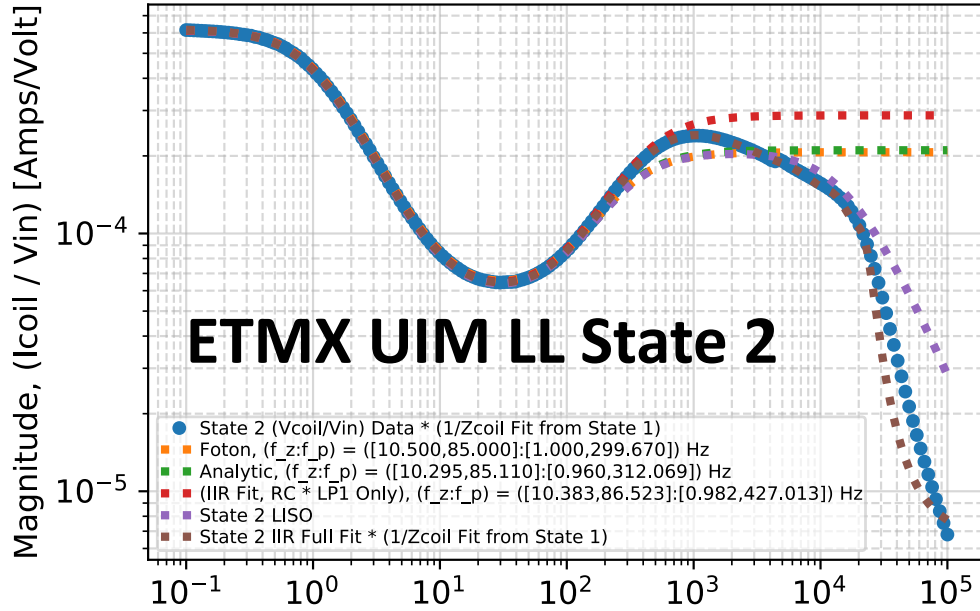
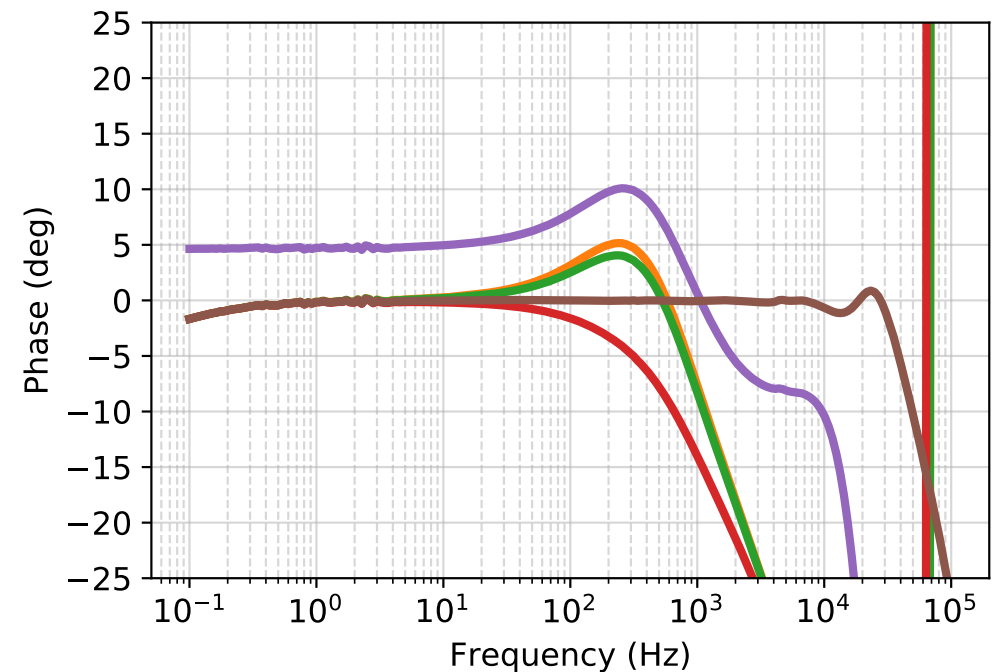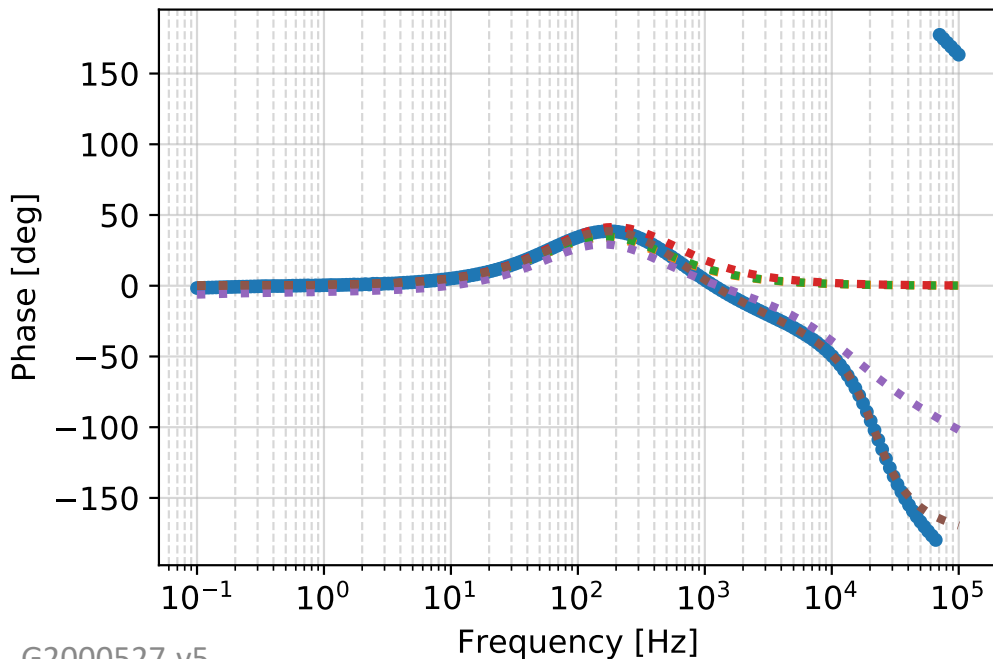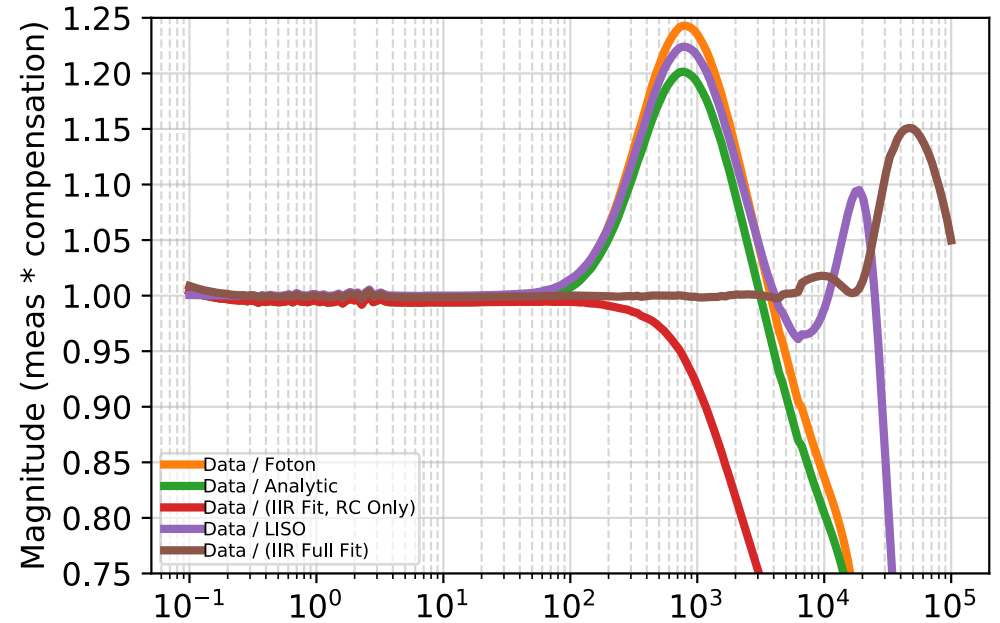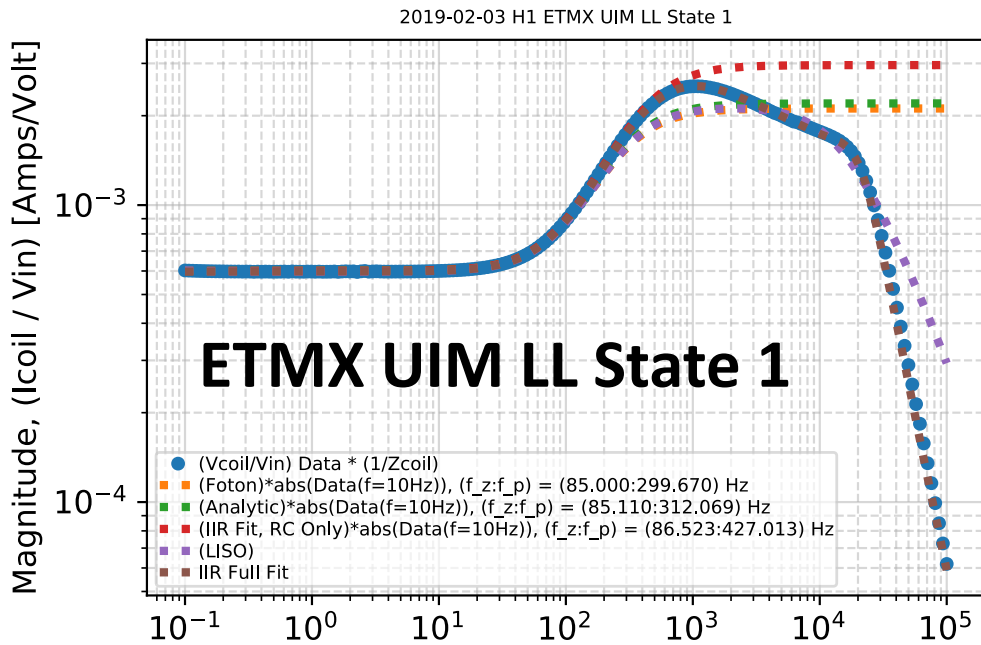
# I.6.4 Fit per Coil: Remember State 1...



# I.6.4 Fit per Coil: Fit answer Comparison: UL and LL

State 1 fit and State 2/1 fit results

Circuit Feature Assignment	UL Fit Zeros	UL Fit Poles
Coil Impedance	696.5942 Hz	
RC Network	87.0329 Hz	431.3965 Hz
SW Closed LP	10.5814 Hz	0.99443 Hz
?????	2246.0201 Hz	1592.0174
Cable impedance?		pair(22092.54 Hz, 59.37 deg)

Hrmm... State 2 fit  $f_z:f_p$  numbers are pretty different from State 1 fit and State 2/1 fit, except for LP1 values

Circuit Feature Assignment	LL Fit Zeros	LL Fit Poles
Coil Impedance	699.0254 Hz	
RC Network	86.5228 Hz	427.0135 Hz
SW Closed LP	10.3830 Hz	0.9820 Hz
?????	2315.2727, 5247.6252 Hz	1623.5029, pair(5943.6595, 10.6624 deg)
Cable impedance?		pair(21390.090 Hz, 58.138 deg)

State 2 fit results

Circuit Feature Assignment	UL Fit Zeros	UL Fit Poles
Nearly canceling	0.028847 Hz	0.026747 Hz
Coil Impedance	842.2736 Hz	
RC Network	89.2645 Hz	472.0885 Hz
SW Closed LP	10.3110 Hz	0.97697 Hz
?????	4401.5227 Hz	2798.8233 Hz
Cable impedance?		pair(21118.6667 Hz, 42.1804 deg)

Circuit Feature Assignment	LL Fit Zeros	LL Fit Poles
Nearly canceling	0.37481	0.36443
Nearly canceling	6.43273	6.36145
Nearly canceling	183.9139	200.7849
Coil Impedance	549.8213	
RC Network	89.9268	346.3705
SW Closed LP	10.2956	0.9999998
?????	1632.2068	1177.1166 Hz,
?????	pair(15713.5244 Hz, 42.2756 deg), 15762.0667 Hz	3750.3363 Hz, pair(7843.1654 Hz, 52.3709 deg)
Cable impedance?	pair(20052.8982 Hz, 26.0454 deg), 21877.4091 Hz, 22594.0678 Hz	pair(13919.8163 Hz, 69.7893 deg), pair(22669.5375 Hz, 77.5484 deg)

# 1.6.4 Fit per Coil: Fit answer Comparison: UR and LR

Circuit Feature Assignment	UR Fit Zeros	UR Fit Poles
Nearly canceling	40.5700 Hz	39.1471 Hz
Nearly canceling	112.8337 Hz	101.2331 Hz
<b>Coil Impedance</b>	<b>767.4099 Hz</b>	
<b>RC Network</b>	<b>77.2791 Hz</b>	<b>455.1022 Hz</b>
<b>SW Closed LP</b>	<b>10.2308 Hz</b>	<b>0.97447</b>
?????	pair(5414.0903 Hz, 57.7074 deg) pair(8543.0235 Hz, 31.6995 deg) pair(12415.6958 Hz, 20.2785 deg)	pair(4588.0341 Hz, 51.4882 deg) pair(6168.5520 Hz, 63.2901 deg)
Nearly canceling	pair(11209.1738 Hz, 2.010 deg)	pair(11298.7088 Hz, 65.2882 deg)
Cable impedance?		pair(21411.5152 Hz, 71.3476 deg)

Circuit Feature Assignment	LR Fit Zeros	LR Fit Poles
<b>Coil Impedance</b>	<b>280.6193 Hz</b>	
<b>RC Network</b>	<b>82.0951</b>	<b>243.1757 Hz</b>
<b>SW Closed LP</b>	<b>13.8309</b>	<b>0.97606 Hz,</b>
Nearly canceling	7.66634 Hz	8.58653 Hz
Nearly canceling	34.3607 Hz,	31.5980 Hz
?????	14.8359 Hz 1030.2985 pair(12506.8258 Hz, 72.7462 deg) pair(13751.5651 Hz, 28.6342 deg) pair(14315.4683 Hz, 41.2455 deg)	18.6402 Hz 596.1594 3794.1125 Hz pair(13081.7578 Hz, 74.9549 deg) pair(10071.4374 Hz, 53.4518 deg) pair(11402.8925 Hz,

Circuit Feature Assignment	UR Fit Zeros	UR Fit Poles
<b>Coil Impedance</b>	<b>671.7041 Hz</b>	
<b>RC Network</b>	<b>85.9533 Hz</b>	<b>422.2943 Hz</b>
<b>SW Closed LP</b>	<b>10.3314 Hz</b>	<b>0.98556 Hz</b>
????	2337.1901 Hz pair(12262.2781 Hz, 15.218 deg) pair(12822.8952 Hz, 21.5666)	5132.4934 Hz pair(11037.6219 Hz, 61.3485 deg)
????	19443.5355	
Cable impedance?		pair(21731.503 Hz, 73.7415 deg)

Circuit Feature Assignment	LR Fit Zeros	LR Fit Poles
<b>Coil Impedance</b>	<b>570.3 Hz</b>	
<b>RC Network</b>	<b>86.019 Hz</b>	<b>380.235 Hz</b>
<b>SW Closed LP</b>	<b>10.4728 Hz</b>	<b>0.98792 Hz</b>
????	160.731 Hz	1104.104 Hz
Nearly canceling	pair(3998.485 Hz, 64.2946 deg)	pair(3991.249Hz, 63.6625 deg)
????	pair(12280.307 Hz, 4.400 deg)	6807.508, 11411.143
Cable impedance?		pair(21818.686 Hz, 59.566 deg)

# 1.6.1 The Fit per Coil: What's next?

You feel I'm in the weeds. I know. \*I\* feel I'm in the weeds. How can we come back up for air? Look at some more weeds.

1. We can blindly assume that the fit is perfect for all coils. If so, we'd use the value of the coil  $f_z$ , divide it out of the  $V_{\text{coil}} / V_{\text{in}}$  data, and look at the  $I_{\text{coil}} / V_{\text{in}}$  transfer function. Does it make sense? Should we bother (re)fitting *that* data?

Conclusion: **There's really something weird with this data, manifesting at 1-2 kHz**

2. Look at the ratio of State 2 to State 1. Is getting the low pass  $f_z:f_p$  pair from that as easy as we expect?

Conclusion: Yes, we can safely extract the fit low pass  $f_z:f_p$  pair.

3. Look (and fit) at state 2 by itself. Does the data match the State 1 fit \* (State 2 / State 1) fit?

Conclusions: **Sort of.** The residuals have same mysterious 1-2 KHz features from State 1, **but the poles and zeros are astoundingly different, some more like expected, some just wrong, with no general trends as each coil is different.**



# 1.6 Fit per Coil: Grand Conclusions

- We definitely, definitely, definitely need to get good measurements.
  - We should always drive the drivers, and measure the response differentially.
- Unfortunately, we can't assume each coil channel is going to be even roughly the same, and we may get conflicting answers between what should be the same answers when switching between states.
  - e.g. State 2 / State 1 for for LP1 is not the same as State 2 alone
  - So we should be prepare to the “two clocks” situation, where don't know which to choose.
- Make the data going in to the fitter as simple as possible, when it makes physical sense to do so.
  - Never, ever, ever take measurements with the coil as a part of the measurement. Just put a no-capacitance, 40 Ohm dummy OSEM “across the back” of the driver as the “coil” “load” impedance.
  - That also means that we can't use the FAST\_I\_MONs measurements either -- not because “they don't measure the output network” -- but because they include the coil impedance which drastically confuses the even the best fitting routines
  - We should perform the same analytical analysis on PUM driver vs. the AOSEM to confirm  $Z_{coil} \ll Z_{out}$ .... another day.

# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
- 7. Converting fit results in to systematic error in  $A_{UIM}$**
8. Converting sys error in  $A_{UIM}$  to sys error in R and Conclusions

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# 1.7 Converting Individual Coil Fit Results in to Systematic Error in $A_{UIM}$

- Let's assume we understood and we're happy with everything from section 1.6.
  - **Remember: we're not, but let's move on anyways, because this is the data we have.**
- The individual coil results must be used retroactively to predict what error was caused in the \*total\* longitudinal actuation strength in the UIM.

You can think of it like this:

$$A_U = E2O * \left( \frac{F_{UL}}{F_{UR}} \right) * DAC * AI * \left( \frac{CD_{UL}}{CD_{LR}} \right) * M * S_U$$

# 1.7 Fit per Coil >> Error in $A_{UIM}$ : Reality

Or like this:

$$F_{ii}(f) = E2O_{ii} * D_{ii}(f) * DAC_{ii} * AI_{ii} * TC_{ii} * CD_{ii}(f) * M_{ii}$$

$$A_{UIM} = S_U(f) * \sum_{ii} F_{ii}$$

where  $ii = UL, LL, UR, LR$ , and for each coil chain, the actuation strength of each driver/coil/magnet chain,  $F_{ii}$ , has the following components:

- $E2O$  is the Euler 2 OSEM matrix (exactly 0.25 for each coil),
- $D(f)$  is the normalized digital compensation “COILOUTF” filter for each coil,
- $DAC$ ,  $AI$ , and  $TC$  are the digital-to-analog converter gain, anti-aliasing filter, and DC transconductance of the coil driver respectively
- $CD(f)$  is the normalized coil driver response,
- $M$  is the magnet strength, and
- $S_U$  is the UIM longitudinal force to TST displacement transfer function response

Ideally,  $D_{ii}(f)$  would be the perfect inverse of  $CD_{ii}(f)$  for every coil, they would cancel to a unity transfer function and we can exclude it from any model.

That’s what we’ve done for the UIM in the calibration group’s DARM loop model.

However, the frequency dependent systematic error in  $A_{UIM}$  arises when  $D_{ii}(f)$  doesn’t perfectly invert  $CD_{ii}(f)$ , and the fact that the frequency dependent error from each stage is \*summed\* means that error is not easily intuited from the individual chain error.

# 1.7 Fit per Coil >> Error in $A_{UIM}$ : Model

$$F_{ii}(f) = E2O_{ii} * D_{ii}(f) * DAC_{ii} * AI_{ii}(f) * TC_{ii} * C_{ii}(f) * M_{ii}$$

$$A_{UIM} = S_U(f) * \sum_{ii} F_{ii}$$

So we need to construct a model with these terms explicitly included.

Let's take the above, and assume everything in between  $D_{ii}$  and  $C_{ii}$  for each chain (namely  $DAC_{ii}$ ,  $AI_{ii}(f)$ , and  $TC_{ii}$ ) is only a common gain to all four chains. This is an OK assumption because

- we take some effort (eg [LHO:42740](#)) to "balance" the gain of each path to minimize length to angle coupling.
- the AI filter response,  $AI(f)$ , which is a 16kHz elliptic lowpass, in general doesn't start to deviate from "just a gain" until several kHz, and each channel would only have a small difference at that. Including the measured differences is an exercise for some other day.

$$F_{ii}(f) = E2O * DAC * AI(f) * TC * M * D_{ii}(f) * C_{ii}(f)$$

$$A_{UIM} = S_U(f) * E2O * DAC * AI(f) * TC * M * \sum_{ii} D_{ii}(f) * C_{ii}(f)$$

Under this assumption, the systematic error,  $\eta_{UIM}$ , can be computed using only what we already have!

$$\eta_{UIM} = \frac{A_{UIM}^{(\text{"no" sys. error})}}{A_{UIM}^{(\text{w/ sys. error})}} = \frac{A_{UIM}^{(\text{well-compensated})}}{A_{UIM}^{(\text{poorly-compensated})}} = \sum_{ii} \frac{[C_{ii}^{fit}]^{-1} C_{ii}^{meas}}{[C_{ii}^{foton}]^{-1} C_{ii}^{meas}} = \sum_{ii} \frac{C_{ii}^{foton}}{C_{ii}^{fit}}$$

# I.7 Fit per Coil >> Error in $A_{UIM}$ : Model

- But wait! Remember the whole reason we got in to this game was to find out what error was caused by \*switching\* from State 1 to State 2,
- So we should also compute





$$\frac{\eta_{UIM}|_2}{\eta_{UIM}|_1} = \frac{\sum_{ii}(C_{ii}^{foton}/C_{ii}^{fit})|_2}{\sum_{ii}(C_{ii}^{foton}/C_{ii}^{fit})|_1}$$

such that we'll know, not only the systematic error under “normal” operation (i.e. in state 1), but also during this Nov 27 – Dec 03 2019 time period.





$$A_{UIM}^{(\text{“no” sys. error})}(\text{most times}) = \eta_{UIM}|_1 A_{UIM}(\text{20200113 Model})$$

$$\begin{aligned} A_{UIM}^{(\text{“no” sys. error})}(\text{Nov 27 – Dec}) &= \eta_{UIM}|_2 A_{UIM}(\text{Nov 27 – Dec 03}) \\ &= \eta_{UIM}|_1 \left( \frac{\eta_{UIM}|_2}{\eta_{UIM}|_1} \right) A_{UIM}(\text{20200113 Model}) \end{aligned}$$
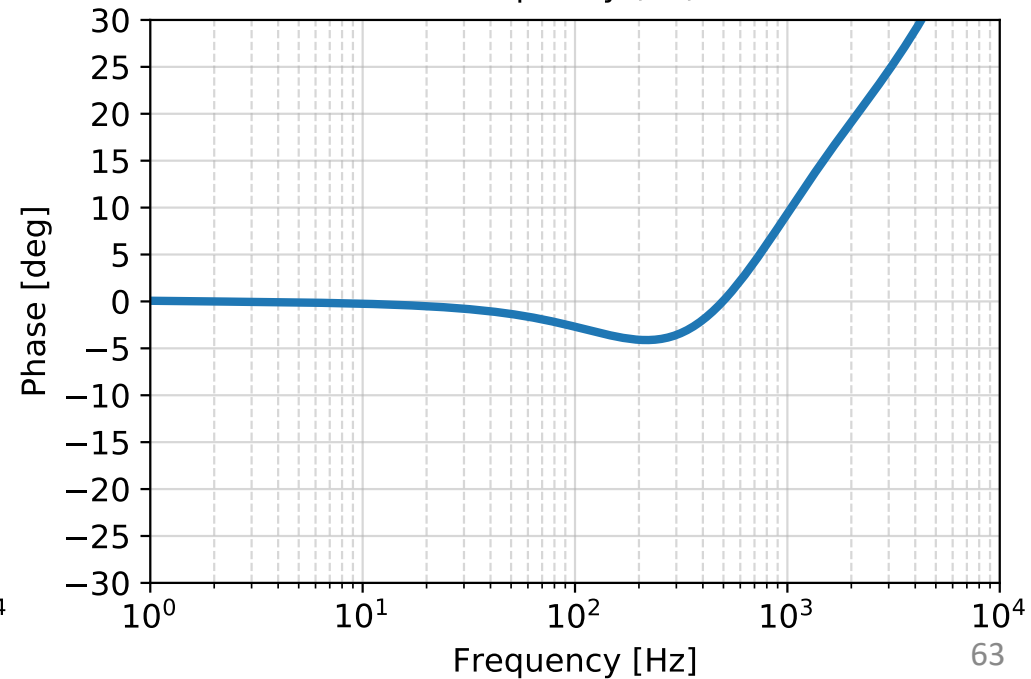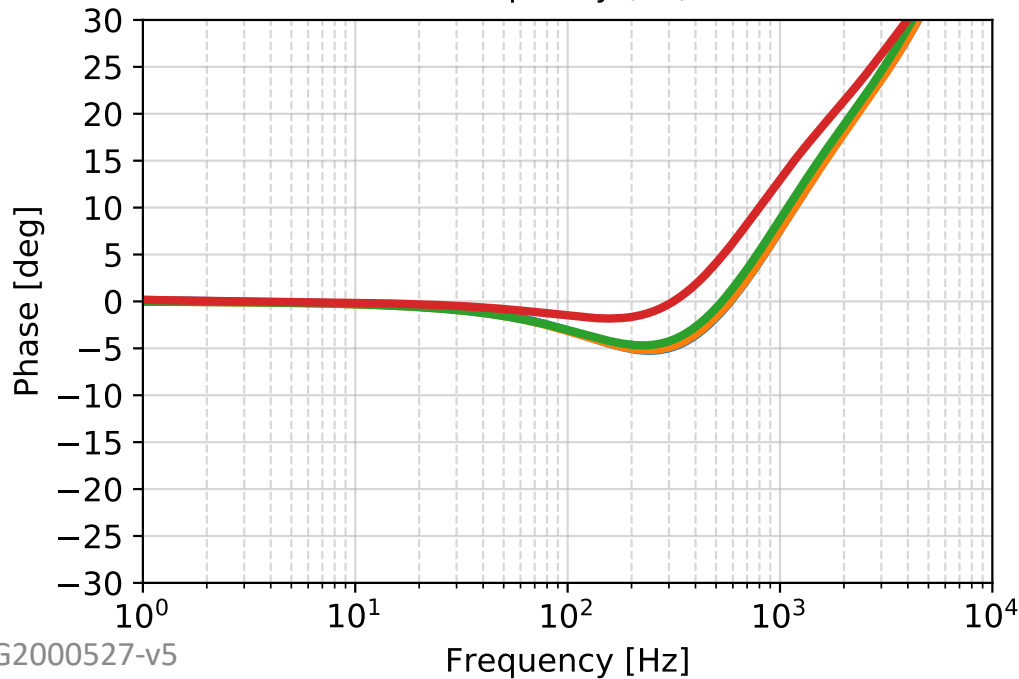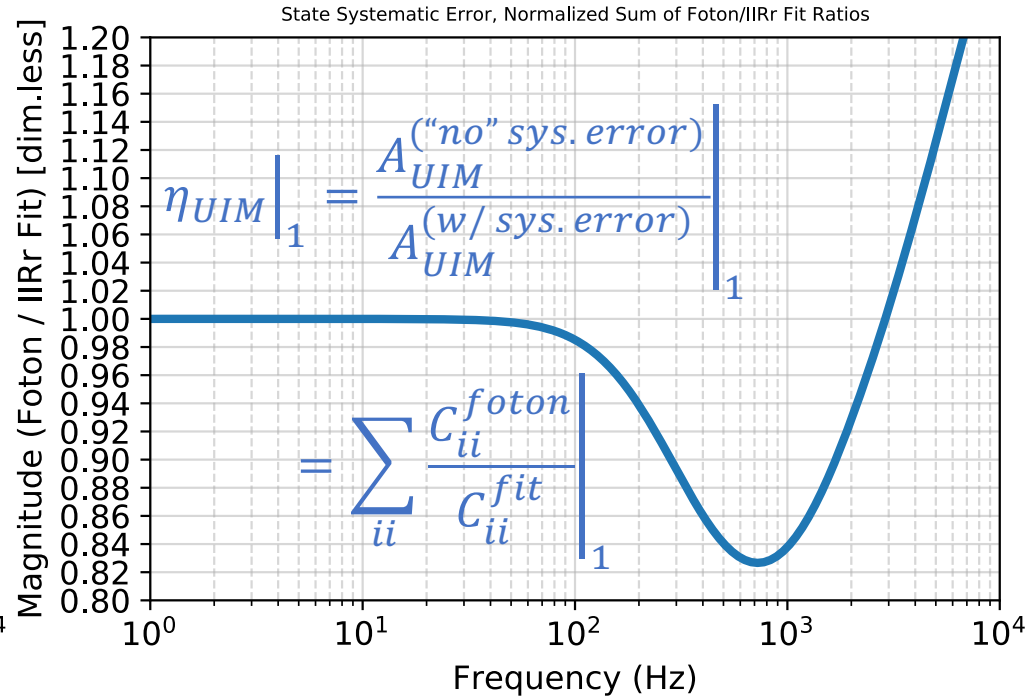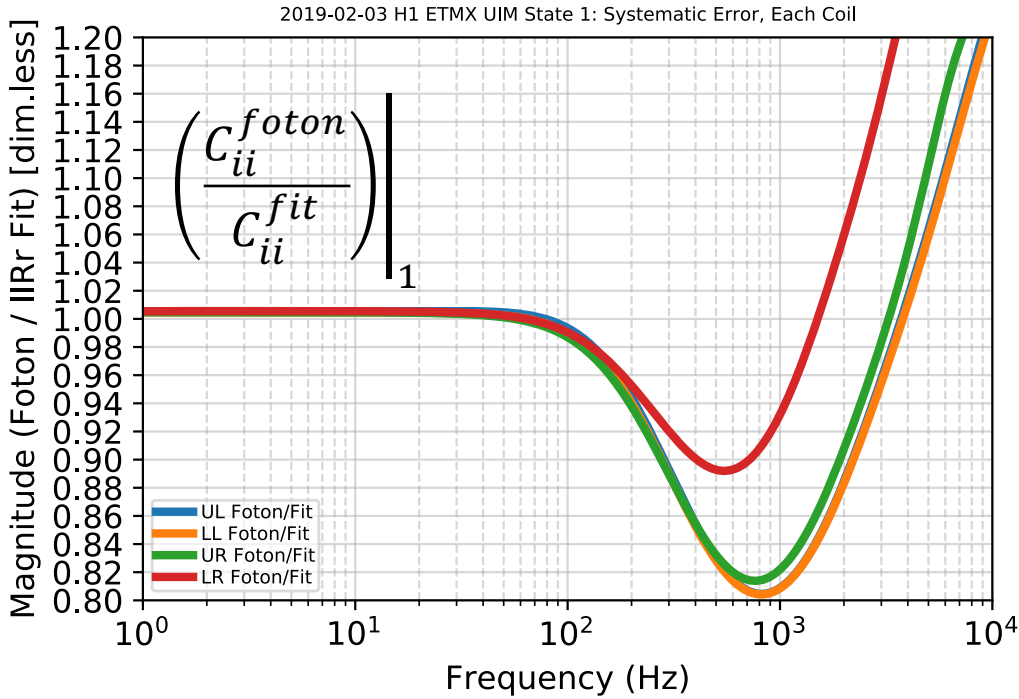
# I.7 Fit per Coil >> Error in $A_{UIM}$ : State 1 Results






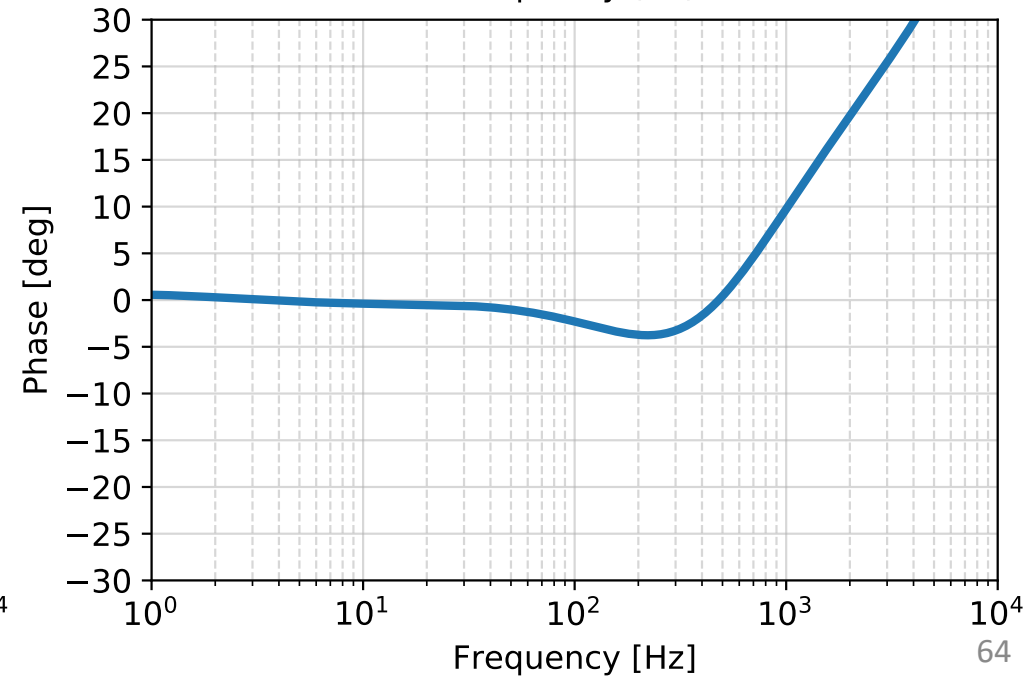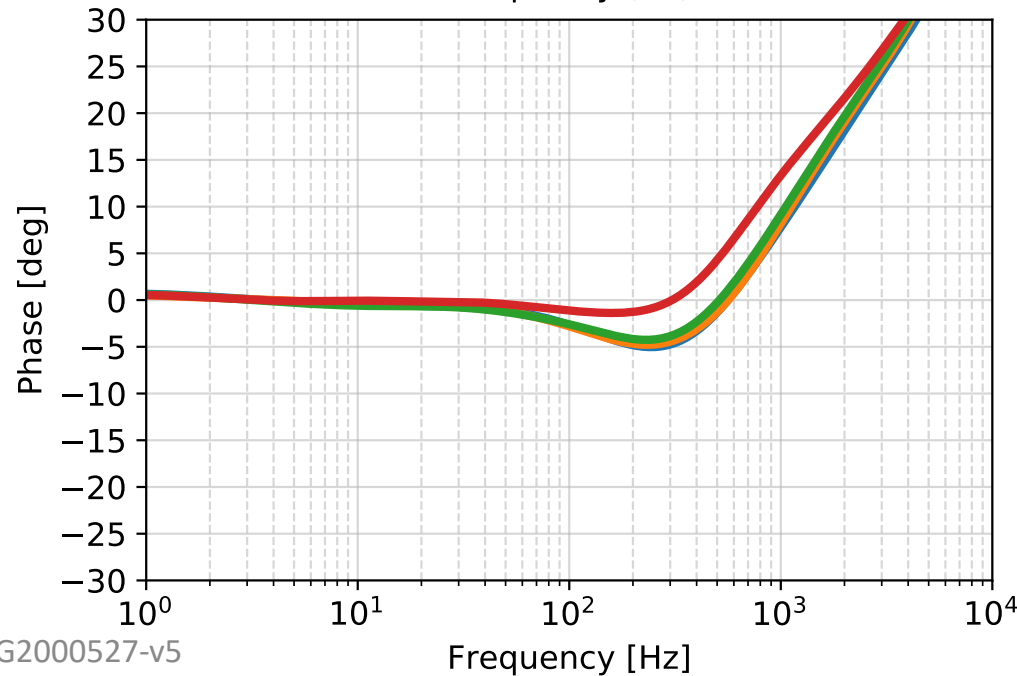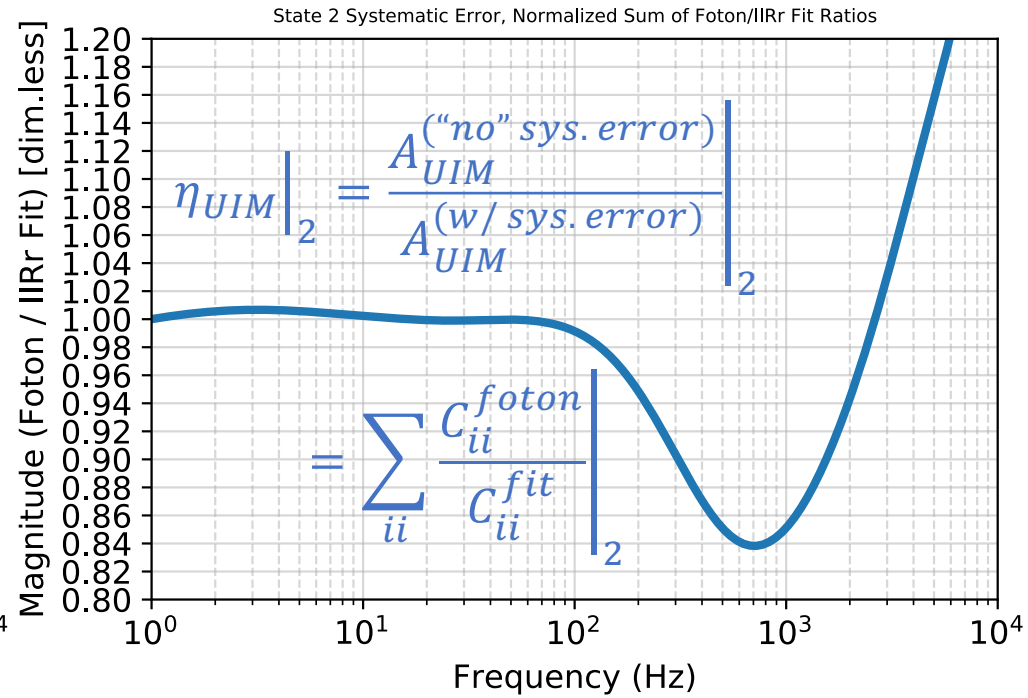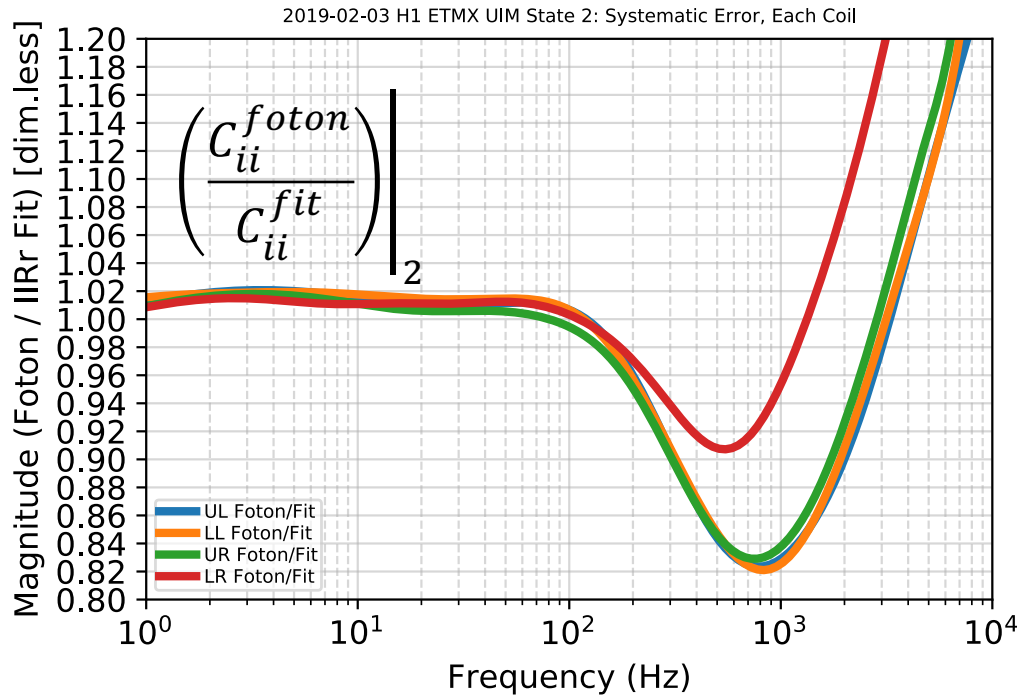
# I.7 Fit per Coil >> Error in $A_{UIM}$ : State 2 Results





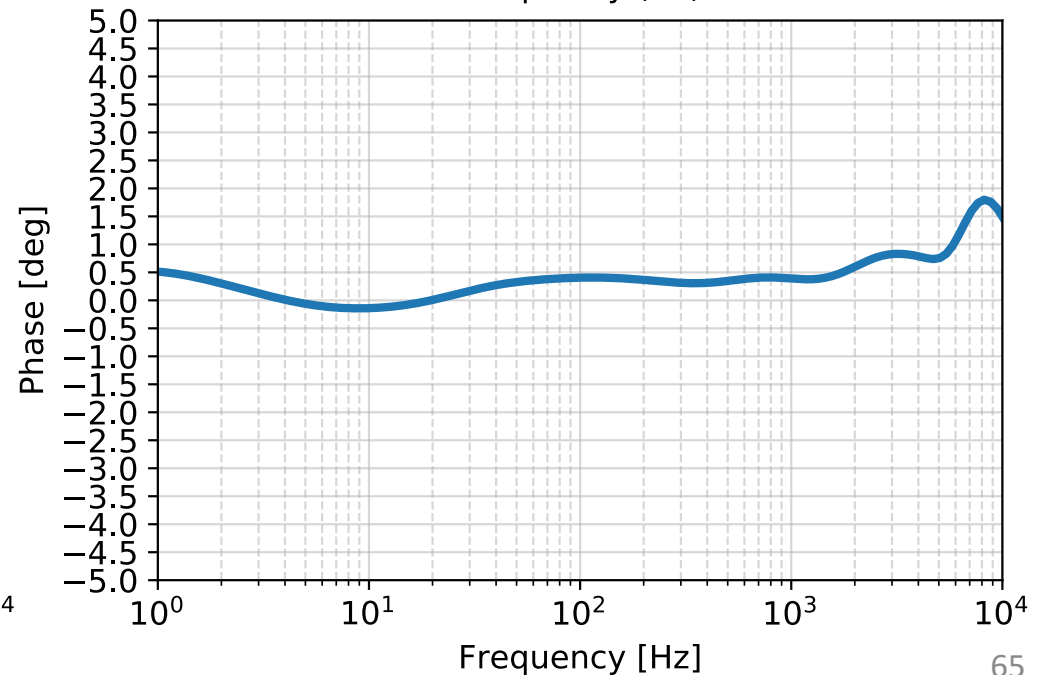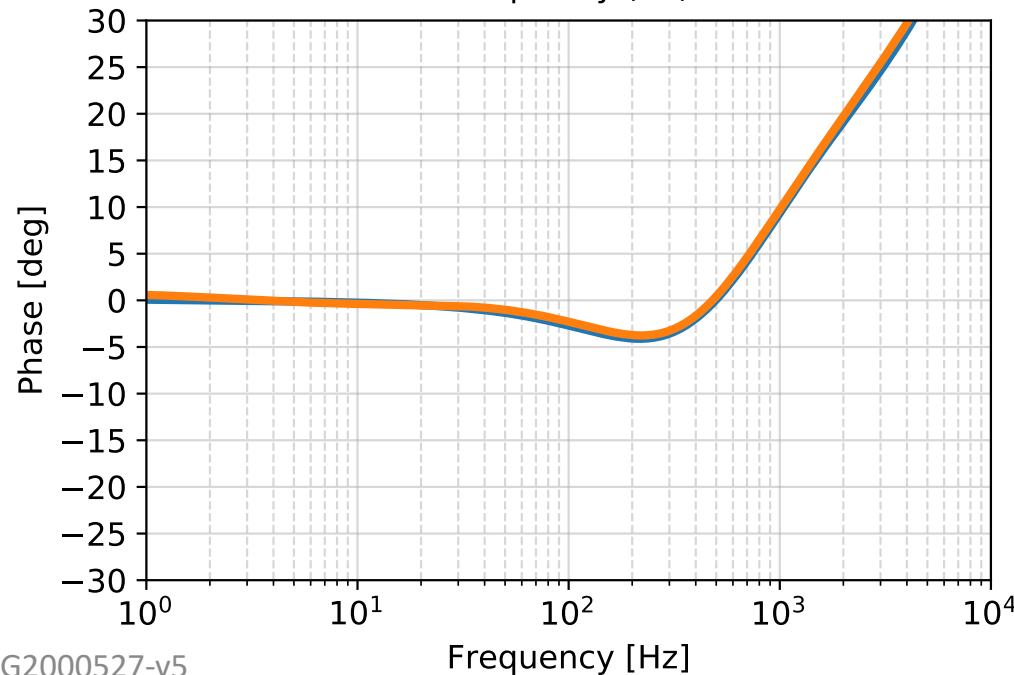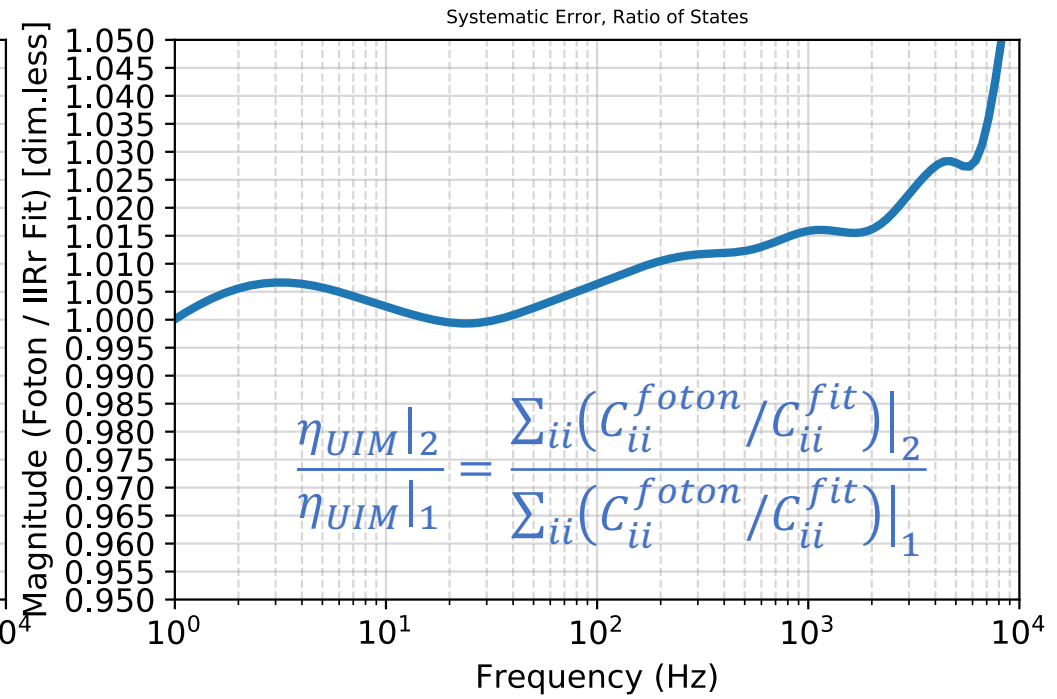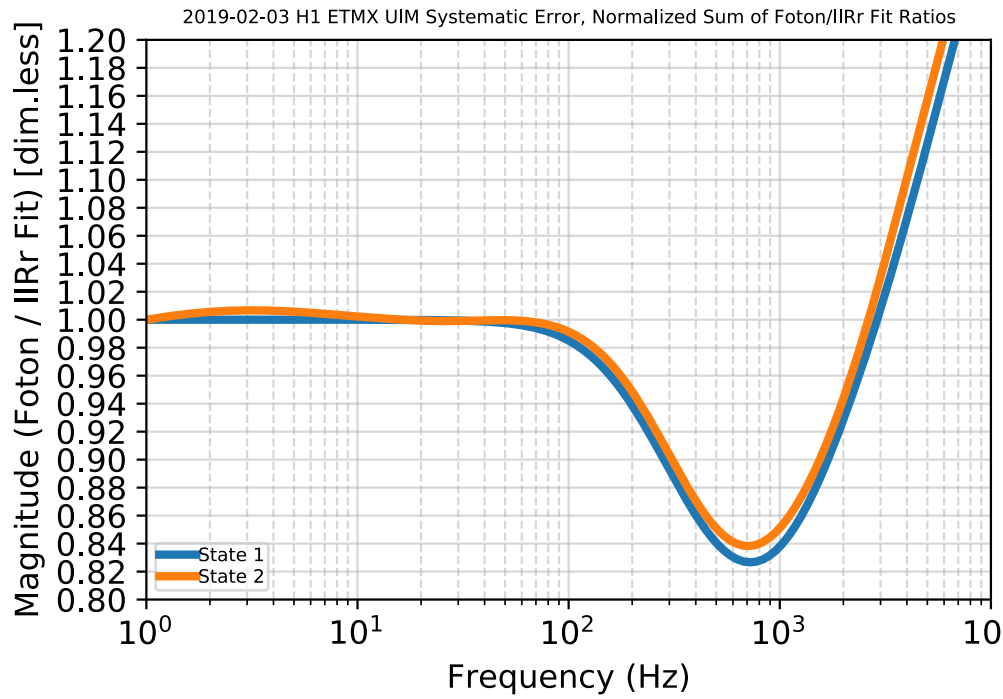
# 1.7 Fit per Coil >> Error in $A_{UIM}$ : Results Compared



# 1.7 Fit per Coil >> Error in $A_{UIM}$ : Discussion

- Huh! So – it looks like the error in State 1 compensation is really of much more concern than the switch between State 1 and State 2 for a short time period.
- That's pretty much it. At least all of this careful study was worth it for some reason.
- On to showing how this manifests in the response function!
- **But also – do remember that this is based on fits of data that doesn't make sense. So hold these truths to be full of salt grains until we get a better measurement.**

$$\eta_{UIM} \Big|_1 = \frac{A_{UIM}^{("no" \text{ sys. error})}}{A_{UIM}^{(w/ \text{ sys. error})}} \Big|_1$$






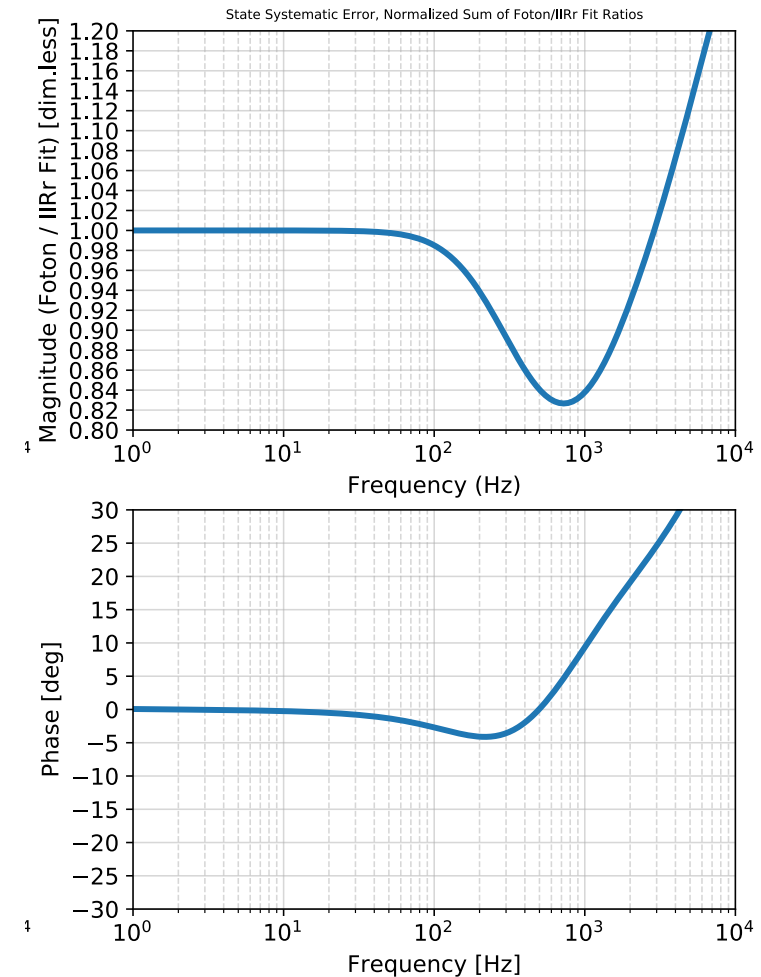


# I.7 Sys. Err in $A_{UIM}$ Recap

But, if we believe the measurement, is this error big w.r.t. other errors in the UIM?

Yeah – it kinda is!

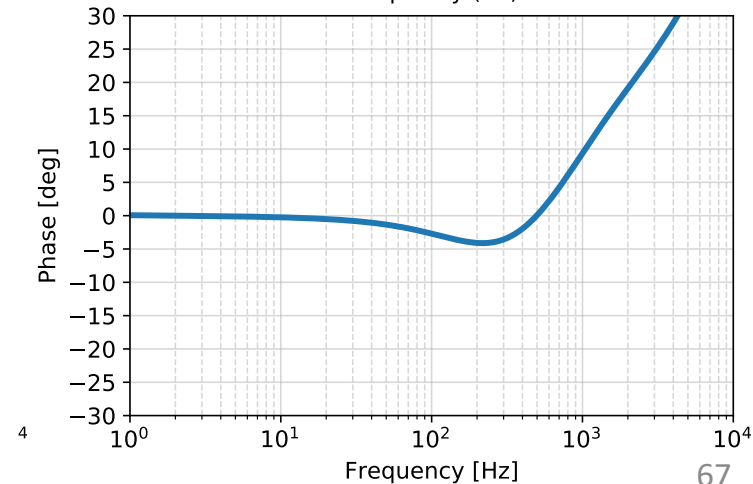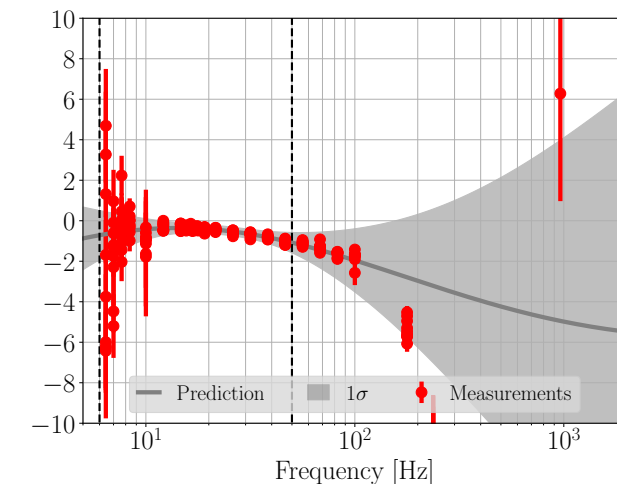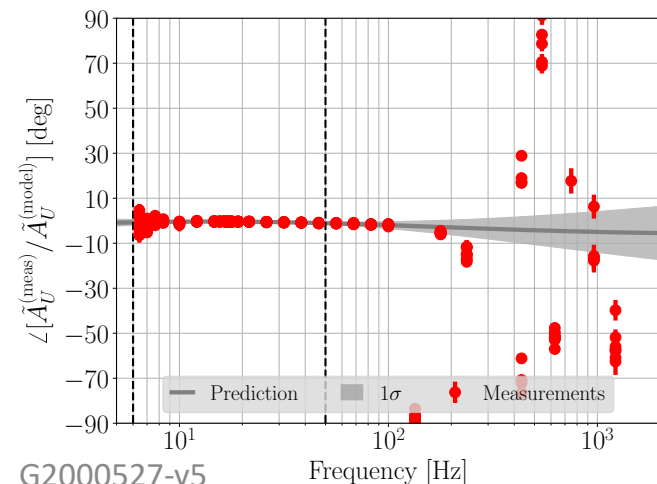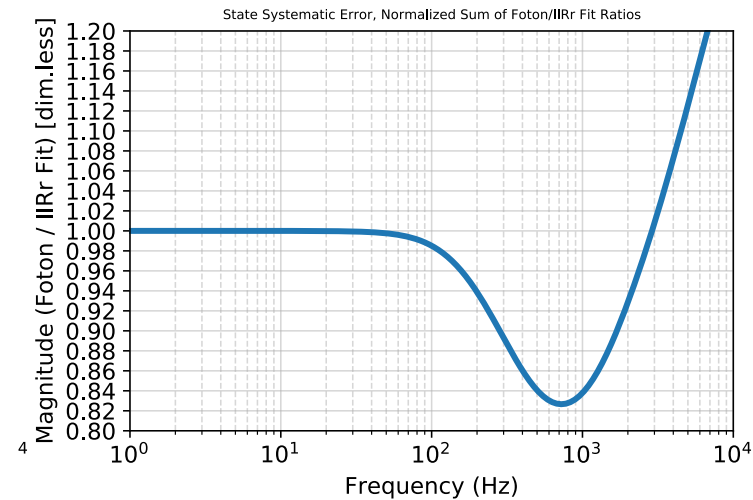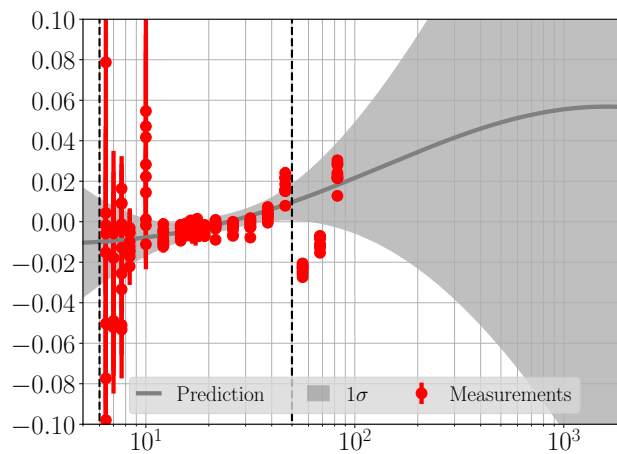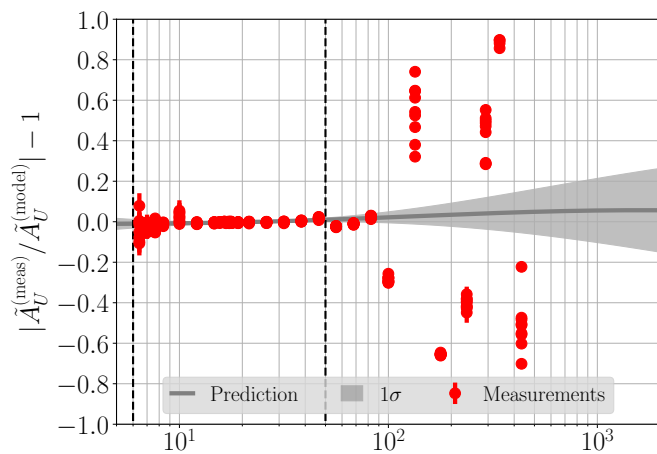Namely – the blade spring bending nonsense completely fools the GPR above 50 Hz. So this kind of smoothly varying function just would not be found in / “accounted for with” the GPR. So, we’re stuck having to model it all and estimate the impact on the Response Function systematic error.



# Outline

Two Parts, each quite long. \*sigh\*

## PART I: The ETMX UIM Driver, from Nov 27 to Dec 03 2019

1. Why do you care about the UIM?
2. Review where we were before we started
3. Review of the Circuit
4. The Measurement
5. Other models of the circuit
6. The Fit and Each Coil Result
7. Converting fit results in to systematic error in  $A_{UIM}$
- 8. Converting sys error in  $A_{UIM}$  to sys error in R and Conclusions**

## PART II: The OMC Whitening Chassis, from Mar 16 to 27 2020

# I.8 Converting Sys. Err in $A_{UIM}$ to that in $R$


- Hey! We wrote a paper on this! Check out Eq. 11 in [P1900245](#):

$$\tilde{\eta}_{R;A_i} = \frac{1}{R(\text{model})} \left[ \frac{1}{C(\text{model})} + \left( \tilde{\eta}_{A_i} \tilde{A}_i^{(\text{model})} + \sum_{j \neq i} \tilde{A}_j^{(\text{model})} \right) \tilde{D} \right]$$
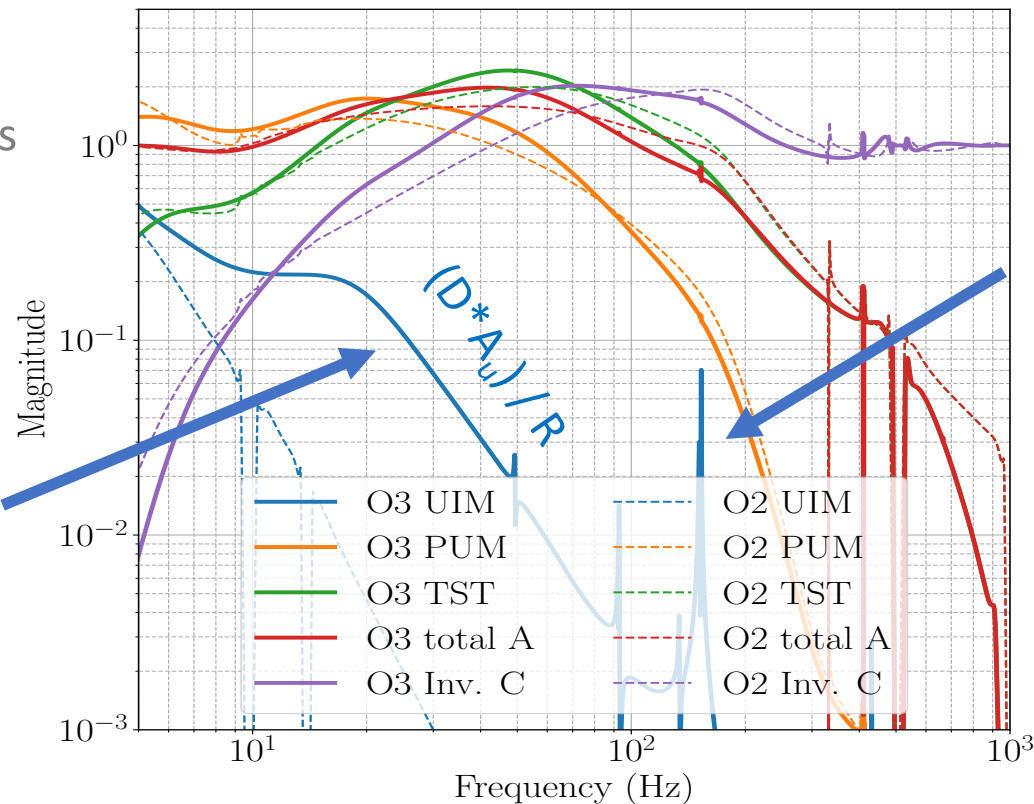
## H1 O3

Error contributions to the response function recapped from Slide 6



UIM Contributes at the ~10% level out to ~25 Hz



Vertical Blade Spring Twisting / Bending in L direction causes UIM contribution to spike back in to play at 150 Hz
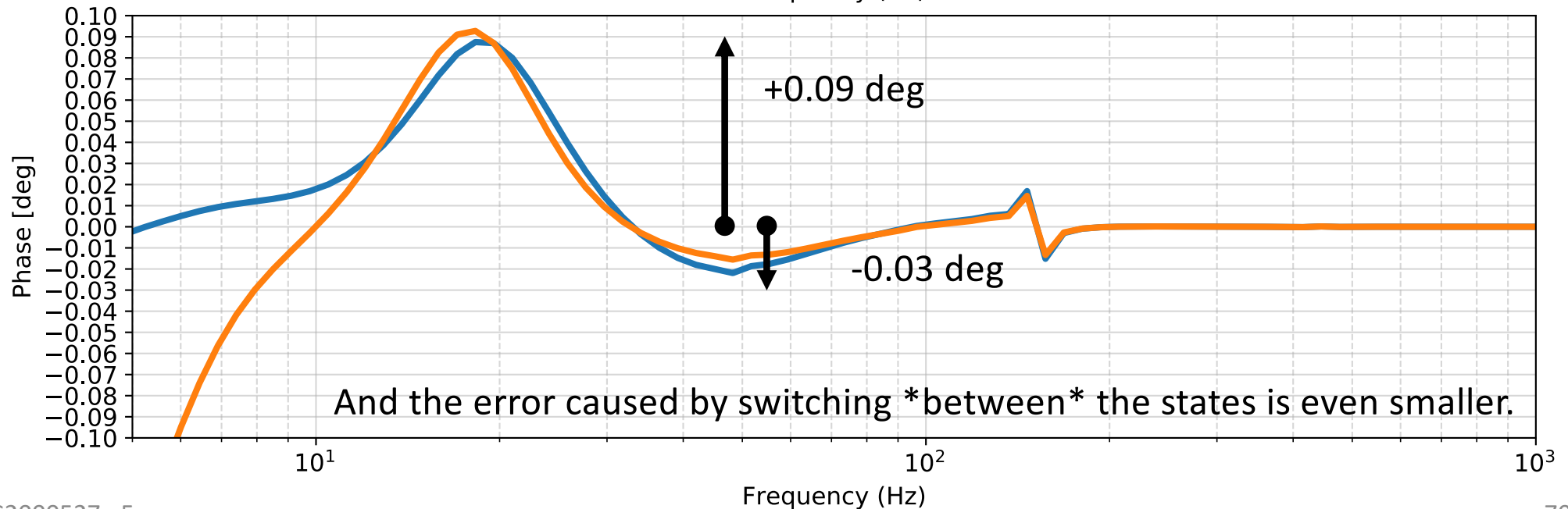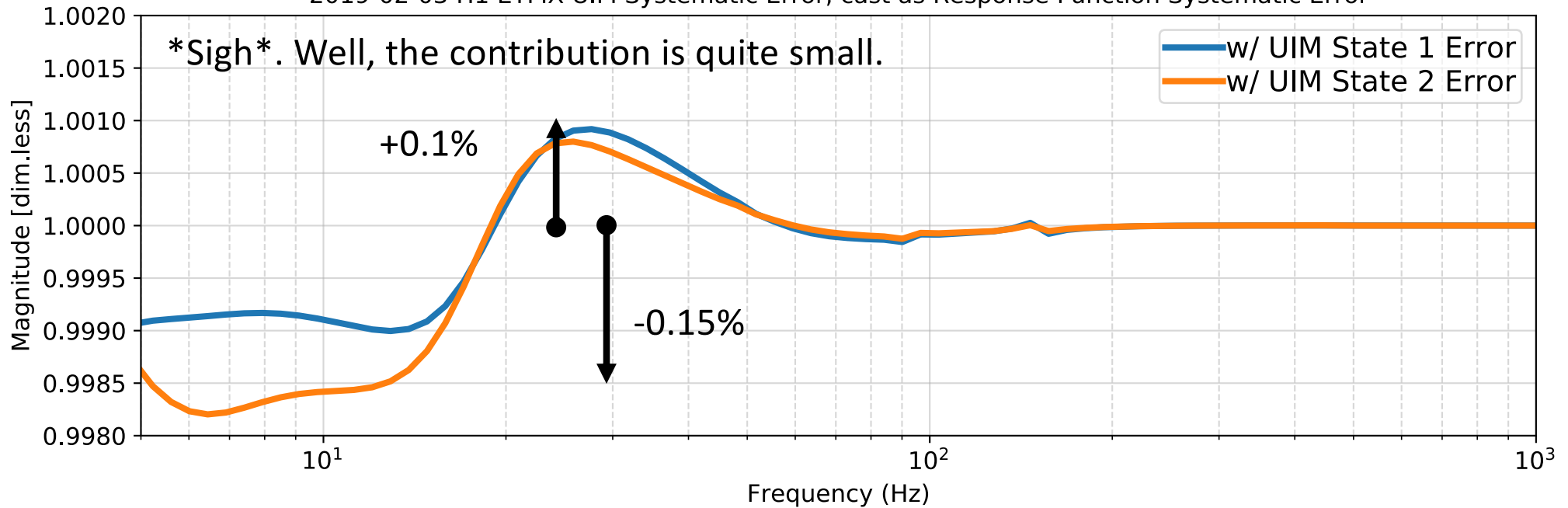
# I.8 Sys. Error R as a result of $A_{UIM}$ Error

2019-02-03 H1 ETMX UIM Systematic Error, cast as Response Function Systematic Error



# I.8 UIM Electronics Error Conclusions

- **The executive summary:** non-Jeff's everywhere whom guessed the answer ahead of time are vindicated in that the UIM electronics error -- either from differences in compensation between states, or poor compensation in general – doesn't substantially contribute to the response function systematic error.
- We may safely proceed with O3B chunk 1 uncertainty budget development without including this systematic error.
  - Note that this would have \*not\* been “covered” by the GPR even if it were non-negligible.
- BUT: we've now learned many valuable lessons about:
  - How to take the right measurement of a coil driver
  - How to make sense of a fit to data using rough analytic expectations from converting a circuit diagram into a collective transfer function
  - How bad the compensation is for the UIM driver response
  - How to propagate electronics errors to the response function