


OMC DCPD Whitening Chassis Design Update

Oct 2022
R. Abbott, J. Kissel, D. Schaetzl
G2201909

ADC Noise Model Validation


Meas: Sampled at 524 kHz, 50 Ohm terminated at AA

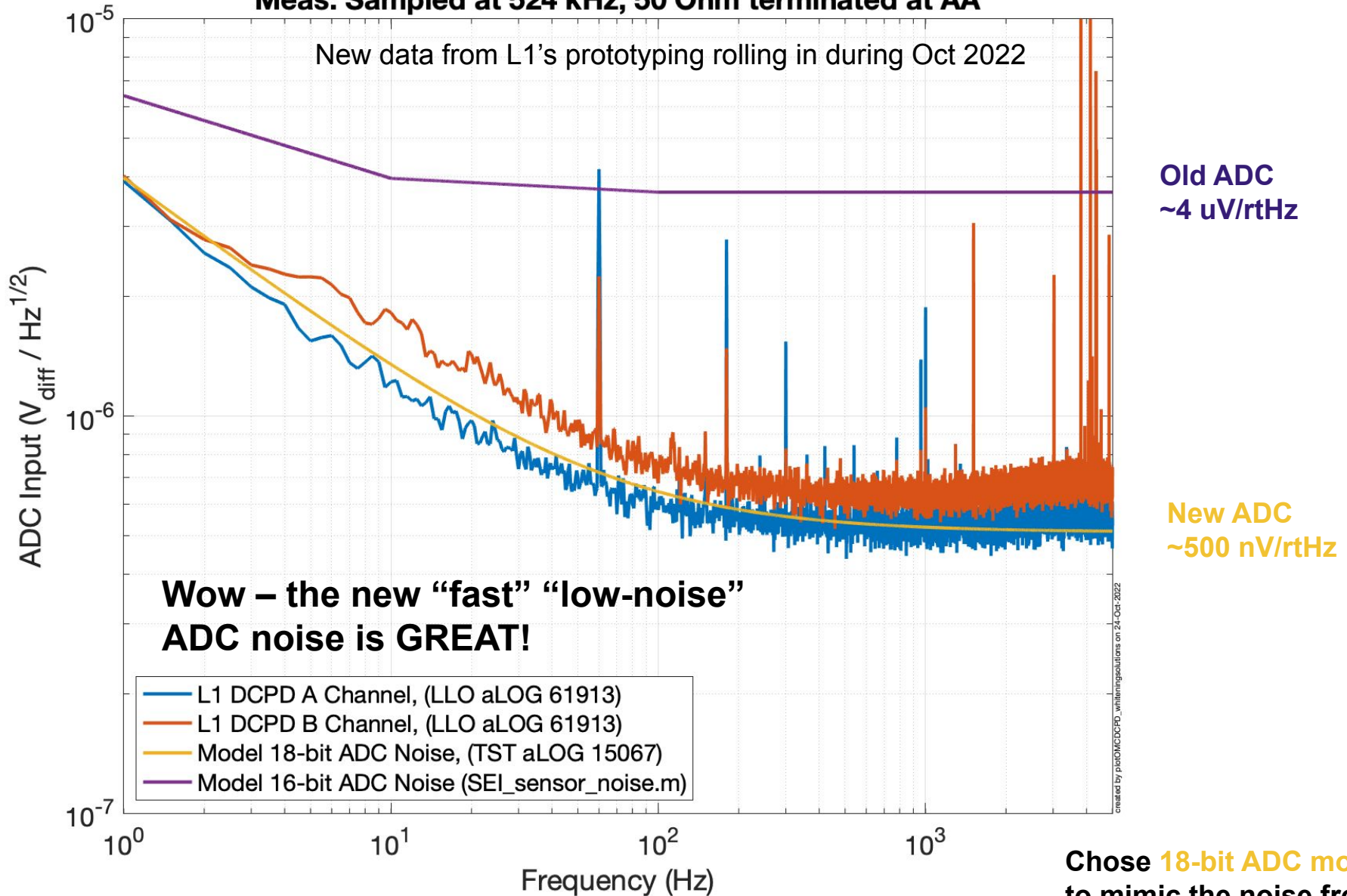New data from L1's prototyping rolling in during Oct 2022



Chose **18-bit ADC model** to mimic the noise from TST:15067, which is similar to DCPD A channel

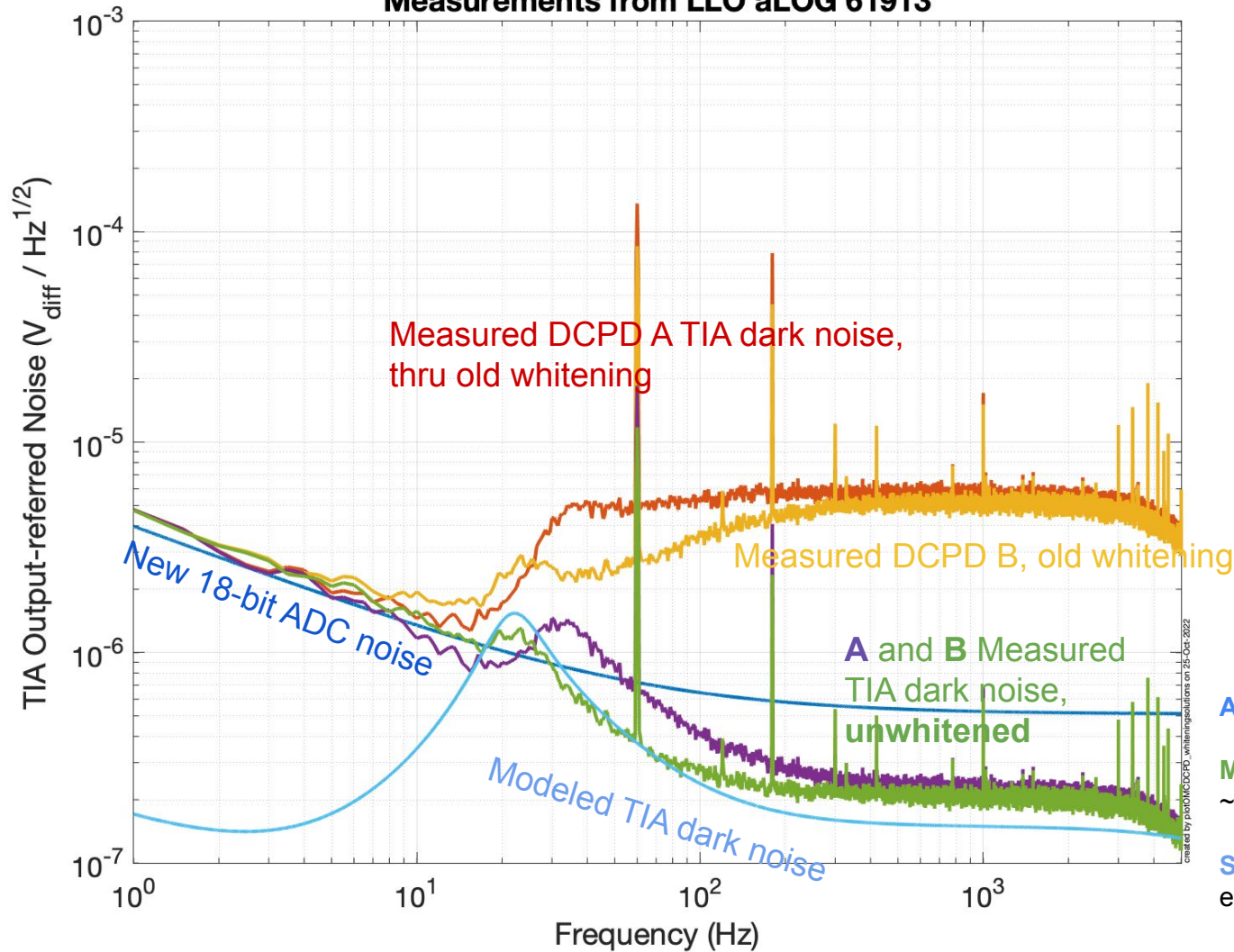Output Reference Noise Model Validation Measurements from LLO aLOG 61913




ADC noise is ~500 nV/rHz,
Measured new TIA dark noise is
~200 nV/rHz
Spice model TIA dark noise
estimates ~150 nV/rHz

Spice model agrees with measured data for TIA output referred electronics self noise, aka “dark” noise.

Some whitening is needed. Measured noise is higher than model, so whitening solution that works for the model should work for measured.

Design Goal: Don't spoil "the" signal-to-noise ratio!

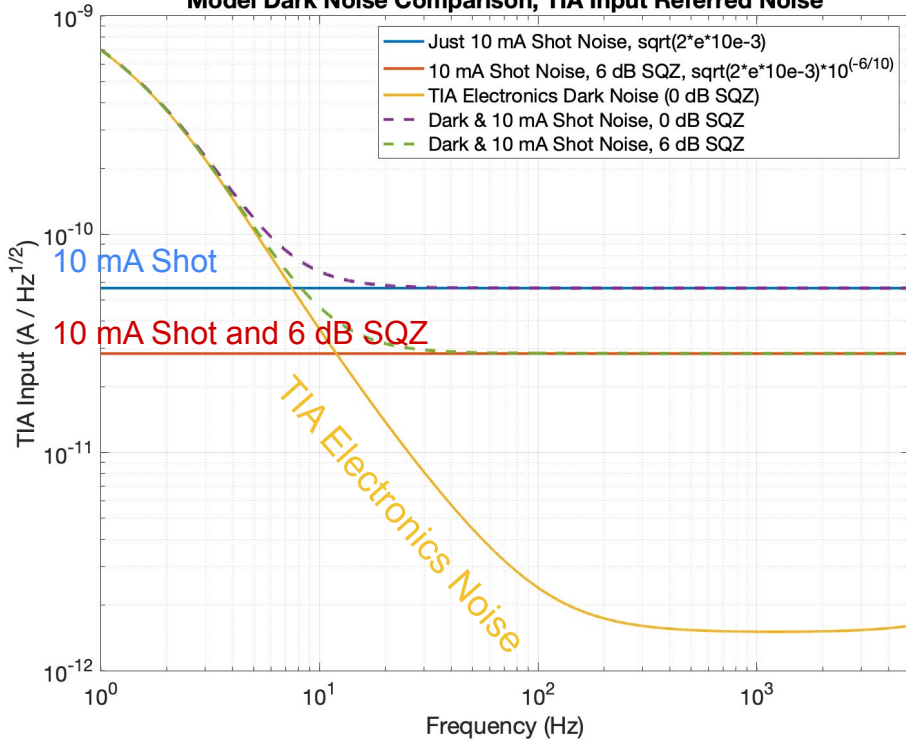Model Dark Noise Comparison, TIA Input Referred Noise




So – what is the “**signal to noise**” ratio we’re trying to preserve?

“10 mA worth of Shot Noise” = $\sqrt{2 \cdot e \cdot [10e-3 \text{ mA}]} = 5.6e-11 \text{ [A/rtHz]}$

Use spice model to estimate the *input* referred **electronics noise**, in A/rtHz.


“**Dark**” **electronics noise** is the same regardless of input, but “signal” will be different between squeezing and no squeezing.

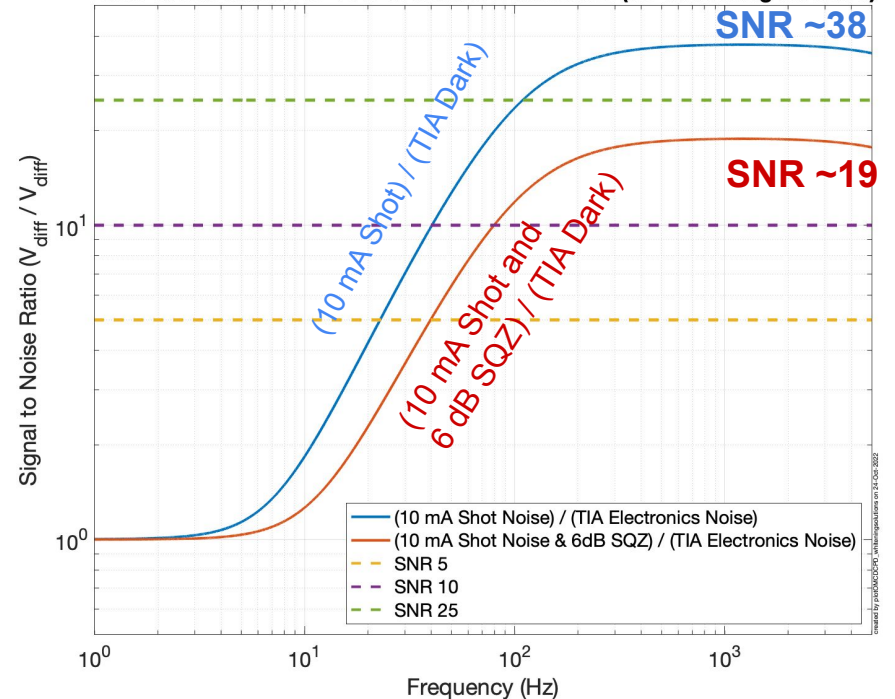Ratio of Shot Noise to TIA Electronics Dark Noise (No Whitening Involved)



No model is perfect, and getting this right to the factor of 2 level is hard. We carry around the “6 dB SQZ” curves also representative of the TIA electronics noise, or ADC noise being larger than models, also degrading the SNR.

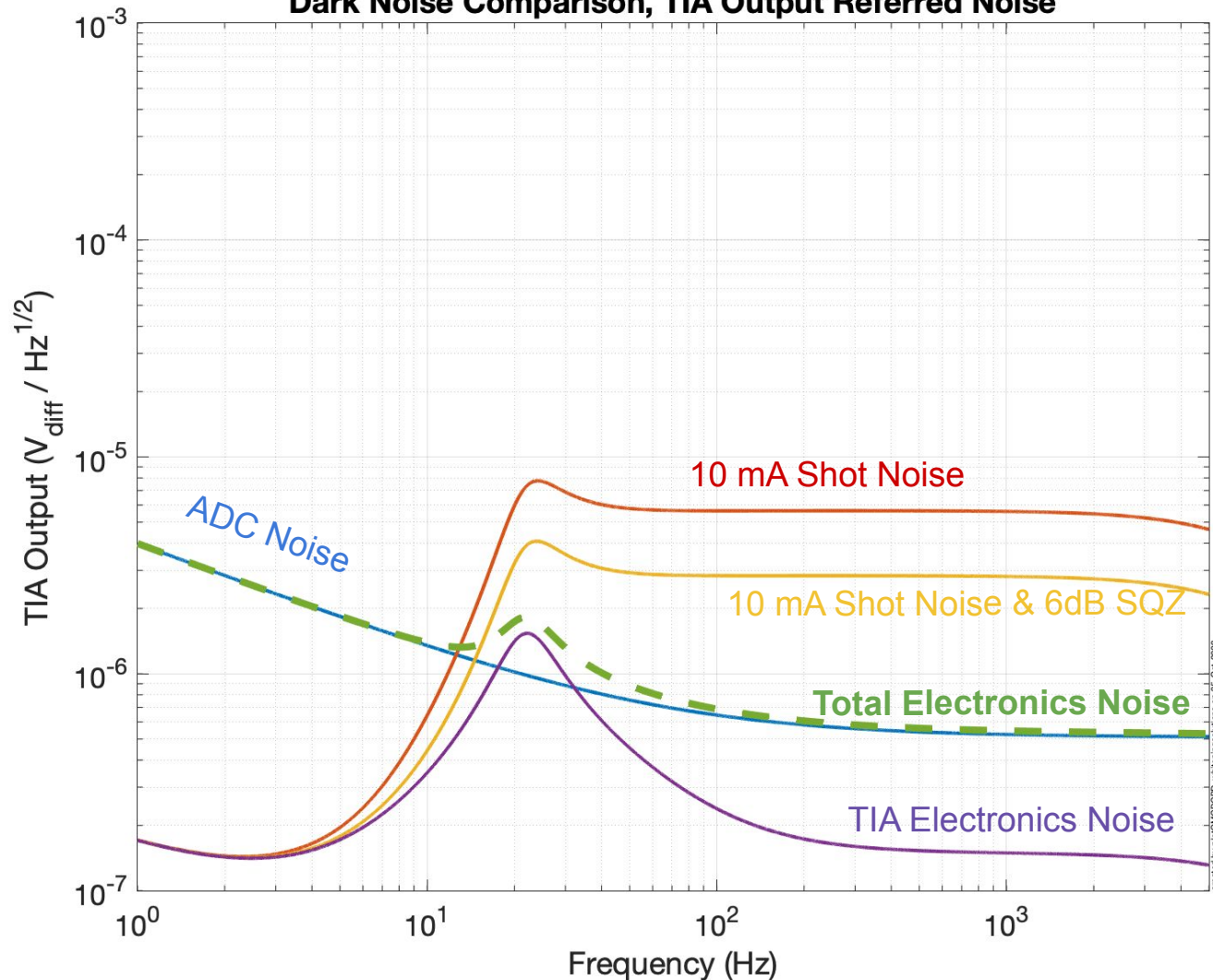Dark Noise Comparison, TIA Output Referred Noise



Back to **TIA output-referred voltage noise** metric.

We assume **spice model TIA dark noise** is representative.

Add two examples of **shot noises** to demonstrate the “signal” part of SNR.

Add **total electronics noise** for the “noise” part of SNR.


If no whitening as shown here, then **ADC noise** dominates the **total electronics noise**

(No whitening was incorrectly suggested in G2201909-v1)

We don't want this (no whitening gain).

Must have *some* whitening gain to surpass ADC noise.

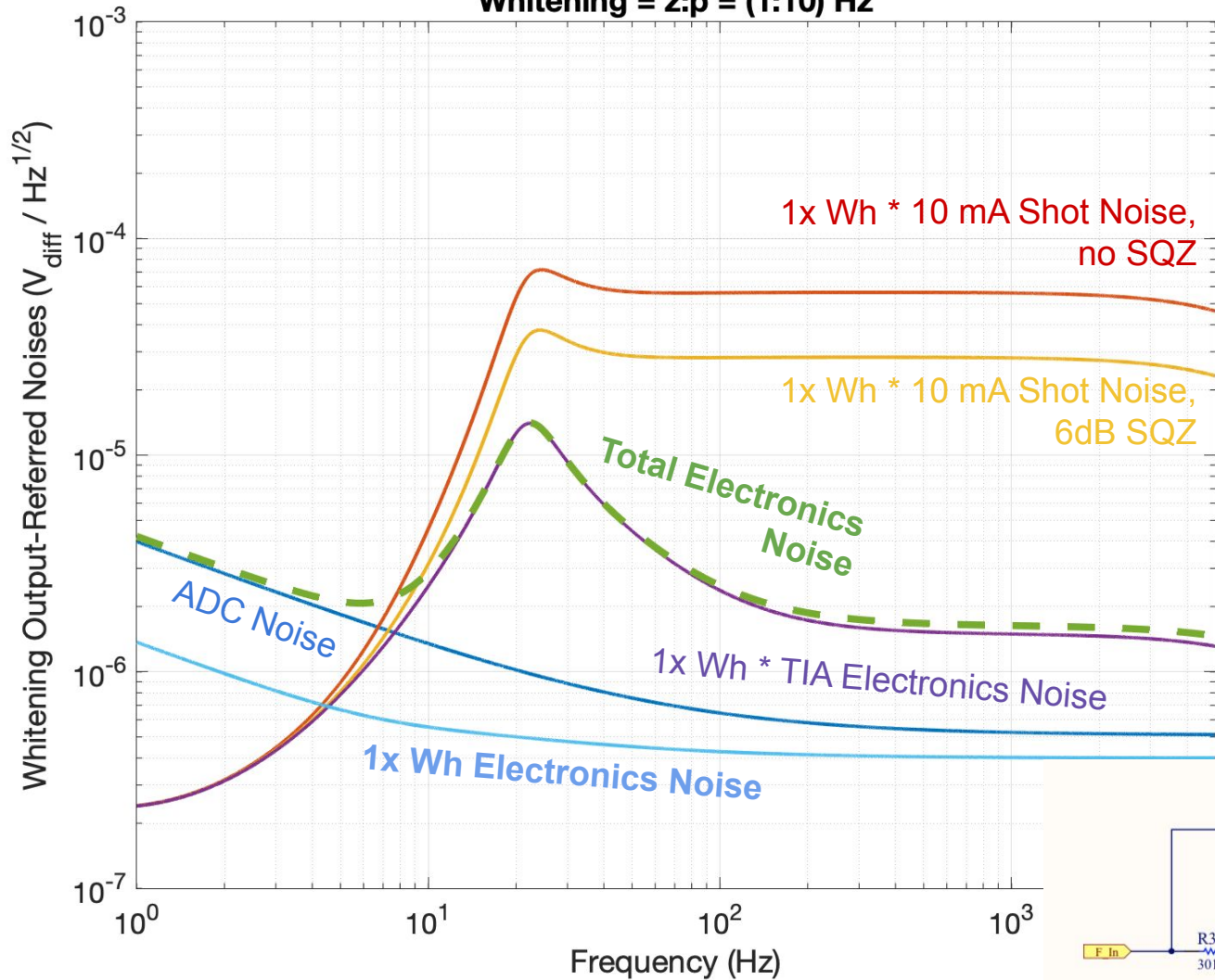Dark Noise & Shot Noise Comparison, Whitenized Whitening = z:p = (1:10) Hz




“Just use what we had in O3.”

If we apply the “battle-tested” design of a single z:p = 1:10 Hz filter that’s used in the majority of ISC whitening chassis ([D1001530](#) page 4),


Then **1x Wh * TIA electronics noise** is above **ADC noise**, and **ADC noise** is only a small contributor to the **total electronics noise**.

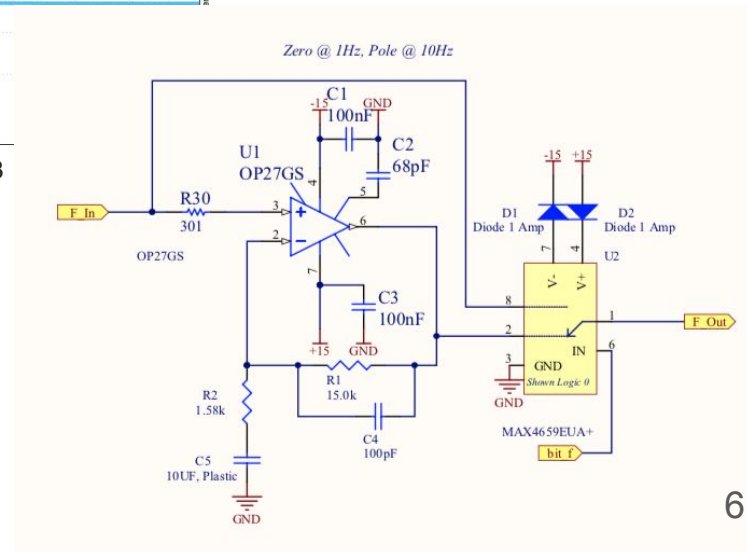This will do nicely.
How about our SNR metric?



Dark Noise & Shot Noise Comparison, Whitened

Whitening = z:p = (1:10) Hz

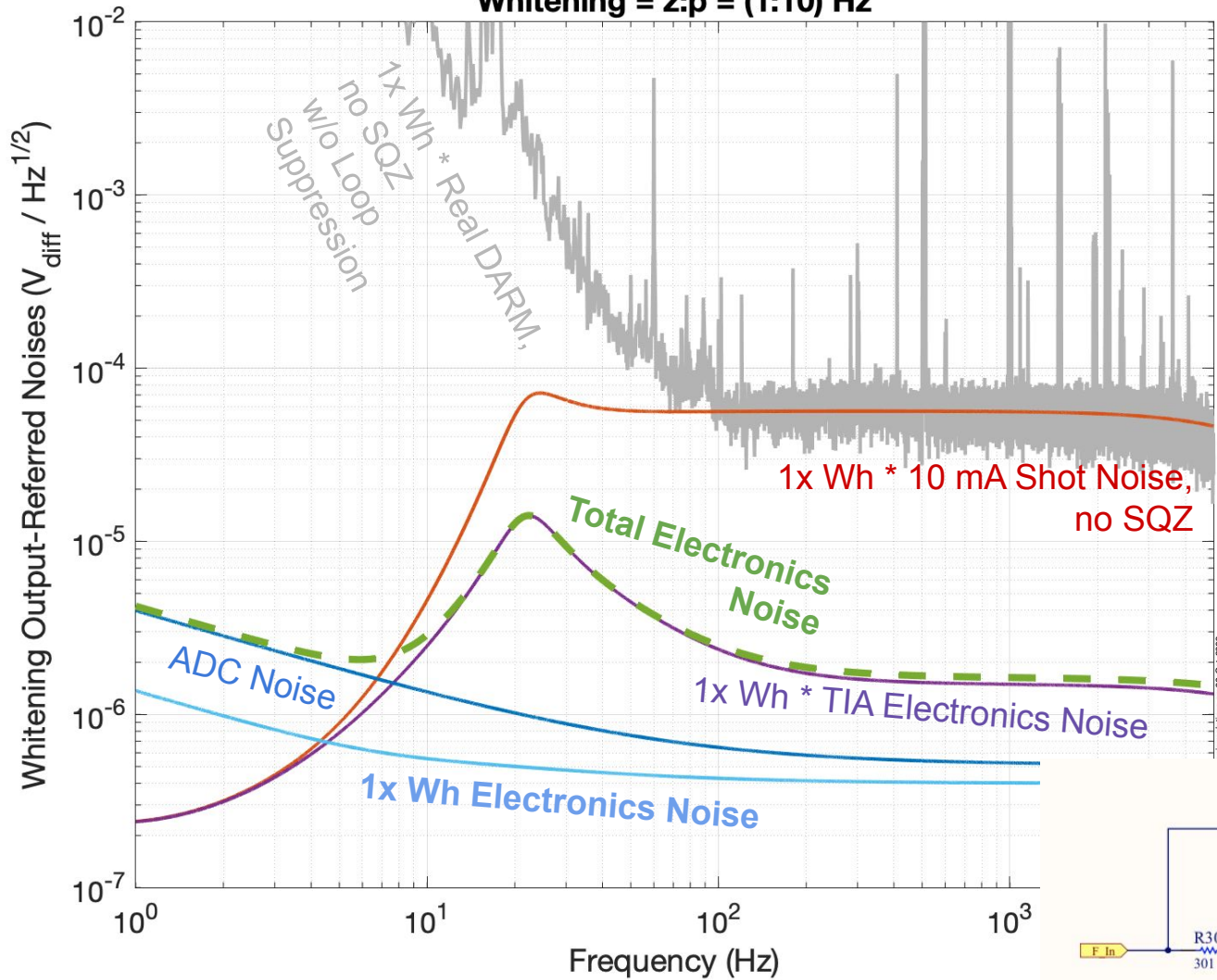


“Just use what we had in O3.”


If we apply the “battle-tested” design of a single z:p = 1:10 Hz filter that’s used in the majority of ISC whitening chassis ([D1001530](#) page 4),

Then **1x Wh * TIA electronics noise** is above **ADC noise**, and **ADC noise** is only a small contributor to the **total electronics noise**.

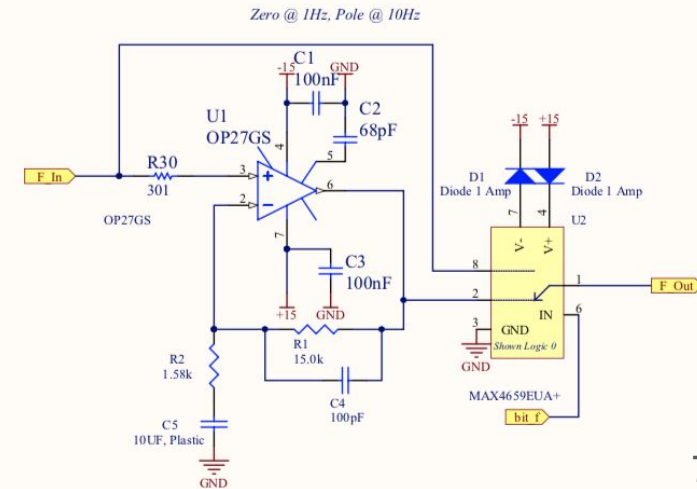This will do nicely.
How about our SNR metric?



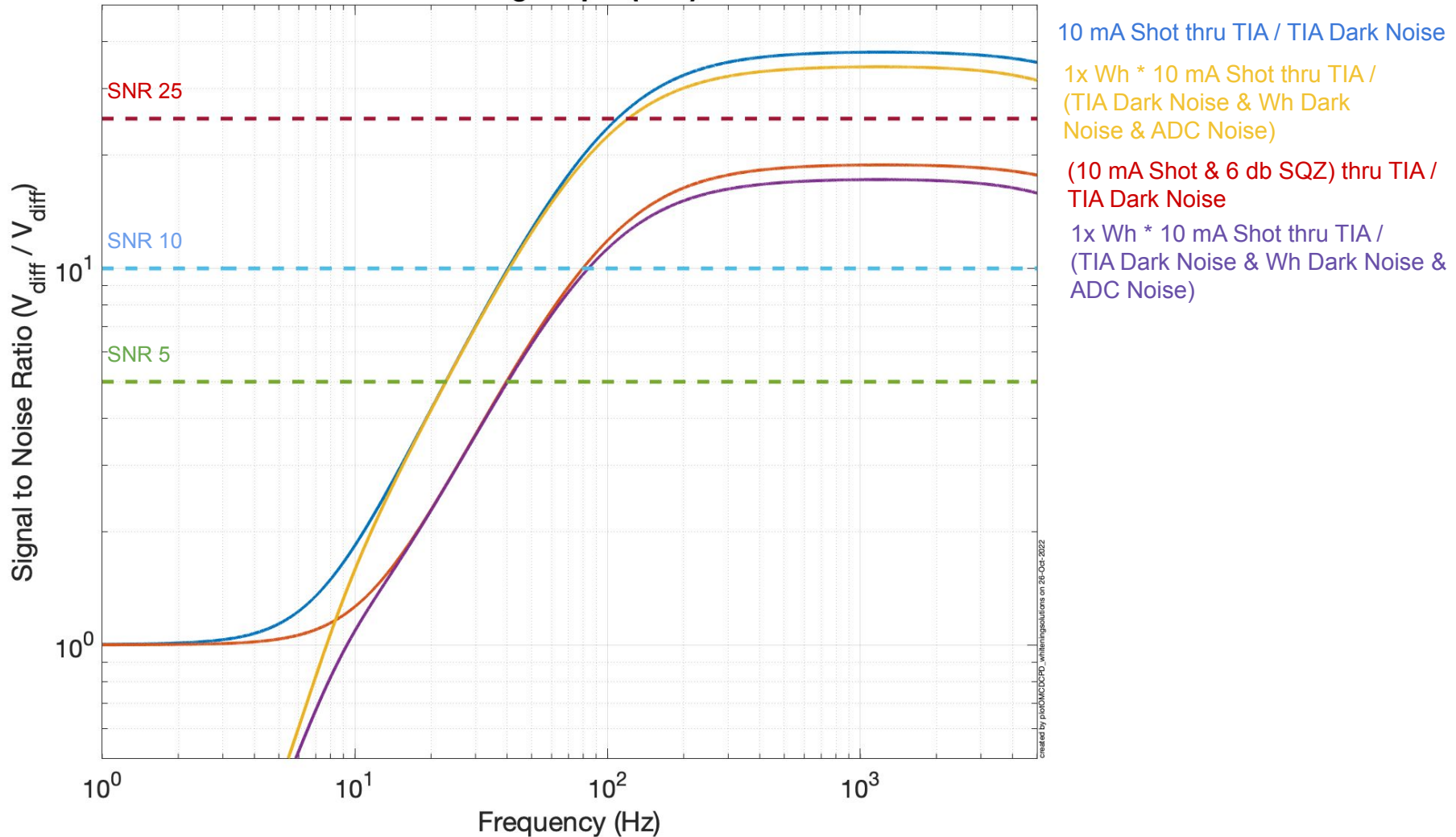Ratio of Shot Noise to Total Electronics Noise Whitening = z:p = (1:10) Hz



With 1x stage of (1:10) whitening, the ADC noise

- Reduces (10 mA) SNR at 1 kHz from **~38** to **~34**
- Reduces (10 mA & 6dB SQZ) SNR at 1 kHz from **~19** to **~17**

**1x (1:10) whitening is enough that ADC Noise does not dominate electronics noise,
Only slightly impacts SNR.**


As long as this SNR doesn't go below 10, then it's acceptable.

Saturation and Violin Modes


Connecting the dots of how this “**representative**” ASD chosen from 2022-09-04, corresponds to what we typically see.

RED DELTAL EXT trace is the data that I’ve grabbed as the representative trace.

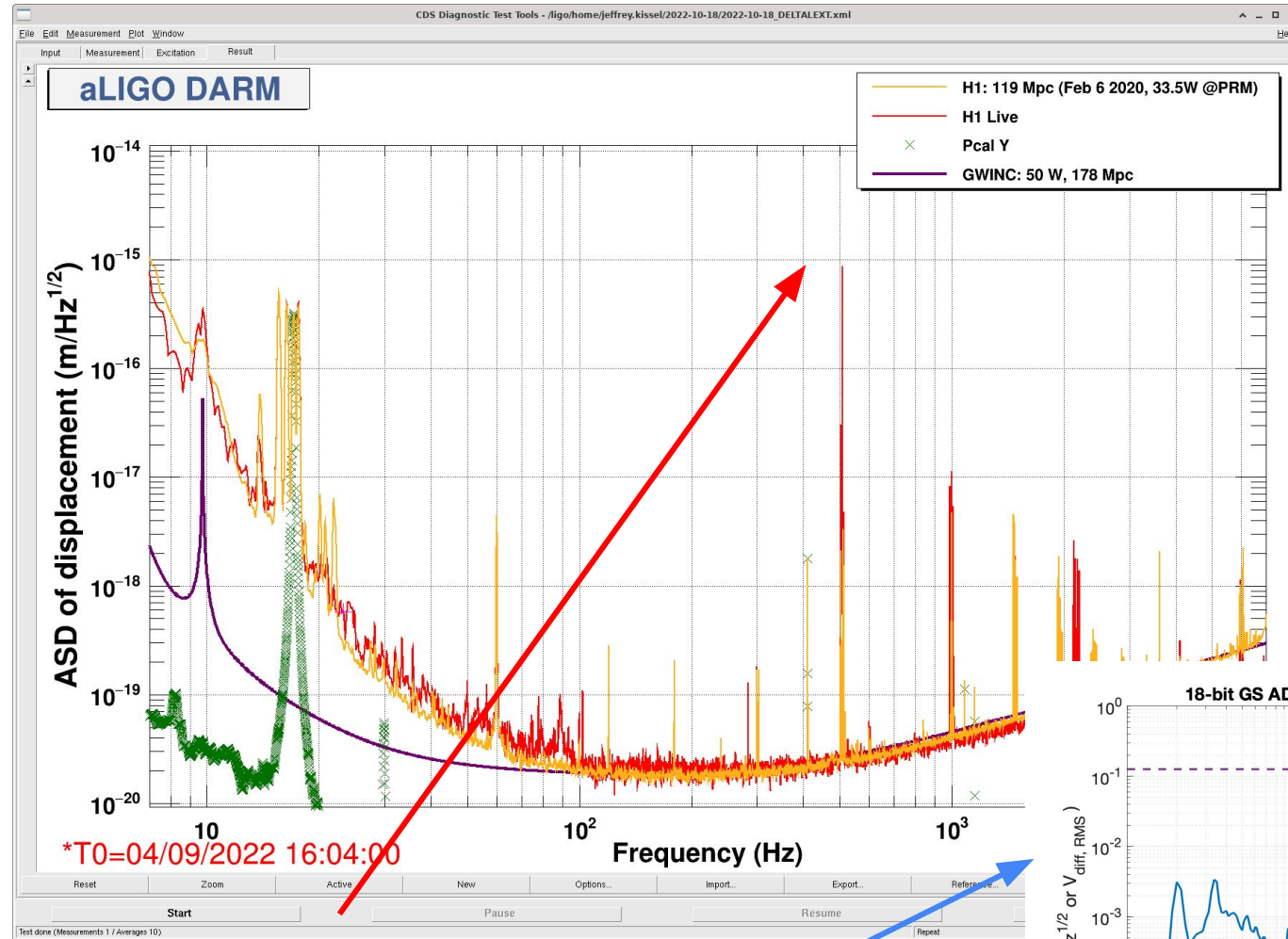YELLOW trace shows typical “good” O3 times, where the violins are several orders of magnitude lower.




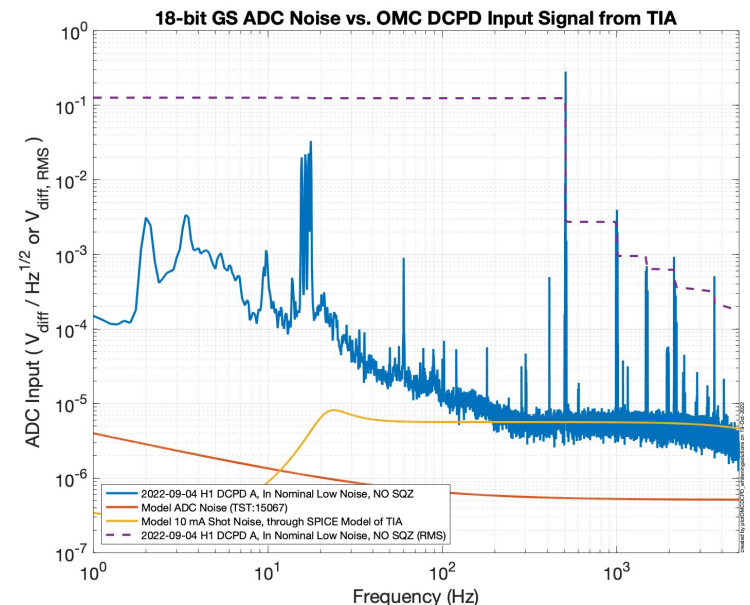When 500 Hz violins are around $\sim 1e-15$ [m / rtHz] in DARM, the current on DCPDs have peak voltage of 0.16 [V_{rms}] = ~ 0.2 [V_{peak}] out of the TIA.






Signal Chain Saturation Check

Whitening = z:p = (1:10) Hz

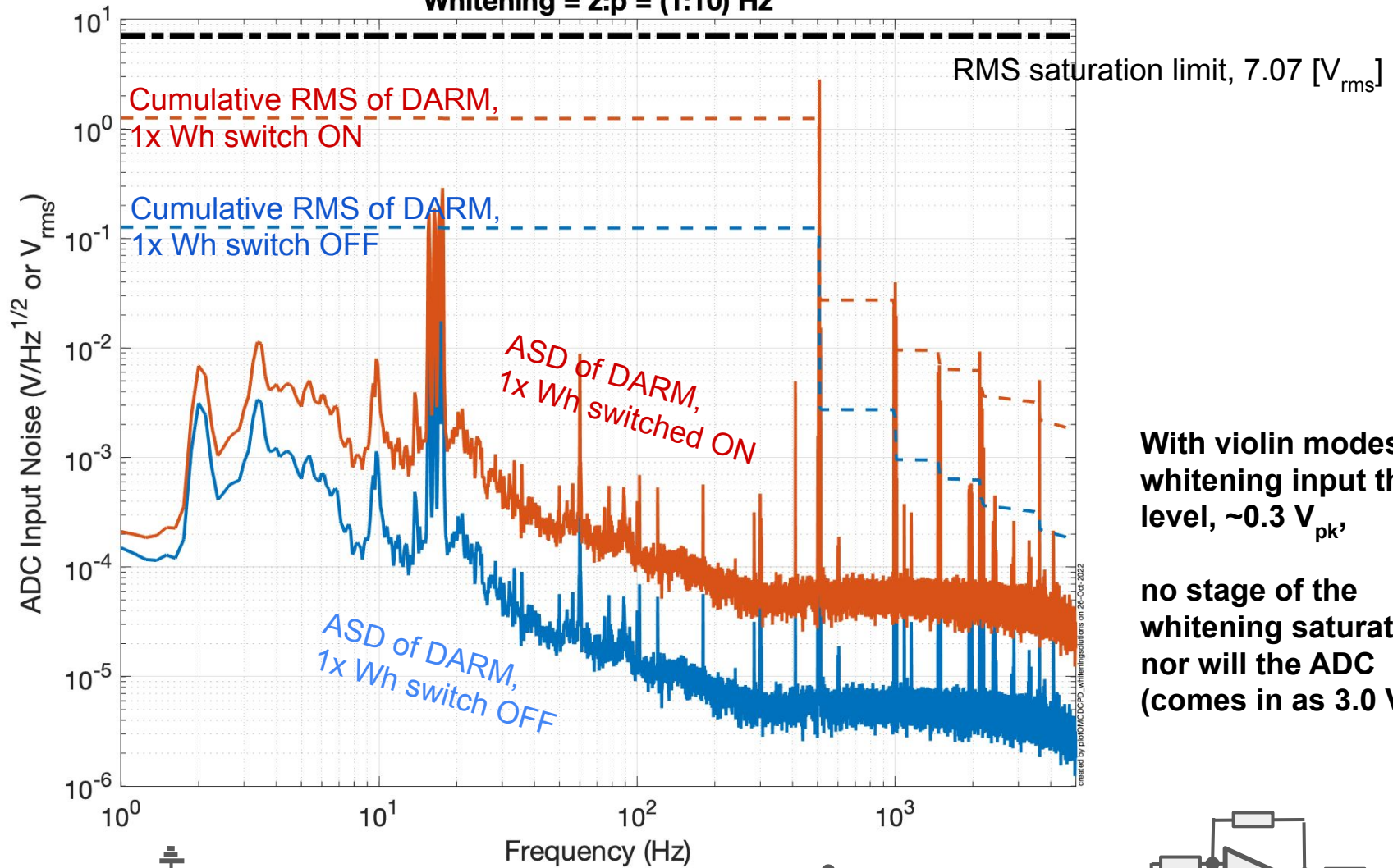


With violin modes at whitening input this level, $\sim 0.3 V_{pk}$,

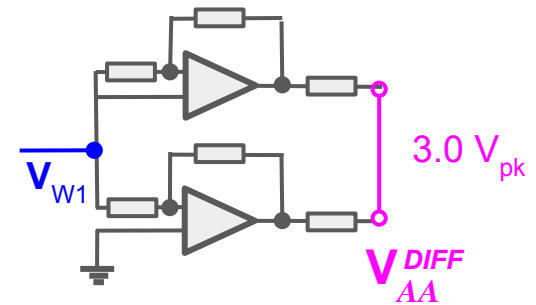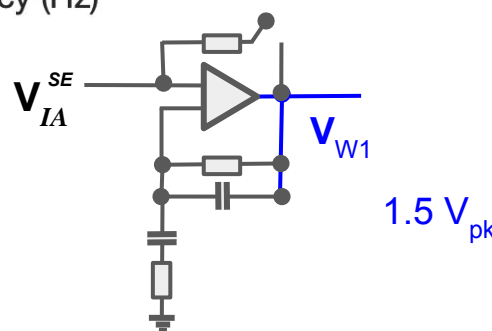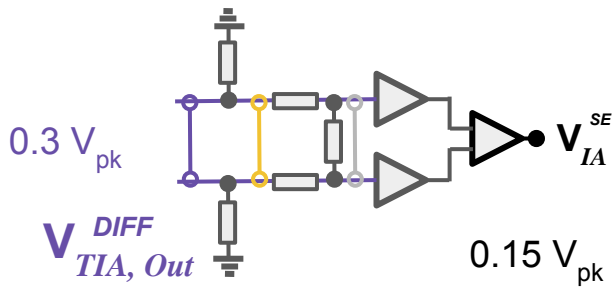no stage of the whitening saturates, nor will the ADC (comes in as $3.0 V_{pk}$).




Design Intent

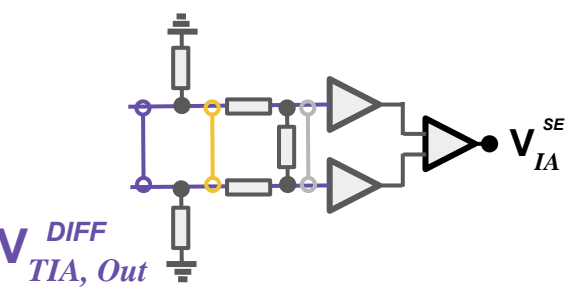

Same differential receiver, but with updated slew-rate limiting pole at ~44.21 kHz, rather than at ~11 kHz


Design Decision 1:

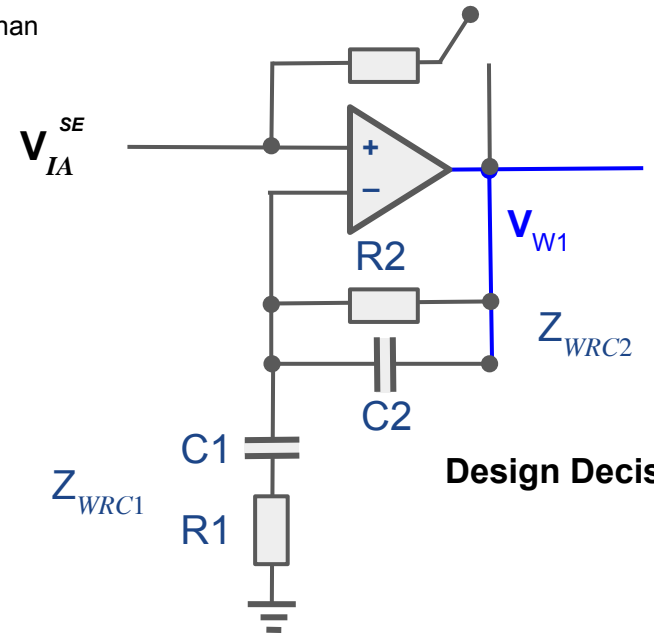- 1x "Standard" stage of Switchable Whitening filter
- Default state is whitening ON (as it was in O3.)
- z:p = 1:10 Hz



Design Decision 2: No DC gain (switchable or not)

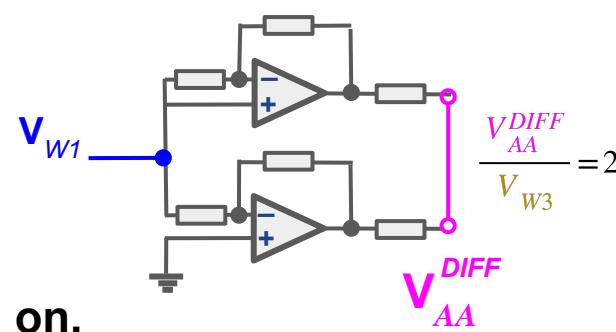Design Decision 3: (carried over from -v1) NO extra 10 kHz Poles in any of these stages. Plenty of 10 kHz poles from TIA and ~44.21 kHz pole from slew-rate limiting filter.



Same differential amplifier

In short: nominal operation has whitening on, with a gain of 10x

Timeline

It's the week of Oct 24 - Nov 4.

Dean says he can have the design finished within ~1-2 weeks of us saying "go for production. Nov 7 - Nov 11 (Maybe another quick review then with all the Altium products finished?)

Can have the chassis back from shops and assembled in 2-3 weeks from that.
Nov 14 - Nov 25.

So, delivery on site is plausible the week of Nov 28 2022.

Jeff / Joe now have experience and understanding of what's coming, and the user interface is a lot more clear, so could measure and compensate the week of Dec 5 - Dec 9.

Great! Let's get this in before O4!

But ... not useful unless both sites have functional low-noise 18-bit ADCs in place.
Open question: how does this jive with the timeline for

- Getting a low-noise 18-bit ADC running at LHO?
- Moving this low-noise 18-bit ADC to another segregated IO chassis?


OTHER UPDATES AND DESIGN CHOICE AIDES

Whitening ON with switch de-energized, LO, 0V
 Bypassed when switch is energized, HI, 5V

△
 Z1 = 1Hz
 P1 = 10Hz

△
 SPDT Relay:
 Contacts: 1.0A continuous current
 Coil: 1.7kohm @ 15V

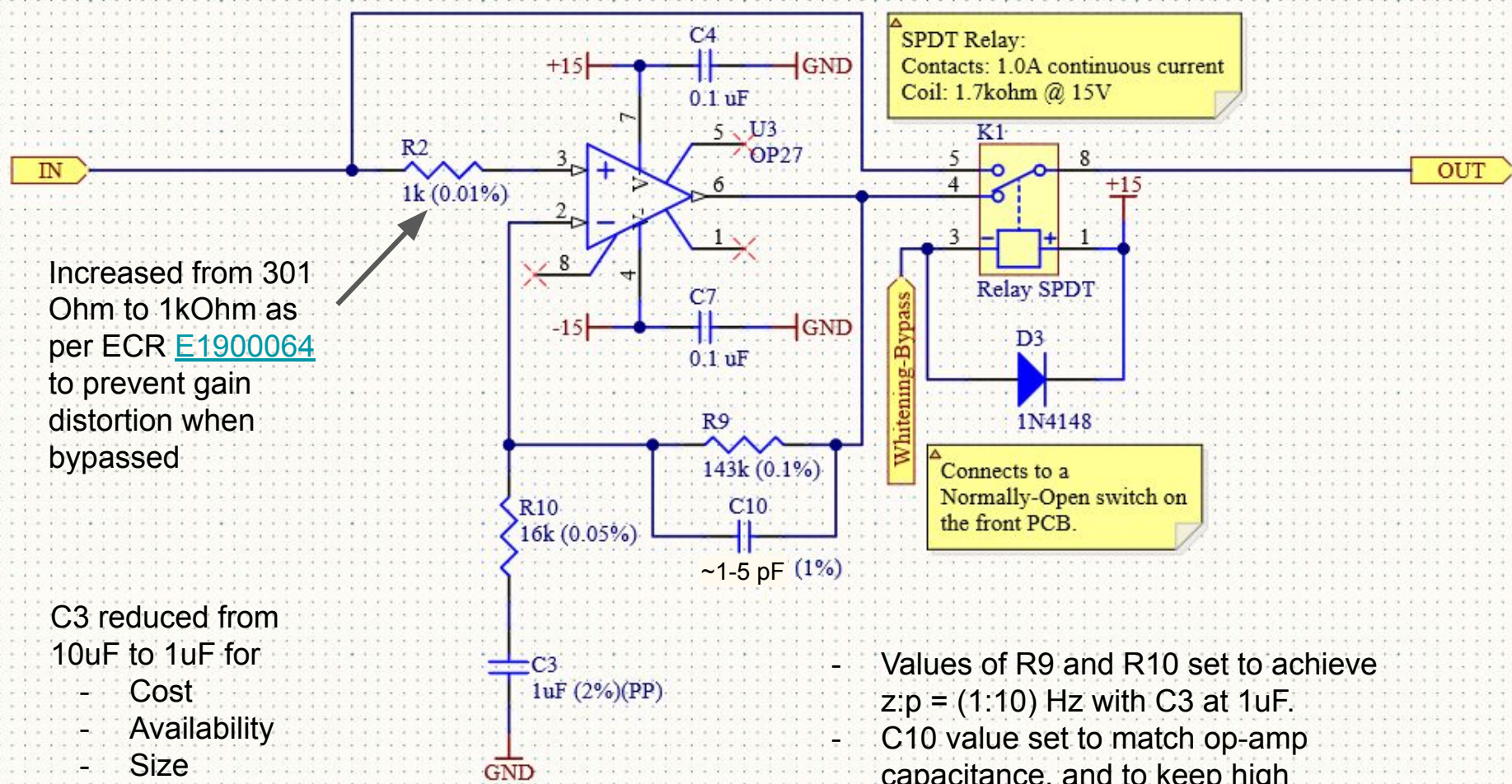△
 Connects to a
 Normally-Open switch on
 the front PCB.





Increased from 301 Ohm to 1kOhm as per ECR [E1900064](#) to prevent gain distortion when bypassed

- C3 reduced from 10uF to 1uF for
- Cost
 - Availability
 - Size

- Values of R9 and R10 set to achieve z:p = (1:10) Hz with C3 at 1uF.
- C10 value set to match op-amp capacitance, and to keep high frequency z:p pair above 100 kHz

PD Signal Readouts – Front-Panel User Interface


PD Signal Monitors

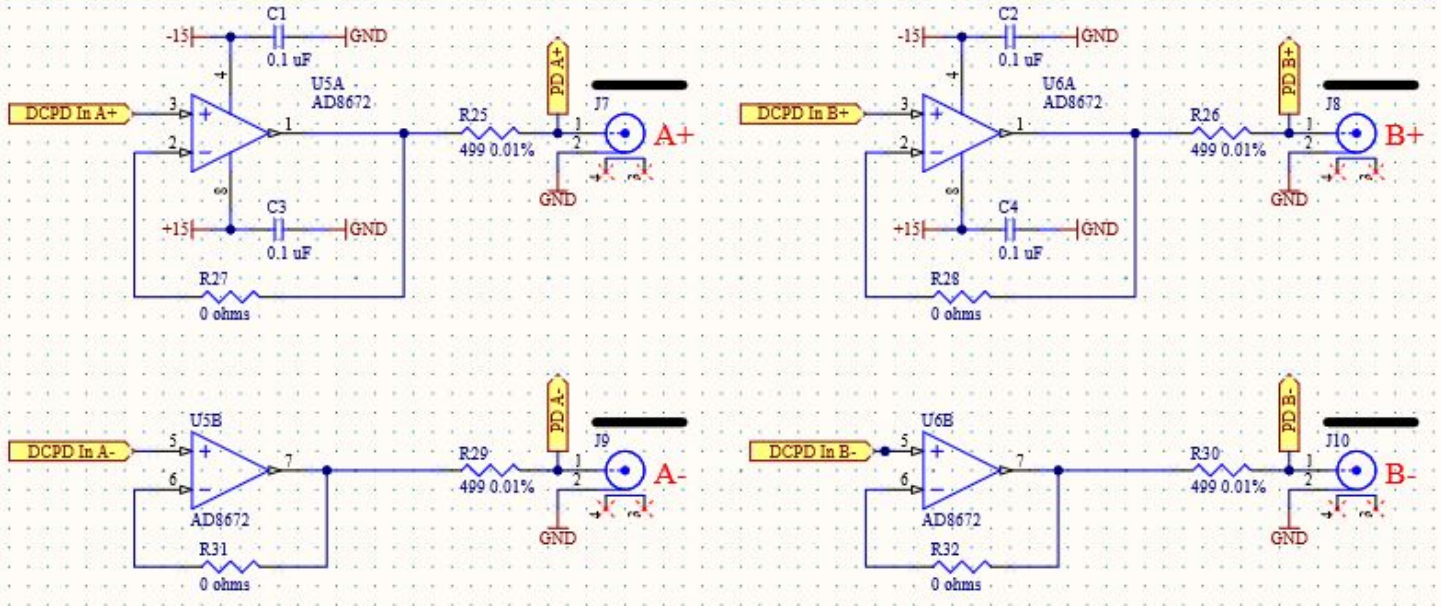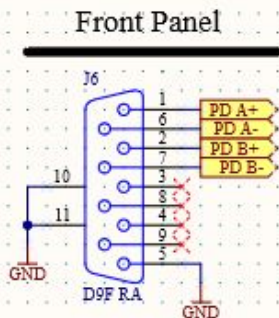

DB9 Differential Output
 For use with SR785
 Accessory Box
 (picked off from buffered
 output just before BNC)

Each leg exposed to BNC for
 quick/diagnostic checks with
 Oscilloscope

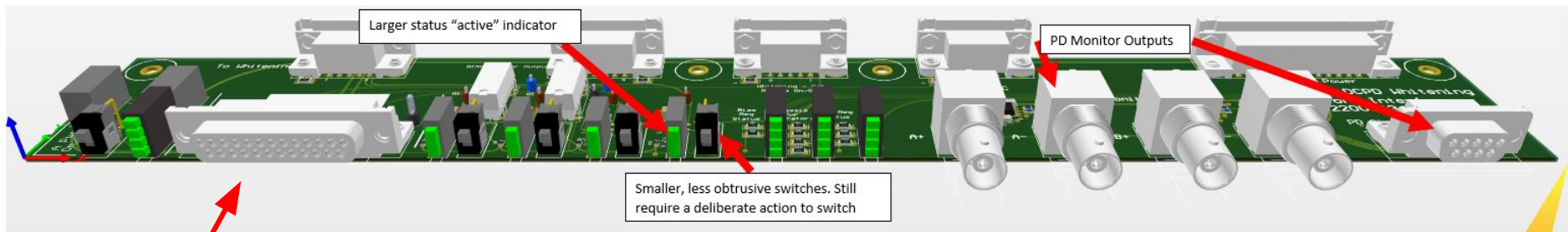PD Signal Readouts – Front-Panel User Interface




DB25 from / to in-vac TIA preamp

What if we read out with several ADC channels?

Out of the scope of this design change, but in case it comes up:
An idea bantered about – because the 18-bit low noise ADC has 32 differential channels available, and we want to segregate the OMC DCPD signals in their own card on their own chassis – why not make copies of the whitening chassis' DCPD voltage output and feed them into multiple channels, then digitally take the average to improve against the ADC noise further?

- 32 available channels on new LN ADC.
- 4 DCPDs, 2 chans per DPCD GW readout and Bias Mon
 - Map 1 DCPD GW readout into 4 ADCs channel.
- 16 + 4 = 20 channels total – plenty enough channels.
- Split the output of the differential receiver into four paths, right out to the DB connector...
- Any need to change the whitening filter design topology (to improve self noise) if we do that? **No.**
 - For copies of 20 nV/rHz noise vs. TIA self noise vs. $\sqrt{2} \cdot (AA+ADC)$ noise...
 - Gut feeling is “no” but if we’re serious about this, we should run the numbers.
- Would we need a new and improved “low noise” AA chassis for this? **No.**
 - Spec for AA chassis has their self noise between 75 to 100e-9 V/rHz.
 - Typical test results have them come in at 30-50 nV/rHz
 - Still well below ~400 nV/rHz of the 18-bit ADC channel.

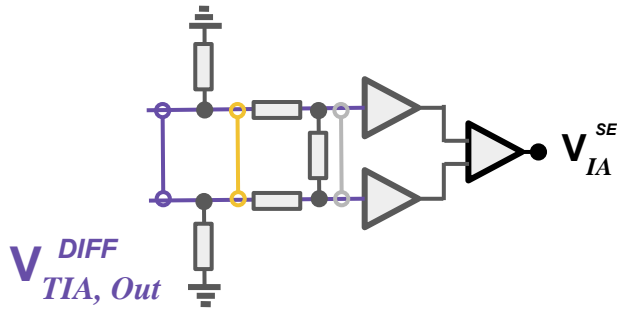Quick note about the slew-rate limiting pole frequency



Previous A+ whitening design had slew-rate limiting filter at

For the [LT1125](#) op amps used.

LT1125 have a slew rate limit of 4.5 [V/us].
For $A = 10$ V sinusoidal signal at frequency
 $\omega = 2 \cdot \pi \cdot f$, then the frequency where we hit
this limit is at

$$\begin{aligned} V &= A \sin(\omega t) \\ dV / dt &= A \omega \cos(\omega t) \\ 4.5e6 \text{ [V/s]} &= 10 \text{ [V]} \omega \cos(\omega t) \\ 2 \cdot \pi \cdot f &= 4.5e6 \text{ [V/s]} / 10 \text{ [V]} \\ f &= 4.5e6 / (2 \cdot \pi \cdot 10) \text{ [Hz]} \\ f &= 71.6e3 \text{ [Hz]} \end{aligned}$$

$$f_p = 71.6 \text{ [kHz]}$$

We don't want to hit this limit, so we've chosen component values ($R=1\text{k}\Omega$, $C=1800\text{pf}$) such that the RC filter – with the C connecting across the two legs, so $C_{eff} = 2C$ – has a pole at

$$f_p = 1 / (2 \cdot \pi \cdot 1e3 \cdot (2 \cdot 1800e-12)) = 44.2 \text{ kHz}$$

Quick Note about Whitening the Bias Monitor

Summary: elected to go without extra whitening for the bias monitor beyond what's in the TIA.

Design criteria: bias noise current to be a factor of 100x below shot noise current (a factor of ten below the factor of ten limit on electronics). Want a *monitor* to be able to detect that level of bias noise.

Assume bias voltage couples in via capacitance of PD, $C_{pd} = 300 \text{ pF}$.

10 mA photocurrent = $\sqrt{2 e I} = 5.6 \text{e-}11 \text{ A/rHz}$

Want to sense 1/10th of shot noise = $5.6 \text{e-}12 \text{ A/rHz}$

$1/(i\omega C_{pd}) * A = 1/(2*\pi*(1 \text{ kHz})*300\text{e-}12 \text{ [F]}) * 5.6\text{e-}12 \text{ [A/rHz]} = \sim 3\text{e-}06 \text{ V/rHz noise}$

Bias monitor in the preamp has a gain of $\sim 20\text{x}$ at in the sensitive LIGO band (DC gain is 2).

So that's = $\sim 6\text{e-}05 \text{ V/rHz noise}$, well above 500 nV/rHz ADC noise.


Other Filter Design Options

- While playing around with whitening we say that a single stage 1:10 Hz whitening filter does still leave some ADC noise in play, reducing the 1 kHz SNR a bit. So we ask a few questions:
- What about a $z:p = 1:20$ Hz filter? A $z:p = 1:25$ Hz? When does the ADC noise *stop* limiting the total electronics noise?
- Also, in those various design scenarios, how much more gain can we tolerate before the system saturates under when violin modes are bad?

These next few slides show plots to show the exploration, but in the end, anything more than the single stage of 1:10 Hz filtering is deemed too much gain (w.r.t. the 10 V limit), and the improvement in SNR is not worth it.

How about 1x stage of 1:20 Hz?

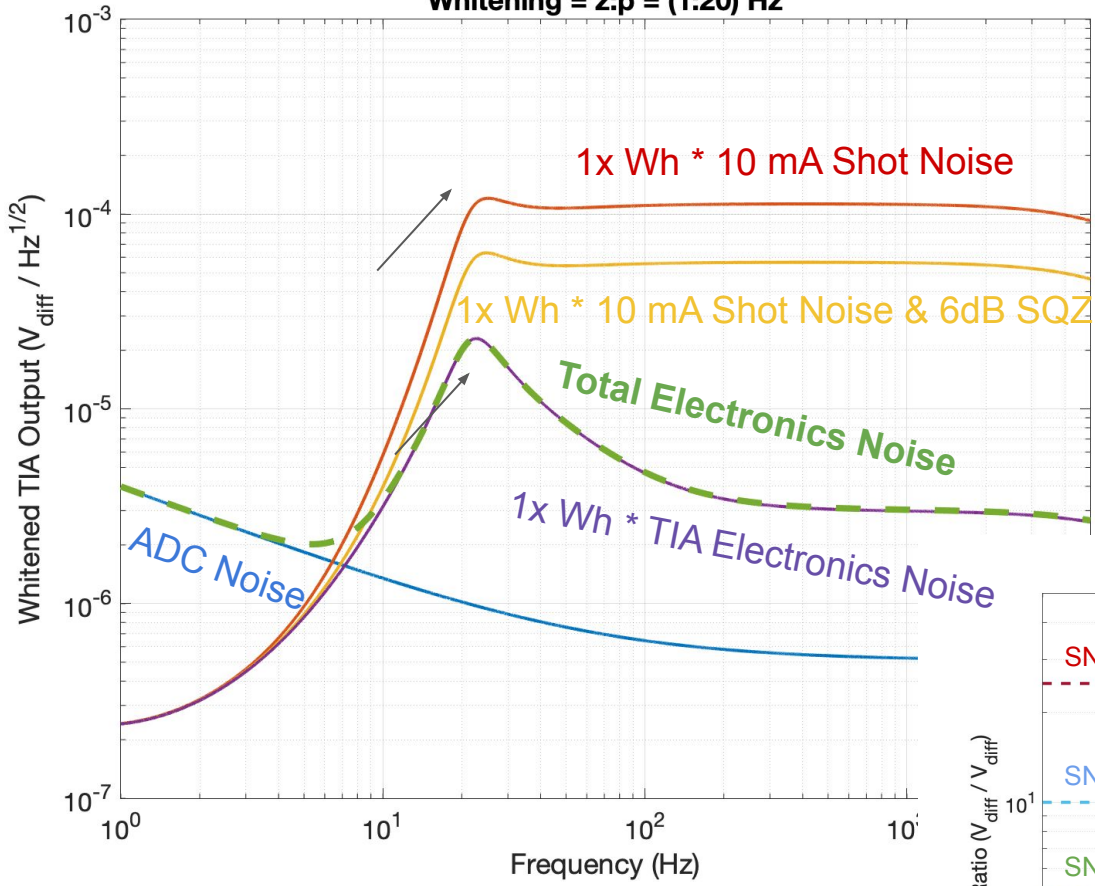Dark Noise & Shot Noise Comparison, Whitenes
Whitening = z:p = (1:20) Hz




1x stage of (1:20) asymptotes to an extra factor of 2x gain above ~20 Hz for a total gain of 20. Quite similar to existing A+ design gain of 25x.

Ensures that **ADC noise** does not contribute at all to **Total electronics noise**.


- With 1x stage of whitening, ADC noise
- Reduces (10 mA) SNR at 1 kHz from **37.52** to **36.95**
 - Reduces (10 mA & 6dB SQZ) SNR at 1 kHz from **18.82** to **18.54**

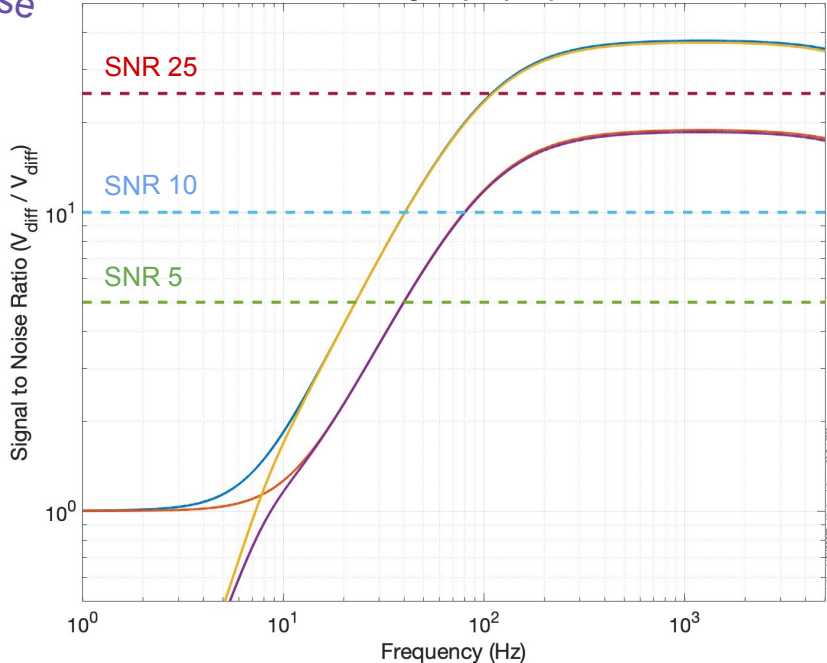Ratio of Shot Noise to Total Electronics Noise
Whitening = z:p = (1:20) Hz




How about 1x stage of 1:20 Hz?

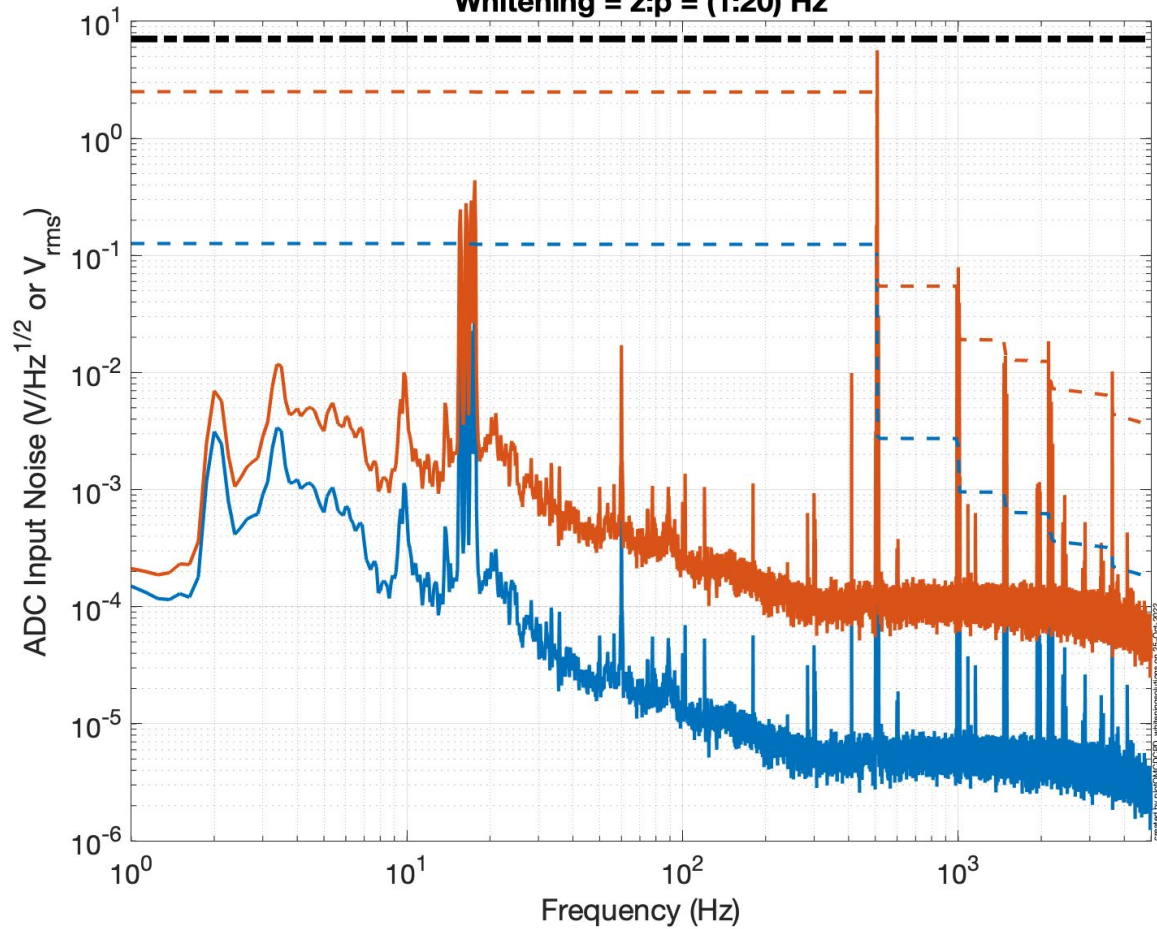Signal Chain Saturation Check
Whitening = z:p = (1:20) Hz



1x stage of (1:20) would not saturate with this example state of violin modes.

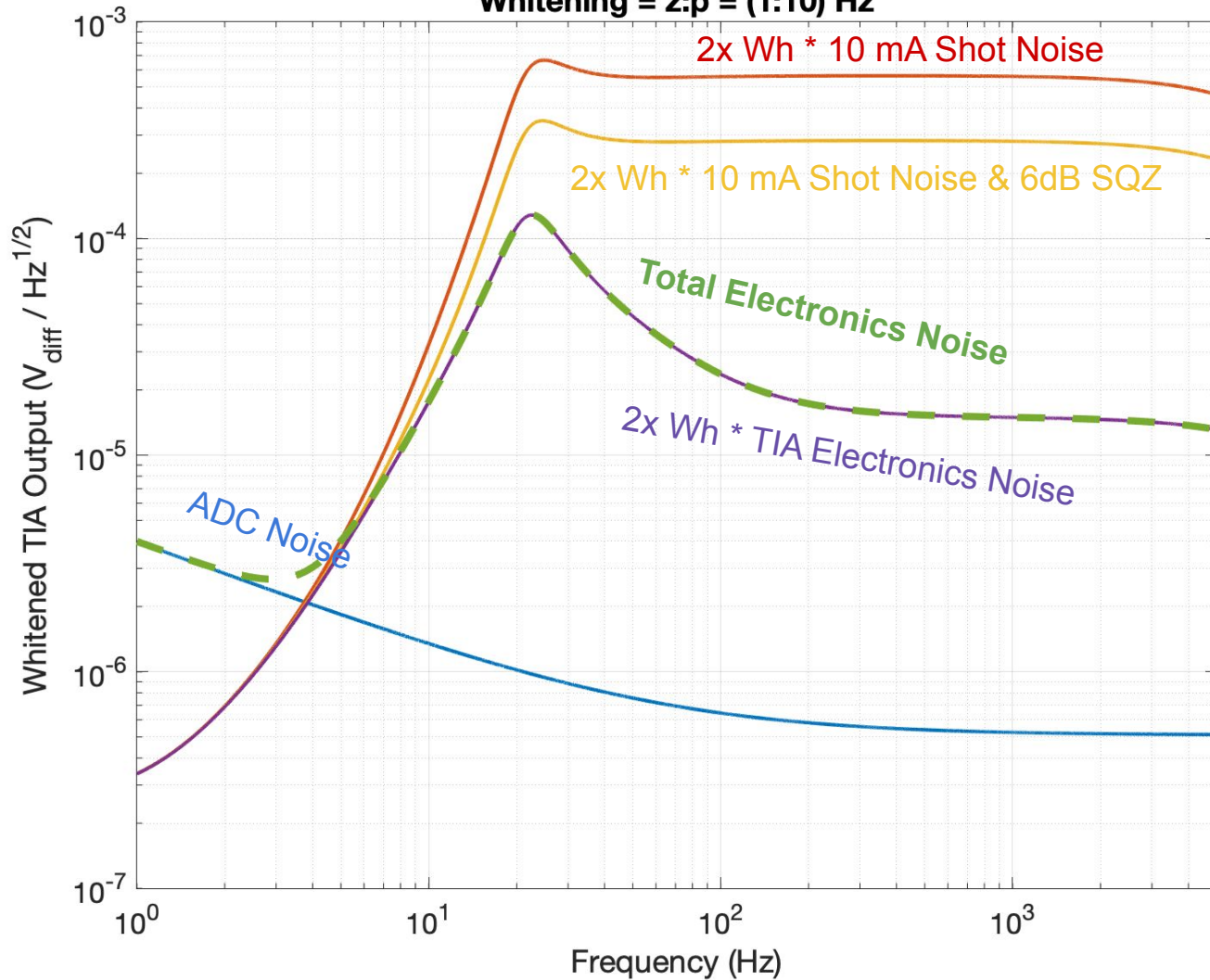Dark Noise & Shot Noise Comparison, Whited Whitening = z:p = (1:10) Hz



Two stages of z:p = 1:10 Hz is likely **too much** voltage gain for too little noise improvement gain.

Noise Improvement:
ADC noise goes from “small” to “negligible” contribution to **total electronics noise**.

The next two slides show that under certain conditions, 2x whitening saturates the signal chain.

Design Intent – Redone / Corrected from -v1

G2201909-v1 design approach was all wrong.

- The **corrected design goal** is now: **preserve “signal-to-noise” ratio** between
 - Shot noise, through the transimpedance amplifier as the “signal” and
 - “Dark” electronics self-noise of the transimpedance amplifier as the “noise”

Cast both noises as “output referred” noises, at the output of the transimpedance amplifier (TIA).
- Mission: create a whitening filter than brings the TIA dark noise, n_{TIA} , well above the new better ADC noise, n_{ADC} .
 - The ADC noise improvement asymptotes to about a factor of ~7x improvement. So, we should expect to need about that much less gain.
 - Former A+ whitening filter design had a gain choice between 25x or 50x in the ~1 kHz region, so we should expect to need *some* whitening, but not a lot.
 - Gain of 25x is currently OK, but need ability to switch it off.
- Whitening filter design must have self-noise, n_{WH} , sufficiently small to not “spoil” the dark noise from the TIA n_{TIA} .
 - -v1 Showed the SNR between shot-noise and ADC noise. It’s not that the signal-to-noise ratio between the ADC “noise” and shot-noise-through-the preamp “signal” “does not matter,” it was just **the wrong metric**. We want


$$n_{TIA} > \sqrt{n_{WH}^2 + n_{ADC}^2},$$

such that it remains true that

$$n_{shot} \gg \sqrt{n_{TIA}^2 + n_{WH}^2 + n_{ADC}^2}$$

- Re: saturations – every electronics component from the TIA to the ADC has +/- 15 V range. That means if the ADC is saturating, then it’s likely that the TIA is also saturating. Thus, there’s no point in putting any low-passing in the signal chain below a gain of 1.0 V/V.
 - The -v1 design suggested **low-passing below a gain of 1.0, and that was wrong**.
 - It also suggested putting a whitening filter up-stream of the low-passing. That also doesn’t make sense, because if the whitening stage is saturating, then **sending a saturated signal into the low-pass won’t work**.

Whitening for below 20 Hz? No.

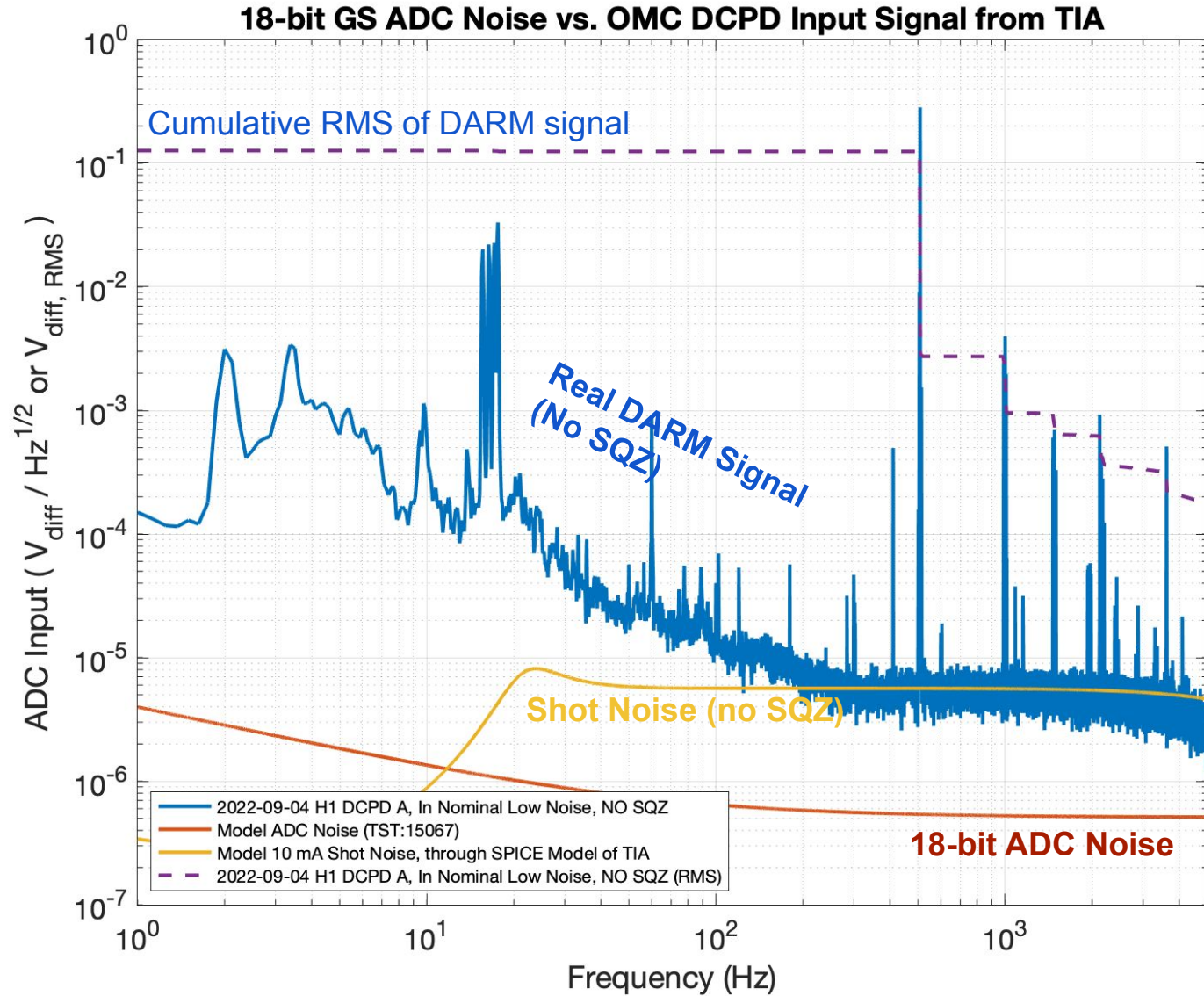

What's the **blue trace**?


Real DARM signal (no SQZ). Quick and dirty recent imperfect data from LHO but good enough for this.

Took a “**representative**” ASD of the H1 DCPDs via front-end [mA / rHz], during nominal low-noise, and multiplied it by the TIA transfer function. Random day of H1 data, (2022-09-04 16:04:00 UTC), with

- **No Squeezing**
- OK **violin Modes**, with 500 Hz peak heights at $\sim 1e-15$ m/rHz (bad days are $1e-14$ m/rHz)
- **DARM loop suppression** ***not*** taken out (if I did “do it right” low-frequency ASD would only get louder, increasing the SNR)

Below ~ 100 Hz, **signal** dominates **shot noise** and remains large w.r.t to **new 18-bit ADC noise**. No need to any low-frequency whitening.

Loop Suppression Removal Demo

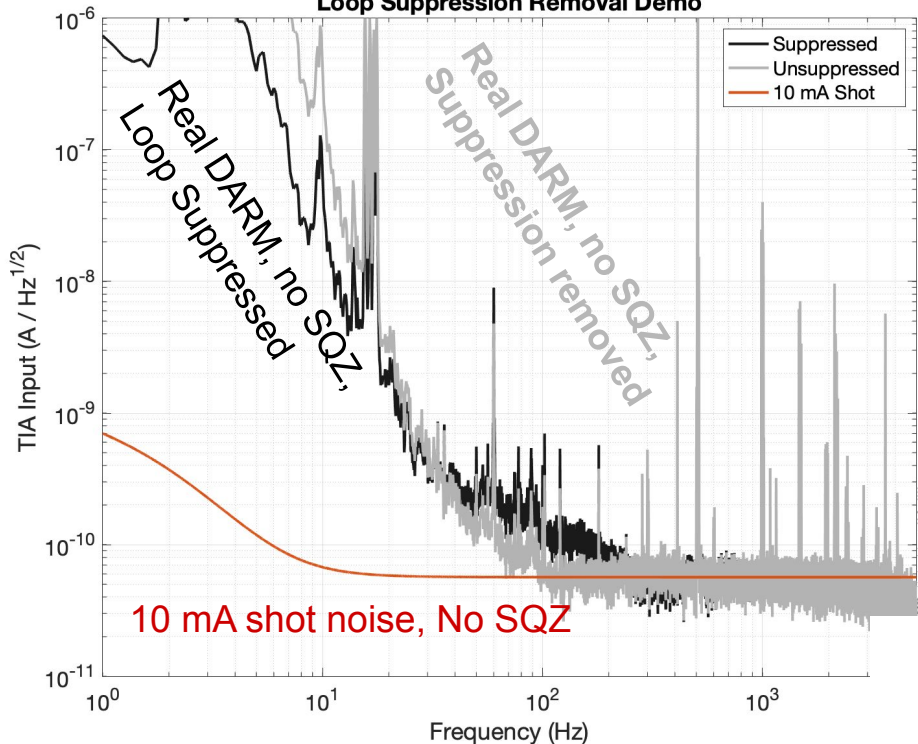

What does the current on the PDs look like if I *do* take out the loop suppression?


As expected, the unsuppressed current is only larger w.r.t. the electronics noise.

For comparison between

- unsuppressed, real DARM, thru TIA and 1x (1:10) Wh
- Unsuppressed, 10 mA shot, thru TIA and 1x (1:10) Wh
- TIA electronics noise thru 1x stage of (1:10) Hz Wh
- Electronics noise from 1x stage of (1:10) Wh itself
- ADC noise,

See slide 6.


Loop Suppression Removal Demo

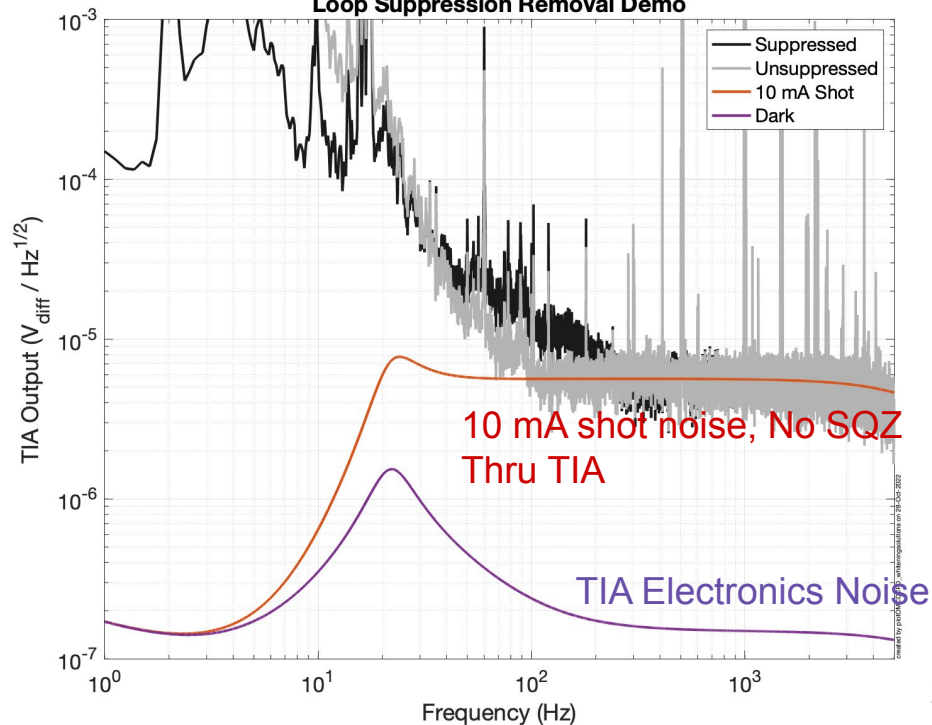

Final Answer Plots Again (pages 6, 7 and 8),
but with no messaging


Dark Noise & Shot Noise Comparison, Whitened

Whitening = z:p = (1:10) Hz

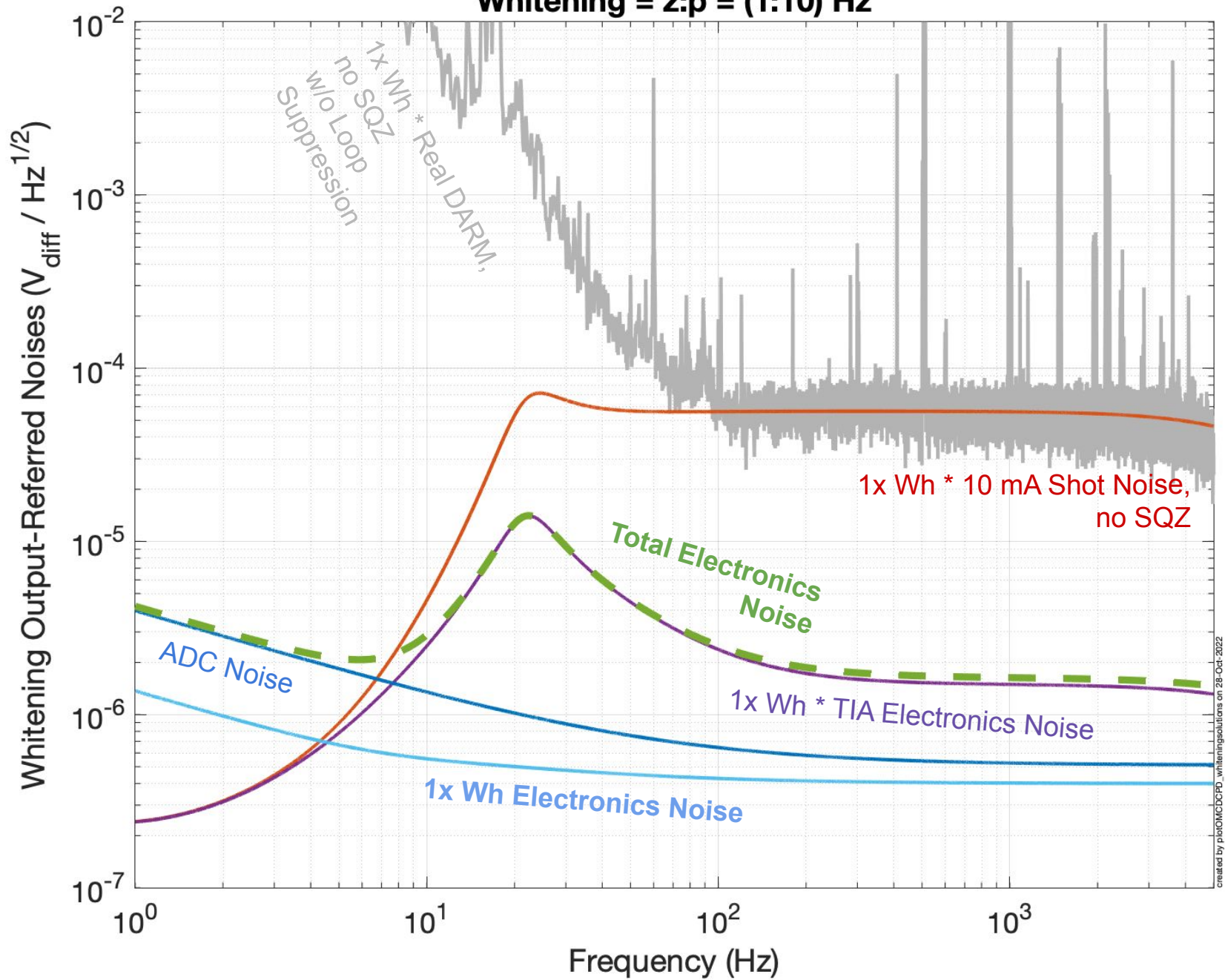

Dark Noise & Shot Noise Comparison, Whitenes

Whitening = z:p = (1:10) Hz

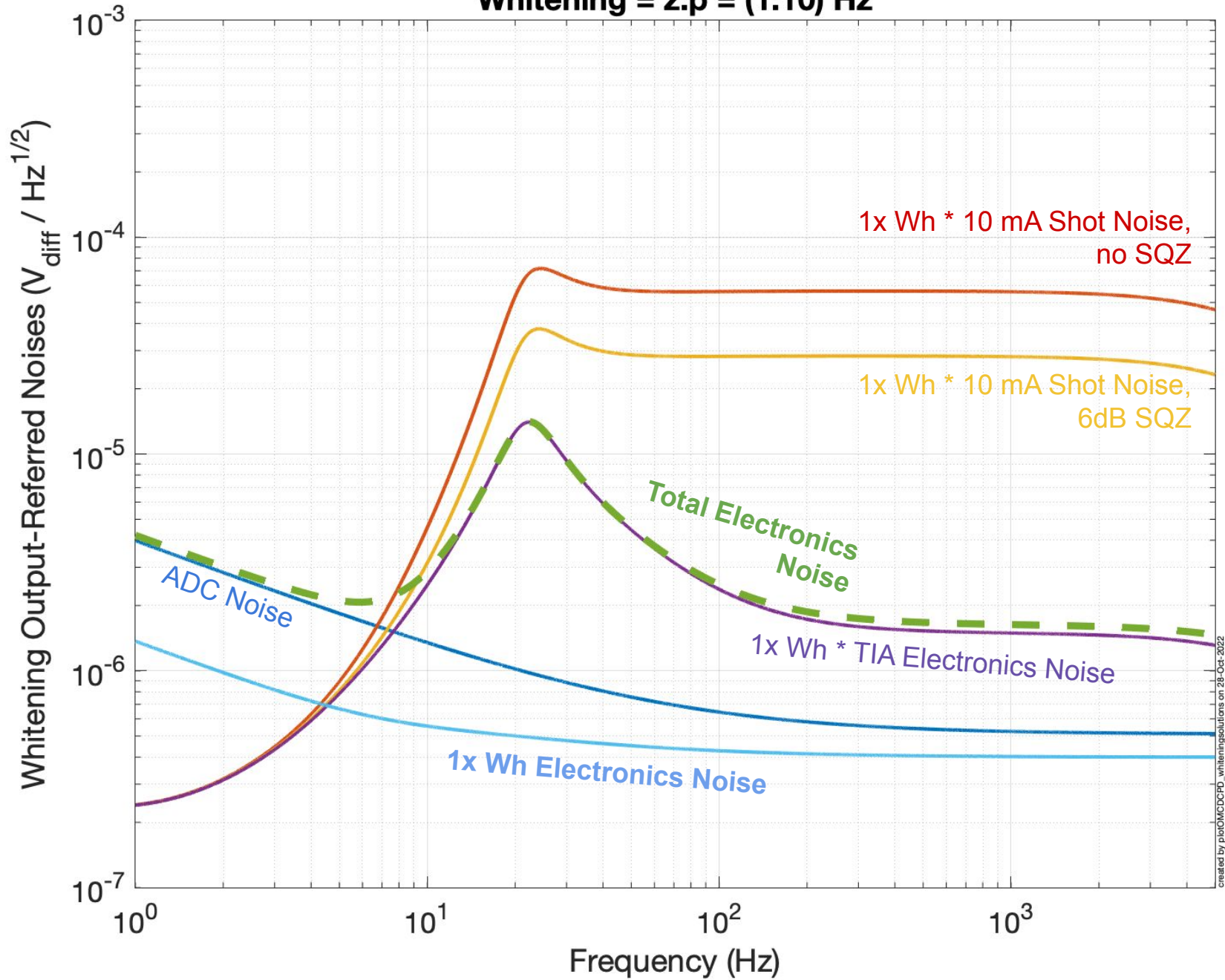

Ratio of Shot Noise to Total Electronics Noise

Whitening = z:p = (1:10) Hz

